

02-Phasors

ECEGR 450
Electromechanical Energy Conversion



Overview

- Phasors Transform
- Phasor Mathematics
- Circuit Analysis Using Phasors

Dr. Louie

2



Questions

Why are AC circuits solved in the phasor domain?

Dr. Louie

3



Phasors

- Analysis of circuits with R, L and/or C components requires solving differential equations
- We will consider only sinusoidal steady-state voltages and currents of the same frequency
- We can then analyze the circuits in the phasor domain much easier than in the time domain

Dr. Louie

4



Phasor Transform

- Shorthand for writing sinusoidal functions
- Used for steady-state calculations
- Contains **amplitude** and **phase angle** information
 - Assumed that frequency is known
- Relies on Euler's Identity

$$v(t) = v_{\max} \cos(\omega t + \theta_v) \xrightarrow{\text{Phasor Transform}} V_{\max} \angle \theta_v$$

Dr. Louie

5

Phasor Transform

$$v(t) = v_{\max} \cos(\omega t + \theta_v) \quad \text{time-domain representation}$$

$$e^{\pm jx} = \cos(x) \pm j \sin(x) \quad \text{Euler's Identity}$$

$$v(t) = v_{\max} \operatorname{Re} \left\{ e^{j(\omega t + \theta_v)} \right\} \quad \text{using Euler's Identity}$$


$$v(t) = v_{\max} \operatorname{Re} \left\{ e^{j\omega t} e^{j\theta_v} \right\} \quad \text{implied, so we suppress this regrouped}$$

$$v(t) = v_{\max} e^{j\theta_v} = V_{\max} \angle \theta_v \quad \text{transformed}$$

$$\mathbf{V} = \frac{v_{\max}}{\sqrt{2}} e^{j\theta_v} = V_{\text{rms}} e^{j\theta_v} \quad \text{in power we divide by } \sqrt{2}, \text{ also known as the effective phasor}$$

Dr. Louie


6



Phasor Transform

- We use the effective phasor because
 - $P = v_{rms} i_{rms} \cos(\phi)$
 - So we can then write $P = VI \cos(\phi)$
- Unless otherwise specified, assume that voltages and currents are given in RMS and all phasors are "effective phasors"
- Also note:
 - $e^{-j90^\circ} = \cos(-90^\circ) + j \sin(-90^\circ) = j \sin(-90^\circ) = -j$


Dr. Louie **7**



Notation

- A bug in the notation
- Book uses a tilde to indicate that a variable is a phasor, as in \tilde{V} , \tilde{I}
 - In other words, \tilde{V} , \tilde{I} are understood to have a magnitude and phase component
- Book uses V , I to indicate the magnitude of the phasor


Dr. Louie **8**



Notation

- Lecture slides use bold uppercase variables (e.g. **V**, **I**) for phasors and other vectors
- Capital letters (e.g. V , I) or absolute values of phasors ($|\mathbf{V}|$, $|\mathbf{I}|$) are used to indicate the magnitude of the phasor
 - $\mathbf{v} = V \angle \theta$
- Lowercase variables (e.g. v , i) are preferred to represent scalars not associated with phasors and vectors
 - Notable exceptions P , Q for real and imaginary power


Dr. Louie **9**



Phasors

- write the phasor representation of $v_1(t) = 1.41 \cos(377t + 0)$
- write the phasor representation of $v_2(t) = 2.12 \cos(377t + 45)$
- write the phasor representation of $v_3(t) = 1.41 \cos(t + 0)$


Dr. Louie **10**



Phasors

<ul style="list-style-type: none"> • write the phasor representation of $v_1(t) = 1.41 \cos(377t + 0)$ • write the phasor representation of $v_2(t) = 2.12 \cos(377t + 45)$ • write the phasor representation of $v_3(t) = 1.41 \cos(t + 0)$ 	<p>solution</p> <p>$\mathbf{V}_1 = 1 \angle 0^\circ$</p> <p>solution</p> <p>$\mathbf{V}_2 = 1.5 \angle 45^\circ$</p> <p>solution</p> <p>$\mathbf{V}_3 = 1 \angle 0^\circ$</p>
--	---


Dr. Louie **11**



Phasors

Phasors have a direct geometric interpretation

- Polar form

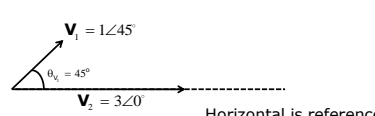

$\mathbf{V}_1 = 1 \angle 45^\circ$

$\theta_{V_1} = 45^\circ$

$\mathbf{V}_2 = 3 \angle 0^\circ$

Horizontal is reference

Dr. Louie **12**

Phasors

- Another way of specifying phasors is in rectangular form
 - Let the Y-axis be the imaginary (j) axis
 - Let the X-axis be the real axis
- Resolving into real and imaginary components
 - $V_1 = 1\angle 45^\circ = 0.707 + j0.707$
 - $V_2 = 3\angle 0^\circ = 3 + j0$

Dr. Louie 13

Addition of Phasors

- Addition and subtraction of phasors are simple using rectangular form
 - Simply add/subtract the real values and add/subtract the imaginary values

$$V_3 = V_1 + V_2 = 3.707 + j0.707$$

Addition is "tip to tail"
Subtraction is "tail to tip"

Dr. Louie 14

Phasors

- To convert from rectangular to polar:
 - $V = a + jb$
 - $V = V\angle\theta = \sqrt{a^2 + b^2} \angle \tan^{-1}\left(\frac{b}{a}\right)$

Dr. Louie 15

Phasors

- What is V_3 in Phasor form?
 $V_3 = 3.707 + j0.707$

Dr. Louie 16

Phasors

- What is V_3 in Phasor form?
 $V_3 = 3.707 + j0.707$
- $V = V\angle\theta = \sqrt{3.707^2 + 0.707^2} \angle \tan^{-1}\left(\frac{0.707}{3.707}\right) = 3.77\angle 10.8^\circ$

Dr. Louie 17

Phasors

- What is V_3 in the time domain?

Dr. Louie 18

Phasors

- What is \mathbf{V}_3 in the time domain?
 $v(t) = 3.77\sqrt{2} \cos(\omega t + 10.8^\circ)$

Dr. Louie 19

Multiplication of Phasors

- Multiplication and division are easier in polar form
 - For multiplication: multiply magnitudes, add angles
 - For division: divide magnitudes, subtract angles

$$\mathbf{V}_4 = \mathbf{V}_1 \mathbf{V}_2 = (1 \angle 45^\circ)(3 \angle 0^\circ)$$

$$\mathbf{V}_4 = 3 \angle 45^\circ$$

Dr. Louie 20

Multiplication of Phasors

Using Matlab

```
>> V1=1*exp(j*45*pi/180)
V1 =
    0.7071 + 0.7071i
>> V2=3*exp(j*0*pi/180)
V2 =
     3
>> V3=V1+V2
V3 =
    3.7071 + 0.7071i
>> Vmag=abs(V3)
Vmag =
    3.7739
>> Vanglerad=angle(V3)
Vanglerad =
    0.1885
>> Vangledeg=Vanglerad*180/pi
Vangledeg =
    10.7991
```

Dr. Louie 21

Phasor Analysis of Inductors

- For inductors
 $i(t) = i_{\max} \cos(\omega t + \theta_i)$
 $v(t) = L \frac{di}{dt}$
 $v(t) = -L\omega i_{\max} \sin(\omega t + \theta_i) = -L\omega i_{\max} \cos(\omega t + \theta_i - 90^\circ)$
- Transforming into phasor form:
 $v(t) = -L\omega i_{\max} \cos(\omega t + \theta_i - 90^\circ)$
 $\Rightarrow \mathbf{V} = -L\omega \mathbf{I} e^{j90^\circ} = jL\omega \mathbf{I}$
 using $e^{j90^\circ} = j$

Dr. Louie 22

Phasor Analysis

$\mathbf{V} = j\omega \mathbf{L} \mathbf{I}$

- Define $X_L = \omega L$ (inductive reactance)
- Therefore
 - $\mathbf{V} = jX_L \mathbf{I}$
- A similar derivation for capacitors yields
 - $X_C = -1/(\omega C)$ (capacitive reactance)
 - $\mathbf{V} = jX_C \mathbf{I}$

Dr. Louie 23

Phasor Analysis

- We can rewrite Ohm's Law to include complex impedances
- $\mathbf{V} = \mathbf{Z} \mathbf{I}$
 - \mathbf{Z} : complex impedance (Ohms)
 - $\mathbf{Z} = R + jX_L + jX_C$ (if in series)
 - $1/\mathbf{Z} = 1/R + j/X_L + j/X_C$ (if in parallel)
- \mathbf{Z} will have a magnitude and phase associated with it $\mathbf{Z} = Z \angle \theta_z$

Dr. Louie 24

Phasor Analysis

- Z** can be found by adding the R, X_L and X_C if in series
 - $\mathbf{Z} = R + jX_C + jX_L$
- Example
 - $\mathbf{Z} = 10 + -j2 + j3$
 - $\mathbf{Z} = 10 + j$ (rectangular coordinates)

Note:
 $\text{Re}\{\mathbf{Z}\} = R$
 $\text{Im}\{\mathbf{Z}\} = X_C + X_L$

Dr. Louie 25

Phasor Analysis

- Parallel:
 - $1/\mathbf{Z} = 1/R + 1/(-jX_C) + 1/(jX_L)$
- Example
 - $1/\mathbf{Z} = 1/10 + 1/(j3) = 0.1 - 0.333j$
 - $\mathbf{Z} = 2.87 \angle 73.3^\circ$

Dr. Louie 26

Phasor Analysis

- Note:
 - $|\mathbf{V}| = V_{rms}$ (magnitude of the phasor)
 - $|\mathbf{I}| = I_{rms}$
- Using phasors
 - $\mathbf{V} = \mathbf{I}\mathbf{Z}$
 - $P = |\mathbf{V}||\mathbf{I}|\cos(\phi)$
 - $P = |\mathbf{I}|^2R = |\mathbf{V}|^2/R$

Dr. Louie 27

Phasor Analysis

- Find the current out of the source, the power out of the source, and power consumed by the resistor assuming:
 - $V_s = 120$ Volts at 60 Hz
 - $L = 0.01$ Henry
 - $R = 10$ Ohms

Dr. Louie 28

Phasor Analysis

- $V_s = 120$ Volts (RMS) at 60 Hz
- $L = 0.01$ Henry
 - $jX_L = j\omega L = j(60 \times 2\pi) \times 0.01 = j3.77$
- $R = 10$ Ohms

Dr. Louie 29

Phasor Analysis

$$\mathbf{Z} = (3.77j + 10) = \sqrt{3.77^2 + 10^2} \angle \tan^{-1}\left(\frac{3.77}{10}\right)$$

$$\mathbf{Z} = 10.69 \angle 20.7^\circ \Omega$$

$$\mathbf{V}_s = \mathbf{I}\mathbf{Z}$$

$$\mathbf{I} = \frac{120 \angle 0^\circ}{10.69 \angle 20.7^\circ} = 11.22 \angle -20.7^\circ \text{ A}$$

phasor diagram

Dr. Louie 30



Phasor Analysis


- Power from the source

$$P = |\mathbf{V}_s| |\mathbf{I}| \cos(\phi) = (120)(11.22) \cos(20.7^\circ) = 1.26 \text{ kW}$$

- Power consumed by the load resistor

$$P = |\mathbf{I}|^2 R = 11.22^2 \times 10 = 1.26 \text{ kW}$$

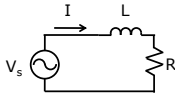- The inductor does not consume any power P



Dr. Louie

31



Summary

- Phasor Domain: allows steady state AC circuits to be easily analyzed (also graphical interpretation)

- Phasors: magnitude and phase info; freq. is assumed

$$\mathbf{V} = \frac{V_{\max}}{\sqrt{2}} e^{j\theta_v} = V_{\text{rms}} e^{j\theta_v}$$

- Effective phasors are used in power systems

$$\mathbf{V}_s = \mathbf{I} \mathbf{Z}$$

- Ohm's Law in phasor domain:

Dr. Louie

32