

03-Real, Imaginary and Complex Power

ECEGR 450
Electromechanical Energy Conversion



Overview

- Complex Power
- Power Triangle
- Examples

Dr. Louie

2



Questions

- How are Real, Reactive and Apparent Power different? How are they related?
- What is "Imaginary" power?

Dr. Louie

3



Complex Power

P is also known as Real Power, Active Power, Average Power
 $P = \mathbf{V}_s \cdot \|\mathbf{I}\| \cos(\phi)$

$$P = \frac{V_{\max}}{\sqrt{2}} \frac{i_{\max}}{\sqrt{2}} \cos(\theta_v - \theta_i)$$

$$P = \text{Re} \left\{ \frac{V_{\max}}{\sqrt{2}} \frac{i_{\max}}{\sqrt{2}} e^{j(\theta_v - \theta_i)} \right\} \quad \text{using } e^{z \pm jx} = \cos(x) \pm j \sin(x)$$

$$P = \text{Re} \left\{ \frac{V_{\max}}{\sqrt{2}} \frac{i_{\max}}{\sqrt{2}} e^{j\theta_v} e^{-j\theta_i} \right\}$$

$$P = \text{Re} \left\{ \frac{V_{\max}}{\sqrt{2}} e^{j\theta_v} \frac{i_{\max}}{\sqrt{2}} e^{-j\theta_i} \right\}$$

$P = \text{Re} \{ \mathbf{VI}^* \}$ * is the complex conjugate operator, it denotes a change in sign of the imaginary part

Dr. Louie

4



Complex Power

- Let **S** be the complex power defined as
 $\mathbf{S} = \mathbf{IV}^*$
 then
 $P = \text{Re} \{ \mathbf{IV}^* \} = \text{Re} \{ \mathbf{S} \}$
- Let Q be the reactive power defined as
 $Q = \text{Im} \{ \mathbf{VI}^* \}$
- Then Q is also known as imaginary power
 $Q = \text{Im} \{ \mathbf{S} \}$
- And therefore: S is also known as apparent power
 $\mathbf{S} = P + jQ$

Dr. Louie

5



Complex Power

- Technically, units of **S**, Q and P are watts*
- To avoid confusion, alternate units are used in practice
 - S: Volt-Amps (VA)
 - Q: Volt-Amps Reactive (VAR)
- Inductors, capacitors consume/supply reactive power, Q
- S and Q are defined values
 - a meaningful physical interpretation is elusive

*See C. Gross "On VA's, VAR's, and Other Traditions in Electric Power Engineering"

Dr. Louie

6

Power Triangle

- Relationships between \mathbf{S} , P and Q can be shown graphically
- $\mathbf{S} = P + jQ$

Note:
P, Q are scalars representing the real and imaginary parts of \mathbf{S}

Dr. Louie 7

Power Triangle

- Consider $P = |\mathbf{V}||\mathbf{I}|\cos(\phi)$
- Since $|\mathbf{S}| = |\mathbf{V}\mathbf{I}^*| = |\mathbf{V}\mathbf{I}| = |\mathbf{V}||\mathbf{I}|$
- Then $P = |\mathbf{S}|\cos(\phi)$
 - P is the projection of \mathbf{S} onto the real axis

Dr. Louie 8

Complex Power

- A similar result can be found for Q
 - $P = |\mathbf{S}|\cos(\phi)$
 - $Q = |\mathbf{S}|\sin(\phi)$
- Q is the projection of \mathbf{S} onto the imaginary axis

Dr. Louie 9

Complex Power Cheat Sheet

$P = \text{Re}\{\mathbf{VI}^*\}$ $= \text{Re}\{\mathbf{IZI}^*\} = \mathbf{I} ^2 \text{Re}\{\mathbf{Z}\}$ $P = \mathbf{I} ^2 R$ $P = \mathbf{V} \mathbf{I} \cos\phi$ $P = \mathbf{I} ^2 \mathbf{Z} \cos\phi$	$Q = \text{Im}\{\mathbf{VI}^*\}$ $Q = \mathbf{I} ^2 X$ $Q = \mathbf{V} \mathbf{I} \sin\phi$ $Q = \mathbf{I} ^2 \mathbf{Z} \sin\phi$
---	--

$\mathbf{S} = P + jQ$
 $\phi = \tan^{-1}(Q/P)$
 $\cos\phi = \frac{P}{\sqrt{P^2 + Q^2}}$

Dr. Louie 10

Example





- Find \mathbf{S} , P and Q for the shown circuit if X_L is 5 Ohms and $V_s = 120$

Dr. Louie 11

Example

- Find \mathbf{S} , P and Q for the shown circuit if X_L is 5 Ohms and $V_s = 120$
 - $\mathbf{V} = \mathbf{V}_s$
 - $\mathbf{Z} = jX_L$
 - $\mathbf{I} = \mathbf{V}_s/\mathbf{Z} = 24\angle -90^\circ$
 - $\phi = 0^\circ - -90^\circ = 90^\circ$
 - $P = |\mathbf{V}||\mathbf{I}|\cos(90^\circ) = 0 \text{ W}$
 - $Q = |\mathbf{I}|^2 X = 2880 \text{ VAR}$
 - $\mathbf{S} = \mathbf{VI}^* = 2880\angle 90^\circ = 0 + j2880 \text{ VA}$

Dr. Louie 12

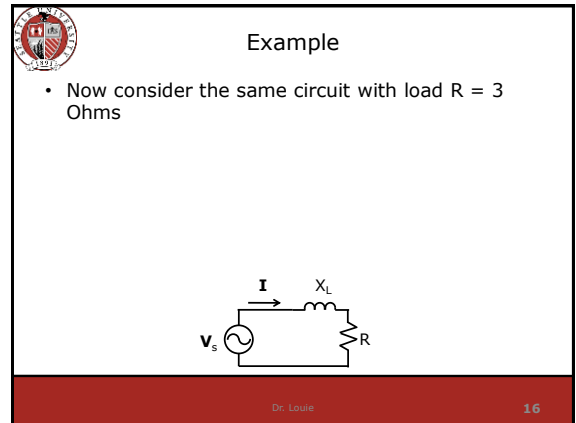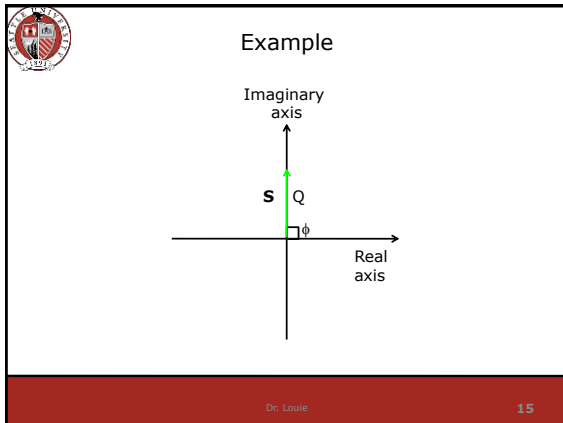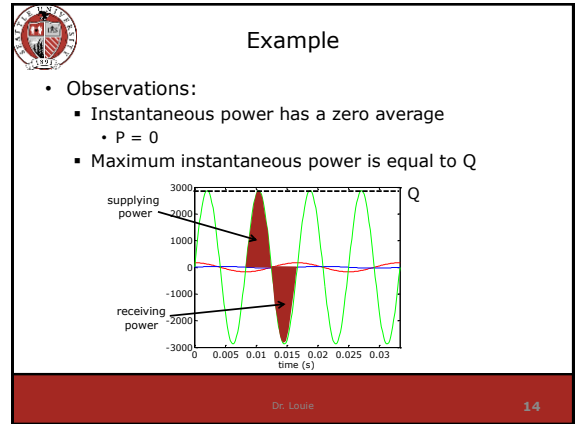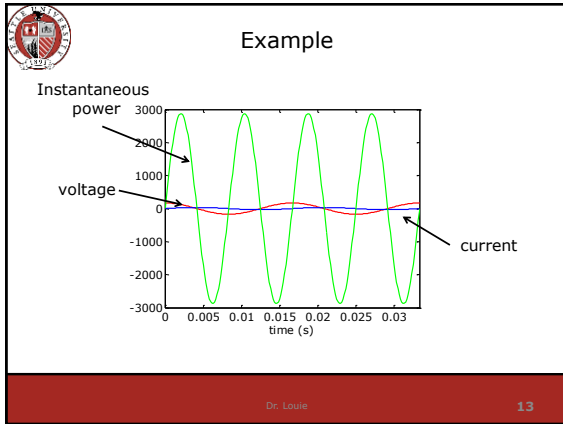

Example

- Now consider the same circuit with load $R = 3$ Ohms
 - $\mathbf{V} = \mathbf{V}_s$
 - $\mathbf{Z} = R + jX_L = 3 + 5j$
 - $\mathbf{I} = \mathbf{V}_s / \mathbf{Z} = 10.58 - 17.65j = 20.58 \angle -59^\circ$
 - $P = |\mathbf{V}| |\mathbf{I}| \cos(59^\circ) = 1272 \text{ W}$
 - $Q = |\mathbf{V}| |\mathbf{I}| \sin(59^\circ) = 2117 \text{ VAR}$
 - $\mathbf{S} = \mathbf{VI}^* = 1272 + j2117 = 2469 \angle 59^\circ \text{ VA}$

Dr. Louie 17

