


05-Three Phase Analysis

Text: 2.4 - 2.7


ECEGR 451
Power Systems




Overview

- Three-Phase Sources
- Delta and Y Connections
- Three-Phase Loads
- Three-Phase Power
- Three-Phase Analysis
- Per-Phase Analysis

Dr. Louie 2



Three-Phase Voltages

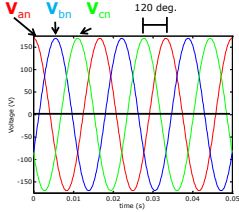


vector diagram

$$\mathbf{V}_{cn} = V_{cn} \angle 120^\circ$$

$$\mathbf{V}_{an} = V_{an} \angle 0^\circ$$


$$\mathbf{V}_{bn} = V_{bn} \angle -120^\circ$$

Dr. Louie 3




Three Phase

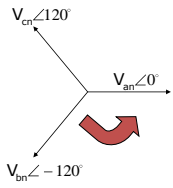- Power systems use 3-phase
- We are concerned with **balanced 3-phase**
- Balanced circuit conditions:
 - impedances are equal for each phase
 - voltage source phasors have equal magnitude and have a 120 deg. phase shift
 - a, b, c phase rotation




Dr. Louie 4



Benefits of Three-Phase Systems


- Efficient use of conductors over three, single phases
- Rotating field is needed for some loads (eg three phase motors)
- Effective for power transfer
- Per-phase analysis can be used in many cases
- Constant power delivery to three phase loads

Dr. Louie 5



Three Phase

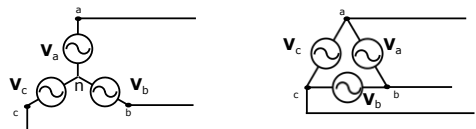Three phase generators connected as Y or Δ



Y (Wye) Delta

Dr. Louie 6

Three Phase Voltage

- Phase voltage:** the voltage across each source (V_a , V_b and V_c)
- Line voltage:** the voltage across the lines of the sources (also called "Line-to-Line Voltage")

Y Delta

Dr. Louie 7

Three Phase Voltage

For Y-connected sources:

Phase Voltages

$$\begin{aligned} V_{an} &= V_a \\ V_{bn} &= V_b \\ V_{cn} &= V_c \end{aligned}$$

Line Voltages

by KVL

$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} = V_{an}(\sqrt{3}\angle 30^\circ) \\ V_{bc} &= V_{bn} - V_{cn} = V_{bn}(\sqrt{3}\angle 30^\circ) \\ V_{ca} &= V_{cn} - V_{an} = V_{cn}(\sqrt{3}\angle 30^\circ) \end{aligned}$$

Dr. Louie 8

Three Phase Voltage

For Delta-connected sources:

Phase Voltages

$$\begin{aligned} V_{ab} &= V_a \\ V_{bc} &= V_b \\ V_{ca} &= V_c \end{aligned}$$

Line Voltages

$$\begin{aligned} V_{ab} &= V_a \\ V_{bc} &= V_b \\ V_{ca} &= V_c \end{aligned}$$

Do not confuse phase voltage with "per-phase voltage" as discussed later

Delta-connections: phase voltages = line voltages

Dr. Louie 9

Three Phase Voltage

Voltages (line or phase) sum to zero

$$\begin{aligned} V_a + V_b + V_c &= 0 \\ V_{an} + V_{bn} + V_{cn} &= 0 \\ V_{ab} + V_{bc} + V_{ca} &= 0 \end{aligned}$$

adding vectors results in 0

Dr. Louie 10

Three Phase Current

- Phase current:** current flowing through the voltage sources in a three-phase circuit
- Line current:** current flowing from a three-phase source to a load
- Each set of phase currents and sets of line currents are balanced:
 - Sum to zero
 - Equal in magnitude
 - Displaced by 120 degrees

Dr. Louie 11

Three Phase Current

Phase currents in Y-connected sources:

Vector Diagram

V_{an} is used as reference

Dr. Louie 12

Three Phase Current

Phase currents in Y-connected sources:

Y-connections: phase current = line current

Dr. Louie 13

Three Phase Current

Phase currents in Delta-connected sources:

Vector Diagram

V_{ab} is used as reference

Dr. Louie 14

Three Phase Current

Line currents in Delta-connected sources:

$$\begin{aligned} I_{12} &= I_{ba} - I_{ac} = I_{ba}(\sqrt{3}\angle -30^\circ) \\ I_{34} &= I_{cb} - I_{ba} = I_{cb}(\sqrt{3}\angle -30^\circ) \\ I_{56} &= I_{ac} - I_{cb} = I_{ac}(\sqrt{3}\angle -30^\circ) \end{aligned}$$

KCL at nodes a, b, c

Dr. Louie 15

Summary

Line Current = Phase Current	Line Current = Phase Current $\times \sqrt{3}\angle -30^\circ$
Line Voltage = Phase Voltage $\times \sqrt{3}\angle 30^\circ$	Line Voltage = Phase Voltage

Y (Wye)

Delta

Dr. Louie 16

Y-Δ Source Conversion

Each configuration has identical line-line voltages, line current, and complex power delivered to the load

Dr. Louie 17

Δ-Y Source Conversion

Each configuration has identical line-line voltages, line current, and complex power delivered to the load

"per-phase" voltage of a delta is the line-line voltage divided by sqrt(3)

Dr. Louie 18

Example

Convert the shown three-phase source to its Y equivalent given: $\mathbf{V}_a = 480\angle 0^\circ$

Dr. Louie 19

Example

Convert the shown three-phase source to its Y equivalent given: $\mathbf{V}_a = 480\angle 0^\circ$

Note: usually we redefine the reference Voltage to be \mathbf{V}_{an} so that $\mathbf{V}_{an} = 277\angle 0^\circ$

Dr. Louie 20

Three Phase Loads

- Three phase sources are connected to three phase loads in two common configurations
 - Y (wye)
 - Delta
- Y sources can be connected to delta and/or Y loads
- Delta sources can be connected to delta and/or Y loads

Dr. Louie 21

Three Phase Loads

- Circuit analysis is easier if loads are connected as Y
- We can transform balanced Delta connected loads into balanced Y connected loads mathematically by

$$\mathbf{Z}_y = \frac{\mathbf{Z}_\Delta}{3}$$
 - \mathbf{Z}_y : complex impedance of Y-connected load (Ohms)
 - \mathbf{Z}_Δ : complex impedance of a Delta-connected load (Ohms)
- Results only apply to terminal conditions

Dr. Louie 22

Conventions & Assumptions

- Voltage: line-to-line in rms
- Current: line in rms
- Current direction: source to load
- Balanced three phase

Dr. Louie 23

Three Phase Power

Total power delivered is the sum of power delivered by each phase

$$\begin{aligned} \mathbf{S}_{3\phi} &= \mathbf{V}_{an}\mathbf{I}_{na}^* + \mathbf{V}_{bn}\mathbf{I}_{nb}^* + \mathbf{V}_{cn}\mathbf{I}_{nc}^* \\ &= 3\mathbf{V}_{an}\mathbf{I}_{na}^* \quad (\text{due to symmetry}) \\ &= 3\mathbf{S} \end{aligned}$$

where

- $\mathbf{S}_{3\phi}$: total three phase complex power (VA)
- \mathbf{S} : single phase complex power (VA)

Dr. Louie 24

Three Phase Power

Similarly

$$P_{3\phi} = \text{Re}\{\mathbf{V}_{an}\mathbf{I}_{na}^*\} + \text{Re}\{\mathbf{V}_{bn}\mathbf{I}_{nb}^*\} + \text{Re}\{\mathbf{V}_{cn}\mathbf{I}_{nc}^*\}$$

$$= 3\text{Re}\{\mathbf{V}_{an}\mathbf{I}_{na}^*\}$$

$$= 3P$$

and

$$Q_{3\phi} = \text{Im}\{\mathbf{V}_{an}\mathbf{I}_{na}^*\} + \text{Im}\{\mathbf{V}_{bn}\mathbf{I}_{nb}^*\} + \text{Im}\{\mathbf{V}_{cn}\mathbf{I}_{nc}^*\}$$


$$= 3\text{Im}\{\mathbf{V}_{an}\mathbf{I}_{na}^*\}$$

$$= 3Q$$

Dr. Louie 25

Three-Phase Analysis

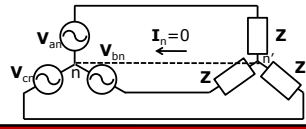- Recall that we can make a hypothetical connection between neutrals without affecting the circuit
 - Neutral Conductor
- For balanced sources and loads, no current flows on the neutral conductor



Dr. Louie 26

Three-Phase Analysis

- Phases can be conceptually decoupled
- No need to solve all three phases
 - Solve for a-phase (current or voltage)
 - Shift +120° for c-phase, and -120° for b-phase
- We can therefore do a per-phase analysis

Dr. Louie 27


Three-Phase Analysis

- Balanced Three-Phase Theorem
- Assume:
 - balanced three-phase system
 - all loads and sources are Y-connected (or convert them to Y-equivalent by dividing delta loads by 3 using per-phase voltage of delta sources)
 - no mutual inductances between phases
- then
 - all neutrals have the same voltage
 - the phases are completely decoupled
 - all corresponding network variables occur in balanced sets of the same sequence as the sources

Dr. Louie 28

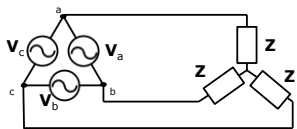Example


Consider the following circuit where the line-line voltage is 12.47kV, and the load impedance is 1200 + 300j Ω. Determine the total complex power consumed by the load.



Dr. Louie 29

Example

1. Verify that the circuit is balanced

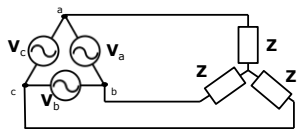

Dr. Louie 30

Example

2. Convert sources and loads to Y-connections

Dr. Louie 31

Example

2. Convert sources and loads to Y-connections

$$V_{an} = \frac{12.47k}{\sqrt{3}} = 7200\angle -30^\circ\text{V}$$

$$V_{bn} = \frac{12.47k}{\sqrt{3}} = 7200\angle -150^\circ\text{V}$$

$$V_{cn} = \frac{12.47k}{\sqrt{3}} = 7200\angle 90^\circ\text{V}$$

shift by +30 degrees for convenience

$$V_{an} = 7200\angle 0^\circ\text{V}$$

$$V_{bn} = 7200\angle -120^\circ\text{V}$$

$$V_{cn} = 7200\angle 120^\circ\text{V}$$

Dr. Louie 32

Example

3. Draw per-phase equivalent circuit

Dr. Louie 33

Example

- Virtual connection between n and n'

Dr. Louie 34

Example

4. Solve resulting circuit for single phase complex power and total complex power

Dr. Louie 35

Example

4. Solve resulting circuit for single phase complex power and total complex power

$$I = \frac{V_{an}}{Z} = 5.82\angle -14^\circ$$

$$S = V_{an}I = 40,654 + j10,163 \text{ VA}$$

$$S_{3\phi} = 3S = 121,960 + j30,490 \text{ VA}$$

alternatively

$$S = \frac{V_{an}^2}{1200} + j\frac{V_{an}^2}{300} = 40,654 + j10,163 \text{ VA}$$

$$S_{3\phi} = 3S = 121,960 + j30,490 \text{ VA}$$

Dr. Louie 36