

## 06-Applications

Text: Unit 4

ECEGR/ISSC 201  
Digital Operations and Computations  
Winter 2011



## Overview

- Conversion of English Statements to Boolean Expressions
- Conversion of Truth Tables
- Binary Adders and Subtracters

Dr. Louie

2



## Applications

- Interested in conversion of text statements to and from logical expressions
- Example  
*The light is to turn on if button A and button B are pushed or if button A is pushed and button B is not pushed or if button C is pushed.*

Dr. Louie

3



## Conversion of Text

1. Identify the logical phrases
2. Assign variables to each phrase
3. Write the logical expression

Dr. Louie

4



## Conversion of Text

- I will pass this course if I study hard and I do not have to work a full time job or if Professor Louie is an easy grader.

Dr. Louie

5




## Conversion of Text

- I will pass this course if I study hard and I do not have to work a full time job or if Professor Louie is an easy grader.

Dr. Louie


6



### Conversion of Text

- I will pass this course if I study hard and I do not have to work a full time job or if Professor Louie is an easy grader.
- Define variables
  - $P = 1$  if you pass the course
  - $A = 1$  if you study hard
  - $B = 1$  if you have to work full time
  - $C = 1$  if Prof. Louie is an easy grader


Dr. Louie 7



### Conversion of Text

- I will pass this course if I study hard and I do not have to work a full time job or if Professor Louie is an easy grader.
- Define variables
  - $P = 1$  if you pass the course
  - $A = 1$  if you study hard
  - $B = 1$  if you have to work full time
  - $C = 1$  if Prof. Louie is an easy grader
- $P = AB' + C$


Dr. Louie 8



### Conversion of Text

- Find the logical expression for:  
*The alarm will sound if and only if the alarm switch is on and the door is not closed or it is after 6pm and the window is not closed.*


Dr. Louie 9



### Example

1. Identify logical phrases  
*The alarm will sound if and only if the alarm switch is on and the door is not closed or it is after 6pm and the window is not closed.*


Dr. Louie 10



### Example

2. Assign variables  
*The alarm will sound if and only if the alarm switch is on and the door is not closed or it is after 6pm and the window is not closed.*  
 $Z$  = alarm will sound  
 $A$  = the alarm switch is on  
 $B'$  = the door is not closed  
 $C$  = it is after 6pm  
 $D'$  = the window is not closed

Dr. Louie 11



### Example


3. Write the logical expression  
*The alarm will sound if and only if the alarm switch is on and the door is not closed or it is after 6pm and the window is not closed.*  
 $Z$  = alarm will sound  
 $A$  = the alarm switch is on  
 $B'$  = the door is not closed  
 $C$  = it is after 6pm  
 $D'$  = the window is not closed  
 $Z = AB' + CD'$

Dr. Louie 12


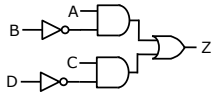
### Conversion of Text

- The logic can be implemented as:  
 $Z = AB' + CD'$



Dr. Louie

13



### Converting Truth Tables

- Assume you are given the following truth table to implement as a circuit:

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

14



### Converting Truth Tables

- First, find all the combinations that result in  $F = 1$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

15



### Converting Truth Tables

- $F = 1$  when  $A = 0$  and  $B = 1$  and  $C = 1$ , this can be expressed as  $A'BC$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

16



### Converting Truth Tables

- $F = 1$  when  $A = 1$  and  $B = 0$  and  $C = 0$ , this can be expressed as  $AB'C'$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

17



### Converting Truth Tables

- What can this row be expressed as?

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

18



### Converting Truth Tables

- What can this row be expressed as?  $F = 1$  when  $A = 1$  and  $B = 0$  and  $C = 1$ , this can be expressed as  $AB'C$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

19



### Converting Truth Tables

- What can this row be expressed as?

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

20



### Converting Truth Tables

- What can this row be expressed as?  $F = 1$  when  $A = 1$  and  $B = 1$  and  $C = 0$ , this can be expressed as  $ABC'$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

21



### Converting Truth Tables

- Finally:  $F = 1$  when  $A = 1$  and  $B = 1$  and  $C = 1$ , this can be expressed as  $ABC$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

22



### Converting Truth Tables

- $F = 1$  if  $A'BC$  or  $AB'C'$  or  $AB'C$  or  $ABC'$  or  $ABC$   
 $\Rightarrow F = A'BC + AB'C' + AB'C + ABC' + ABC$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0


Dr. Louie

23


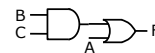
### Converting Truth Tables

- Next, simplify:
- $F = A'BC + AB'C' + AB'C + ABC' + ABC$   
 $= A'BC + AB'(C' + C) + AB(C' + C)$   
 $= A'BC + AB' + AB$   
 $= A'BC + A$   
 $= A + BC$



Dr. Louie

24



### Converting Truth Tables

- We could also do the same procedure by
  - Writing the terms that result in  $F = 0$
  - Writing terms in which  $F' = 1$  or  $F' = 0$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

25



### Converting Truth Tables

- Terms that result in  $F = 0$ 
  - $F = 0$  if  $A = 0, B = 0$  and  $C = 0$
  - $A + B + C = 0$  iff  $A = B = C = 0$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Dr. Louie

26



### Converting Truth Tables

- Terms that result in  $F = 0$ 
  - $F = 0$  if  $A = 0, B = 0$  and  $C = 0$
  - $F = 0$  if  $A = 0, B = 0$  and  $C = 1$
  - $F = 0$  if  $A = 0, B = 1$  and  $C = 0$
- Combining:  $(A+B+C)(A+B+C')(A+B'+C)$  will equal 0 iff any of the above combinations occur
- All other combinations result in  $F = 1$
- This must equal the previously derived expression:
- $(A+B+C)(A+B+C')(A+B'+C) = A + BC$

Dr. Louie

27



### Example

- Write a simplified expression for  $F$  in SoP form:

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Dr. Louie

28



### Example

- Write a simplified expression for  $F$  in SoP form:
- Identifying rows with  $F = 1$ 
  - $A'B'C'$
  - $A'B'C$
  - $AB'C'$
  - $ABC$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Dr. Louie

29




### Example

- Write a simplified expression for  $F$  in SoP form:
- $F = A'B'C' + A'B'C + AB'C' + ABC$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Dr. Louie

30




### Example

- Minimizing:
- $F = A'B'(C' + C) + AB'(C' + C)$
- $F = A'B' + AB' = B'(A + A') = B'$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Dr. Louie 31




### Example

- Write a simplified expression for F in PoS form

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Dr. Louie 32




### Example

- Write a simplified expression for F in PoS form

A	B	C	F	F'
0	0	0	1	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

Dr. Louie 33




### Example

- Write a simplified expression for F in PoS form
- $A + B' + C$
- $A + B' + C'$
- $A' + B' + C$
- $A' + B' + C'$

A	B	C	F	F'
0	0	0	1	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

Dr. Louie 34




### Example

$F = (A+B'+C)(A +B'+C')(A'+B'+C)(A'+B'+C')$

A	B	C	F	F'
0	0	0	1	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

Dr. Louie 35



### Example

$F = (A+B'+C)(A +B'+C')(A'+B'+C)(A'+B'+C')$   
 $F = (A+B'+C)(A +B'+C')(A'+B')$   
 $F = (A + B')(A'+B')$   
 $F = B'$

Dr. Louie 36



### Example

- The final answer in SoP or PoS form must give the same truth table
- Previous example is a special case in which the PoS and SoP forms are the same ( $B'$ )


Dr. Louie

37


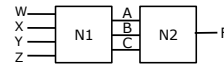
### Incompletely Specified Functions

- Complex circuits are often composed of subcircuits
- Assume that not all combinations of A, B and C are output by N1 (i.e., there is no combination of W, X, Y, Z that result in certain A, B, C combinations occurring)



Dr. Louie

38



### Incompletely Specified Functions

- Assume that the following ABC combinations do not occur:
  - 001
  - 110
- How do we design the circuit?

Dr. Louie

39



### Incompletely Specified Functions

- Truth table with unspecified values represented as "X"
- These are "don't care" terms

A	B	C	F
0	0	0	1
0	0	1	X
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	1

Dr. Louie

40



### Incompletely Specified Functions

- Don't cares need to be specified as either a 1 or 0
- We should assign a value that reduces the complexity of the circuit
- Try each of the four combinations

Dr. Louie

41



### Incompletely Specified Functions

- With 0 assigned to the don't cares:
  - $F = A'B'C' + A'BC + ABC = A'B'C' + BC$

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Dr. Louie

42



### Incompletely Specified Functions

- With 1 to the first, 0 to the second don't care
  - $F = A'B'C' + A'B'C + A'BC + ABC = A'B' + BC$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Dr. Louie

43



### Incompletely Specified Functions

- With 0 to the first, 1 to the second don't care
  - $F = A'B'C' + A'BC + ABC' + ABC = A'B'C' + A'BC + AB$

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Dr. Louie

44



### Incompletely Specified Functions

- With 1 to assigned to both don't cares
  - $F = A'B'C' + A'B'C + A'BC + ABC' + ABC = A'B' + BC + AB$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Dr. Louie

45



### Incompletely Specified Functions

- Which is the simplest?
  - $F = A'B'C' + BC$
  - $F = A'B' + BC$
  - $F = A'B'C' + A'BC + AB$
  - $F = A'B' + BC + AB$
- Second choice (first  $X = 1$ , second  $X = 0$ )

Dr. Louie

46



### Truth Table Examples

- Design a binary adder for two, 1-bit numbers
  - A two bit output is needed

Dr. Louie

47



### Truth Table Example

- Design a binary adder for two, 1-bit numbers
- Let  $a$ ,  $b$  be the numbers to be added
- A table for the input/output combinations is:

a	b	Sum
0	0	00
0	1	01
1	0	01
1	1	10

Dr. Louie

48



### Truth Table Example

- This can easily be converted into a truth table:

a	b	Sum
0	0	00
0	1	01
1	0	01
1	1	10

A	B	X	Y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

first digit      second digit

Dr. Louie 49

### Truth Table Example

- Write the expressions for X and Y

A	B	X	Y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Dr. Louie 50

### Truth Table Example

- Write the expressions for X and Y
  - $X = AB$
  - $Y = A'B + AB' = A \oplus B$
- This is simple, which is why we use 2's complement addition

A	B	X	Y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Dr. Louie 51

### Binary Adders and Subtracters

- Goal: design an adder that adds two 4-bit unsigned binary numbers
- Output: 4 bit output and a carry
- One approach: develop a truth table (of what dimension?) and determine the expression
  - Complicated
- Our approach: modularize--design a module that adds two bits and a carry, connect four together

Dr. Louie 52

### Binary Adders and Subtracters

- $A_x$ : bit of first number
- $B_x$ : bit of second number
- $C_x$ : carry output
- $S_x$ : sum output

C<sub>4</sub>    S<sub>3</sub>    S<sub>2</sub>    S<sub>1</sub>    S<sub>0</sub>

Adder    Adder    Adder    Adder

A<sub>3</sub>B<sub>3</sub>    A<sub>2</sub>B<sub>2</sub>    A<sub>1</sub>B<sub>1</sub>    A<sub>0</sub>B<sub>0</sub>

If adding 1's complement numbers, otherwise ignore C<sub>0</sub> and discard C<sub>4</sub>

Dr. Louie 53

### Binary Adders and Subtracters

- Example 2's complement addition
  - A = 1011 => A<sub>0</sub> = 1; A<sub>1</sub> = 1; A<sub>2</sub> = 0; A<sub>3</sub> = 1
  - B = 1110 => B<sub>0</sub> = 0; B<sub>1</sub> = 1; B<sub>2</sub> = 1; B<sub>3</sub> = 1

C<sub>4</sub>    S<sub>3</sub>    S<sub>2</sub>    S<sub>1</sub>    S<sub>0</sub>

Adder    Adder    Adder    Adder

A<sub>3</sub>B<sub>3</sub>    A<sub>2</sub>B<sub>2</sub>    A<sub>1</sub>B<sub>1</sub>    A<sub>0</sub>B<sub>0</sub>

Dr. Louie 54

**Binary Adders and Subtractors**

- Example
  - $A_0 + B_0 = 1 + 0 \Rightarrow S_0 = 1; C_1 = 0$

A = 1011; B = 1110

Dr. Louie 55

**Binary Adders and Subtractors**

- Example
  - $A_0 + B_0 = 1 + 0 \Rightarrow S_0 = 1; C_1 = 0$
  - $C_1 + A_1 + B_1 = 0 + 1 + 1 \Rightarrow S_1 = 0; C_2 = 1$

A = 1011; B = 1110

Dr. Louie 56

**Binary Adders and Subtractors**

- Example
  - $A_0 + B_0 = 1 + 0 \Rightarrow S_0 = 1; C_1 = 0$
  - $C_1 + A_1 + B_1 = 0 + 1 + 1 \Rightarrow S_1 = 0; C_2 = 1$
  - $C_2 + A_2 + B_2 = 1 + 0 + 1 \Rightarrow S_2 = 0; C_3 = 1$

A = 1011; B = 1110

Dr. Louie 57

**Binary Adders and Subtractors**

- Example
  - $A_0 + B_0 = 1 + 0 \Rightarrow S_0 = 1; C_1 = 0$
  - $C_1 + A_1 + B_1 = 0 + 1 + 1 \Rightarrow S_1 = 0; C_2 = 1$
  - $C_2 + A_2 + B_2 = 1 + 0 + 1 \Rightarrow S_2 = 0; C_3 = 1$
  - $C_3 + A_3 + B_3 = 1 + 1 + 1 \Rightarrow S_3 = 1; C_4 = 1$

A = 1011; B = 1110

Dr. Louie 58

**Binary Adders and Subtractors**

- Did the counter operate properly?
- The decimal equivalent of the 2s complement numbers:  $N^* = 2^n - N$ 
  - $A = 1011 \Rightarrow 11 = 16 - N \Rightarrow N = 5 \Rightarrow A = -5$
  - $B = 1110 = -2$
- $A + B = -7 \Rightarrow 1001$
- Our solution is (ignoring the final carry over)
  - $S_3S_2S_1S_0 = 1001$
- Success!

Dr. Louie 59

**Binary Adders and Subtractors**

- Need to determine the expressions for  $S_x$  and  $C_x$
- We can build a truth table from the various cases of  $A_x, B_x,$  and  $C_x$  values
- Consider the generic adder

Dr. Louie 60

### Binary Adders and Subtractors

X	Y	C <sub>in</sub>	C <sub>out</sub>	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Dr. Louie 61

### Binary Adders and Subtractors

- The resulting expression is:
  - Sum =  $X'YC_{IN} + X'YC'_{IN} + XYC'_{IN} + XYC_{IN}$
  - Sum =  $X'(Y'C_{IN} + YC'_{IN}) + X(Y'C_{IN} + YC_{IN})$
  - Sum =  $X'(Y \oplus C_{IN}) + X(Y \oplus C_{IN})'$
  - Sum =  $X \oplus Y \oplus C_{IN}$

Dr. Louie 62

### Binary Adders and Subtractors

- The resulting expression is:
  - $C_{OUT} = X'YC_{IN} + XY'C_{IN} + XYC'_{IN} + XYC_{IN}$
  - $C_{OUT} = X'YC_{IN} + XY'C_{IN} + XYC'_{IN} + XYC_{IN}$  add three more times to simplify
  - $C_{OUT} = (X'YC_{IN} + XYC_{IN}) + (XY'C_{IN} + XYC'_{IN}) + (XYC'_{IN} + XYC_{IN})$
  - $C_{OUT} = (YC_{IN}) + (XC_{IN}) + (XY)$

Dr. Louie 63

### Binary Adders and Subtractors

- When working with numbers in 1's or 2's complement form, errors due to overflow can be detected by checking if
  - two positive numbers result in a negative number
  - two negative numbers result in a positive number
- Recall: an overflow error occurs when in an n-bit system, the correct display of the answer requires more than n bits

Dr. Louie 64

### Binary Adders and Subtractors

- Find an expression for V, which is equal to 1 when an overflow error occurs

Dr. Louie 65

### Binary Adders and Subtractors


- Find an expression for V, which is equal to 1 when an overflow error occurs
  - $V = A_3'B_3'S_3 + A_3B_3S_3'$

Dr. Louie 66


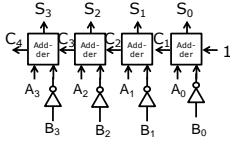
## Binary Adders and Subtractors

- Subtracting numbers is easily done by adding the 1's or 2's complement of the number to be subtracted
- Example:  $A - B$ 
  - Recall a 2's complement can be found by complementing each bit and adding 1



Dr. Louie

67



## Binary Adders and Subtractors

- A subtractor circuit can also be designed
- Borrow and difference outputs for each column

X	Y	b	$b_{i+1}$	$d_i$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Dr. Louie

68