


## 06-Basic Laws Part 3

Text: Chapter 2.5-2.8


ECEGR 210  
Electric Circuits I



### Overview


- Voltage Drop
- Voltage Divider
- Series Resistors
- Current Divider
- Parallel Resistors
- Delta-Wye Conversion

2



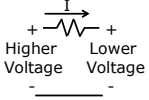
### Voltage Drop

- The voltage difference across the terminals of a resistor is called the "voltage drop"
  - If the current is negative, then it is a voltage rise
- Voltage drop is caused by the current flowing through the resistor and by Ohm's Law is equal to  $I \times R$




Dr. Louie 3



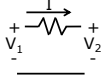
### Voltage Drop

- The current through a resistor can be quickly found by:
 
$$I = \frac{V_1 - V_2}{R}$$



  - Where  $V_1$  and  $V_2$  are referenced to the same node, and  $V_1 > V_2$

Dr. Louie 4




### Voltage Drop


- For example, the current through the resistor can be computed as:
 
$$0 = -V_1 + V_R + V_2$$

$$0 = -V_1 + IR + V_2$$
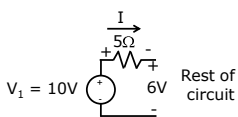
$$I = \frac{V_1 - V_2}{R} = \frac{4}{5} = 0.8A$$




Dr. Louie 5


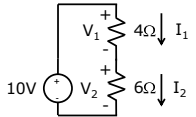
### Multi-Resistor Circuits

- Now back to multi-resistor circuits
- What is the voltage across each resistor?
  - KVL:  $10 = V_1 + V_2$
  - KCL:  $I_1 = I_2$
  - Ohm's Law:
    - $V_1 = 4I_1$
    - $V_2 = 6I_2$



Dr. Louie 6


### Multi-Resistor Circuits

- Using
  - $10 = V_1 + V_2$
  - $I_1 = I_2 = I$
  - $V_1 = 4I_1$
  - $V_2 = 6I_2$
- Gives
 
$$10 = 4I + 6I$$

$$I = \frac{10}{4+6}$$

$$V_1 = 10 \cdot \frac{4}{4+6} = 4V$$


$$V_2 = 10 \cdot \frac{6}{4+6} = 6V$$

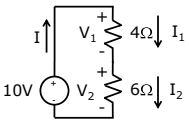

Dr. Louie 7
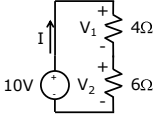
### Multi-Resistor Circuits

- From this simple example, note:
  - Resistors are in series
  - Proportion of applied voltage across a resistor, is the same proportion of the resistor to the total resistance
  - $R_1$ : 40% of total resistance and 40% of the voltage ( $V_1 = 4V$ )
  - $R_2$ : 60% of total resistance and 60% of the voltage ( $V_2 = 6V$ )



Dr. Louie 8

### Voltage Divider


- The voltage across each resistor is
 
$$V_1 = \frac{R_1}{R_1 + R_2} V$$

$$V_2 = \frac{R_2}{R_1 + R_2} V$$
- More generally, the voltage across the nth resistor of N resistors in series is:
 
$$V_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} V$$

Dr. Louie 9

### Example

- Find  $V_1, V_2, V_3$

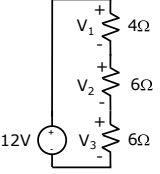

Dr. Louie 10


### Example

- Find  $V_1, V_2, V_3$ 

$$V_1 = 12 \cdot \frac{4}{4+6+6} = 3V$$

$$V_2 = 12 \cdot \frac{6}{16} = 4.5V$$


$$V_3 = 12 \cdot \frac{6}{16} = 4.5V$$

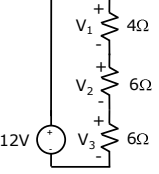

Dr. Louie 11
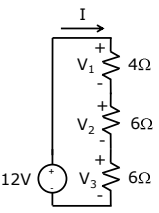
### Series Resistances

- What is the current?
  - $V_1 = 3V = 4I$ 
    - $I = 0.75A$
  - $V_2 = 4.5V = 6I$ 
    - $I = 0.75A$
  - $V_3 = 4.5V = 6I$ 
    - $I = 0.75A$



Dr. Louie 12

**Series Resistances**

- Find an equivalent circuit with one resistor ( $R_{eq}$ ) so that the same current flows

Dr. Louie 13

**Series Resistances**

- By Ohm's Law:  $12 = 0.75R_{eq}$ 
  - $R_{eq} = 16\Omega$
- Note  $R_{eq} = 4 + 6 + 6 = 16\Omega$

Dr. Louie 14

**Series Resistances**

- More generally: the equivalent resistance ( $R_{eq}$ ) of any number ( $N$ ) of resistors in series is the sum of the individual resistances ( $R_n$ )

$$R_{eq} = \sum_{n=1}^N R_n$$

Dr. Louie 15

**Series Resistances**

- Consider a 100 m wire whose resistivity is 1 Ohm per 25m.
- We can model this in many ways
- For example:

Dr. Louie 16

**Series Resistances**

- The equivalent resistance of series connected resistors is the sum of their resistances

Dr. Louie 17

**Example**

- Compute the equivalent resistance between the terminals of the following circuits

Dr. Louie 18

**Example**

- Compute the equivalent resistance between the terminals of the following circuits

Dr. Louie 19

**Series Resistance**

- When adding resistances in series the overall resistance increases
- Less current flows than if there is only one resistance

Dr. Louie 20

**Example**

- Find the voltage across each resistor, and the power supplied by the voltage source.

Dr. Louie 21

**Example**

- Find the voltage across each resistor, and the power supplied by the voltage source.

$$V_1 = 8 \frac{3}{9} = 5.33V$$

$$V_2 = 8 \frac{6}{9} = 2.67V$$

Dr. Louie 22

**Example**

- Find the voltage across each resistor, and the power supplied by the voltage source.

$$P_s = \frac{V_1^2}{R_1} + \frac{V_2^2}{R_2} = 7.12W$$

or

$$I_s = \frac{8}{9} = 0.89A$$

$$P_s = V_s I = 7.12W$$

Dr. Louie 23

**Example**

- The voltmeter reads 2V. What is  $R_2$ ?

Dr. Louie 24

**Example**

- The voltmeter reads 2V. What is  $R_2$ ?


$$V = 2$$

$$2 = 12 \frac{R_2}{10 + R_2}$$

$$10 + R_2 = 6R_2$$

$$R_2 = 2\Omega$$


or by inspection

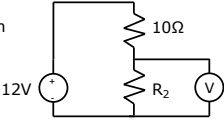

Dr. Louie 25

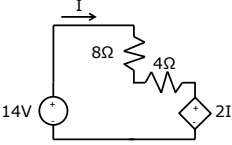**Example**

- Find  $I$ , and the voltage across the dependent voltage source.




Dr. Louie 26

**Example**

- First find  $I$ , then the voltage across the independent source  $V_d$


$$14 = 12I + V_d = 14I$$


$$I = 1A$$
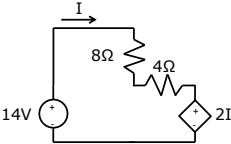
$$V_d = 2V$$


Dr. Louie 27

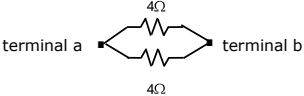**Parallel Resistance**


- Assume two  $4\Omega$  wires are connected as terminal a  terminal b
- What is the circuit model of this?



Dr. Louie 28

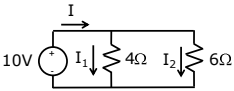**Current Divider**


- Find the fraction of  $I$  that flows through each resistor



Dr. Louie 29

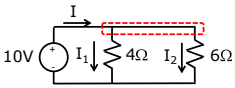**Current Divider**

- By KCL
  - $I = I_1 + I_2$
- By KVL
  - $10 = V_1 = V_2$
- By Ohm's Law
  - $V_1 = 4I_1$
  - $V_2 = 6I_2$



Dr. Louie 30

### Current Divider

- Combining
  - $I = I_1 + I_2$
  - $10 = V_1 = V_2$
  - $V_1 = 4I_1$
  - $V_2 = 6I_2$
- Yields
  - $I_2 = I_1 \frac{4}{6}$
  - $I = I_1 + \frac{4}{6}I_1 = I_1 \frac{6+4}{6}$
  - $I_1 = \frac{6}{6+4}I$
  - $I_2 = \frac{4}{6+4}I$

Describes how current divides

Dr. Louie 31

### Current Divider

- Note:
  - $I_1 = \frac{6}{6+4}I = \frac{R_2}{R_1+R_2}I = 0.6I$
  - $I_2 = \frac{4}{6+4}I = \frac{R_1}{R_1+R_2}I = 0.4I$
- If we divide the numerators and denominators by  $R_1R_2$ , then:
  - $I_1 = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}}I = \frac{G_2}{G_1+G_2}I$
  - $I_2 = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}}I = \frac{G_1}{G_1+G_2}I$

Dr. Louie 32


### Current Divider

- From this simple example:
  - Resistors are in parallel
  - Greater current flows through the resistor with lower resistance
  - Proportion of current through a resistor is proportional to the conductance of that resistor to the total conductance
    - 60 percent of total through the 4 Ohm resistor
    - 40 percent of total through 6 Ohm resistor

Dr. Louie 33
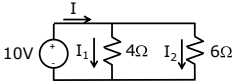
### Parallel Resistance


- We now know how the current divides, but how much current flows?
  - $I = I_1 + I_2$
  - $I = 10 \frac{1}{R_1} + 10 \frac{1}{R_2} = 10 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = 4.17A$
  - Therefore
    - $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = G_1 + G_2 = 2.4\Omega$  (sum of conductances)



Dr. Louie 34
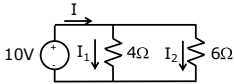
### Parallel Resistance

- Note:
  - $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1R_2}{R_1+R_2}$
- The equivalent resistance of two parallel resistors is their product divided by their sum



Dr. Louie 35

### Current Divider

- The equivalent resistance of N resistors in parallel is
  - $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} = G_1 + G_2 + \dots + G_N = G_{eq}$
- The current through the nth resistor of N resistors in parallel is:
  - $I_n = \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}I$
  - $= \frac{G_n}{G_1 + G_2 + \dots + G_N}I$

Dr. Louie 36



## Parallel Resistance

- When adding resistances in parallel the equivalent resistance decreases
  - Resistance always be less than the smallest individual resistance
- More total current flows
- Symbol "||" is used in an equation to designate a parallel relationship between elements
- Example:  $R_1 || R_2$

Dr. Louie

37



## Current Divider

- The equivalent resistance is always smaller than the smallest individual resistance
- Example: a 100 Ohm, 10 Ohm and 1 Ohm resistors are placed in parallel. What is the equivalent resistance?

Dr. Louie

38



## Current Divider

- The equivalent resistance is always smaller than the smallest individual resistance
- Example: a 100 Ohm, 10 Ohm and 1 Ohm resistors are placed in parallel. What is the equivalent resistance?

$$\frac{1}{R_{eq}} = 0.01 + 0.1 + 1$$

$$R_{eq} = 0.901\Omega$$


Dr. Louie

39


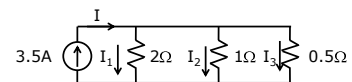
## Example

- Find the current through each resistor, and the power supplied by the current source



Dr. Louie

40




## Example

- Find the current through each resistor, and the power supplied by the current source

$$I_1 = \frac{\frac{1/2}{1/2 + 1/1 + 1/0.5}}{I} = \frac{0.5}{0.5 + 1 + 2} 3.5 = 0.5A$$

$$I_2 = \frac{1/1}{3.5} I = 1A$$

$$I_3 = \frac{1/0.5}{3.5} I = 2A$$

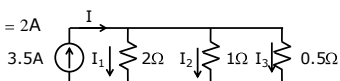

Dr. Louie

41



## Example

- Find the current through each resistor, and the power supplied by the current source


$$V = I_1 R_1 = 0.5 \times 2 = 1$$

$$P = IV = 3.5W$$

or

$$R_{eq} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{0.5 + 1 + 2} = 0.286\Omega$$

$$P = I^2 R_{eq} = 3.5W$$

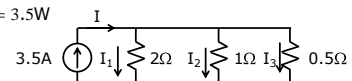

Dr. Louie

42

### Parallel Circuits

- It may be easier to combine parallel resistors two at a time (easy to compute product-over-sum)
- Example:

$$\frac{1 \times 0.5}{1 + 1.5} = 0.33\Omega$$

$$\frac{2 \times 0.33}{2 + 0.33} = 0.286\Omega$$

Dr. Louie 43

### Delta-Wye Circuits

- It is possible for elements to be arranged such that they are not in series or parallel
- Examples

Tee connection Pi connection

Dr. Louie 44

### Delta-Wye Circuits

- Often interested in converting a Delta (Π) to a Wye (Tee) or vice versa
- Interested in terminal characteristics
  - Convert from Delta to Wye (or vice versa) so that same resistance is seen from terminals (1,2) and (3,4)

Wye connection Delta connection

Dr. Louie 45

### Delta-Wye Circuits

- Resistance between terminals 1,2 in Wye is:
  - $R_{12} = R_1 + R_3$
- In Delta it is:
  - $R_{12} = R_b || (R_a + R_c)$

Wye connection Delta connection

Dr. Louie 46

### Delta-Wye Circuits

- Setting them equal and solving...
  - $R_b || (R_a + R_c) = R_1 + R_3$
- Repeating for terminals 1,3 and 3,4 gives
  - $R_c || (R_c + R_b) = R_1 + R_2$
  - $R_a || (R_c + R_b) = R_2 + R_3$

Wye connection Delta connection

Dr. Louie 47

### Delta-Wye Circuits

- Solving  $R_1, R_2$  and  $R_3$  in terms of  $R_a, R_b, R_c$  by combining equations
 
$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Wye connection Delta connection

Product of adjacent divided by sum of resistors (see Fig. 2.49)

Dr. Louie 48






### Delta-Wye Circuits

- Solving  $R_a$ ,  $R_b$  and  $R_c$  in terms of  $R_1$ ,  $R_2$ ,  $R_3$  by combining equations


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
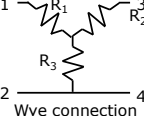
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$




Wye connection

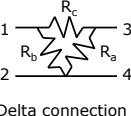

Delta connection

Sum of products of all combinations of resistors taken two at a time divided by the opposite Wye resistor (see Fig. 2.49)

Dr. Louie
49



### Delta-Wye Circuits

- How are the equations reduced when  $R_1 = R_2 = R_3$  or  $R_a = R_b = R_c$ ?
  - $R_Y = \frac{R_\Delta}{3}$
  - $R_\Delta = 3R_Y$
- This occurs in balanced three phase networks

Dr. Louie
50