

06-Three Phase Analysis

ECEGR 450
Electromechanical Energy Conversion



Overview

- Three Phase Power
- Three Phase Analysis
- Per Phase Analysis
- Practical Considerations

Dr. Louise

2



Questions

- How does three phase power compare to single phase power?
- What is the "neutral" connection in a three phase system?

Dr. Louise

3



Conventions & Assumptions

- Voltage: line-to-line in rms
- Current: line in rms
- Current direction: source to load
- Balanced three phase

Dr. Louise

4



Three Phase Power

Benefits of three phase power:

- efficient use of conductors over three, single phases
- rotating field is needed for some loads (eg three phase motors)
- effective for power transfer
- per-phase analysis can be used in many cases
- Constant power delivery to three phase loads

Dr. Louise

5



Three Phase Power

- Total power delivered is the sum of power delivered by each phase

$$\begin{aligned} \mathbf{S}_{3\phi} &= \mathbf{V}_{an} \mathbf{I}_{na}^* + \mathbf{V}_{bn} \mathbf{I}_{nb}^* + \mathbf{V}_{cn} \mathbf{I}_{nc}^* \\ &= 3\mathbf{V}_{an} \mathbf{I}_{na}^* \quad (\text{due to symmetry}) \\ &= 3\mathbf{S} \end{aligned}$$

- where
 - $\mathbf{S}_{3\phi}$: total three phase complex power (VA)
 - \mathbf{S} : single phase complex power (VA)

Dr. Louise

6

Three Phase Power

Similarly

$$P_{3\phi} = \operatorname{Re}\{\mathbf{V}_{an}\mathbf{I}_{na}^*\} + \operatorname{Re}\{\mathbf{V}_{bn}\mathbf{I}_{nb}^*\} + \operatorname{Re}\{\mathbf{V}_{cn}\mathbf{I}_{nc}^*\}$$

$$= 3\operatorname{Re}\{\mathbf{V}_{an}\mathbf{I}_{na}^*\}$$

$$= 3P$$

and

$$Q_{3\phi} = \operatorname{Im}\{\mathbf{V}_{an}\mathbf{I}_{na}^*\} + \operatorname{Im}\{\mathbf{V}_{bn}\mathbf{I}_{nb}^*\} + \operatorname{Im}\{\mathbf{V}_{cn}\mathbf{I}_{nc}^*\}$$

$$= 3\operatorname{Im}\{\mathbf{V}_{an}\mathbf{I}_{na}^*\}$$

$$= 3Q$$

Dr. Louie 7

Three Phase Power

What about instantaneous power?

$$p_{ip}(t) = i_{\max} v_{\max} \cos(\omega t + 0) \cos(\omega t + \theta_a) +$$

$$i_{\max} v_{\max} \cos(\omega t - 120^\circ) \cos(\omega t + \theta_a - 120^\circ) +$$

$$i_{\max} v_{\max} \cos(\omega t + 120^\circ) \cos(\omega t + \theta_a + 120^\circ)$$

$$p_{ip}(t) = \frac{1}{2} v_{\max} i_{\max} [\cos(-\theta_a) + \cos(2\omega t + \theta) +$$

$$\cos(-\theta_a) + \cos(2\omega t + \theta - 120^\circ) +$$

$$\cos(-\theta_a) + \cos(2\omega t + \theta + 120^\circ)]$$

Next use: $\cos(x + y) = \cos x \cos y - \sin x \sin y$

Dr. Louie 8

Three Phase Power

$$p_{ip}(t) = \frac{1}{2} v_{\max} i_{\max} [3 \cos(-\theta_a) + \cos(2\omega t + \theta) +$$

$$\cos(2\omega t + \theta) \cos(-120^\circ) - \sin(2\omega t + \theta) \sin(-120^\circ)$$

$$\cos(2\omega t + \theta) \cos(120^\circ) - \sin(2\omega t + \theta) \sin(120^\circ)]$$



$$p_{ip}(t) = \frac{1}{2} v_{\max} i_{\max} [3 \cos(-\theta_a) + \cos(2\omega t + \theta) +$$

$$\frac{-1}{2} \cos(2\omega t + \theta) - \frac{\sqrt{3}}{2} \sin(2\omega t + \theta)$$

$$\frac{-1}{2} \cos(2\omega t + \theta) - \frac{\sqrt{3}}{2} \sin(2\omega t + \theta)]$$

$$p_{ip}(t) = \frac{3}{2} v_{\max} i_{\max} \cos(\phi) \quad \text{What does this say about the real power?}$$

Dr. Louie 9

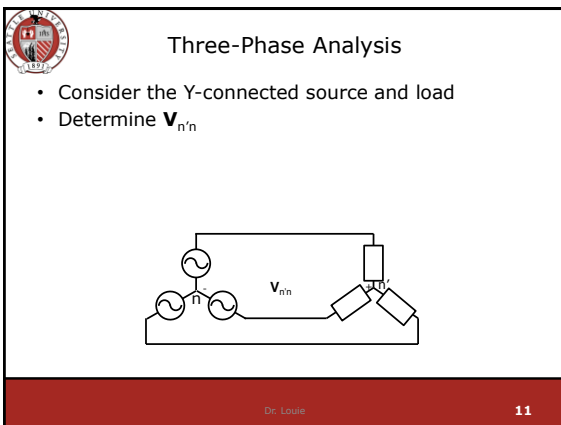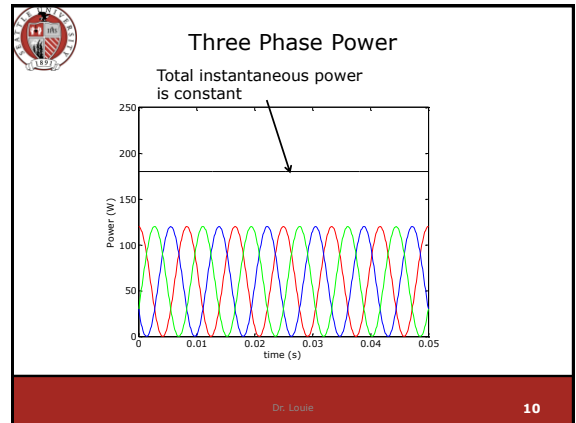

Three-Phase Analysis

- Analysis is easier using admittance, \mathbf{Y}

$$\mathbf{Y} = \frac{1}{\mathbf{Z}}$$

- Line current is equal to phase current

$$\left. \begin{aligned} \mathbf{I}_{na} &= \mathbf{Y}(\mathbf{V}_{an} - \mathbf{V}_{n'n}) \\ \mathbf{I}_{nb} &= \mathbf{Y}(\mathbf{V}_{bn} - \mathbf{V}_{n'n}) \\ \mathbf{I}_{nc} &= \mathbf{Y}(\mathbf{V}_{cn} - \mathbf{V}_{n'n}) \end{aligned} \right\} \text{due to wye connection}$$

Dr. Louie 12

Three-Phase Analysis

- Summing the line current

$$\mathbf{I}_{na} + \mathbf{I}_{nb} + \mathbf{I}_{nc} = \mathbf{Y}(\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn}) - 3\mathbf{Y}\mathbf{V}_{nn'}$$

- Previously we showed that

$$\mathbf{I}_{na} + \mathbf{I}_{nb} + \mathbf{I}_{nc} = 0$$

$$\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$$

- Therefore

$$0 = \mathbf{Y}(0) - 3\mathbf{Y}\mathbf{V}_{nn'}$$

$$\Rightarrow \mathbf{V}_{nn'} = 0$$

Dr. Louie 13

Three-Phase Analysis

- Since $\mathbf{V}_{nn'} = 0$, we can make a hypothetical connection without affecting the circuit
- Called the Neutral Conductor
- For balanced sources and loads, no current flows on the neutral conductor

Dr. Louie 14

Three-Phase Analysis

Let's now analyze the current through the a-phase load

$$\mathbf{V}_{an} = \mathbf{V}_{an'}$$

$$\mathbf{I}_{na} = \frac{\mathbf{V}_{an'}}{\mathbf{Z}}$$

Dr. Louie 15

Three-Phase Analysis

Let's now analyze the current through the b-phase load

$$\mathbf{V}_{bn} = \mathbf{V}_{bn'}$$

$$\mathbf{I}_{nb} = \frac{\mathbf{V}_{bn'}}{\mathbf{Z}}$$

But

$$\mathbf{V}_{bn} = \mathbf{V}_{an}(1\angle -120^\circ)$$

$$\mathbf{I}_{nb} = \frac{\mathbf{V}_{bn'}}{\mathbf{Z}} = \frac{\mathbf{V}_{an}(1\angle -120^\circ)}{\mathbf{Z}} = \mathbf{I}_{na}(1\angle -120^\circ) \text{ (b-phase current in terms of a-phase current)}$$

Dr. Louie 16

Three-Phase Analysis

- Let's now analyze the current through the c-phase load

$$\mathbf{V}_{cn} = \mathbf{V}_{cn'}$$

$$\mathbf{I}_{nc} = \frac{\mathbf{V}_{cn'}}{\mathbf{Z}}$$

- But

$$\mathbf{V}_{cn} = \mathbf{V}_{an}(1\angle 120^\circ)$$


$$\mathbf{I}_{nc} = \frac{\mathbf{V}_{cn'}}{\mathbf{Z}} = \frac{\mathbf{V}_{an}(1\angle 120^\circ)}{\mathbf{Z}} = \mathbf{I}_{na}(1\angle 120^\circ) \text{ (c-phase current in terms of a-phase current)}$$

Dr. Louie 17

Three-Phase Analysis

- Once \mathbf{I}_{na} is solved for, simply shift it by $-/+120$ degrees to find \mathbf{I}_{nb} and \mathbf{I}_{nc}
- Phases can be conceptually decoupled
- No need to solve all three phases
 - Solve for a-phase (current or voltage)
 - Shift $+120^\circ$ for c-phase, and -120° for b-phase
- We can therefore do a per-phase analysis

Dr. Louie 18




Three-Phase Analysis

- **Balanced Three-Phase Theorem**
- **Assume:**
 - balanced three-phase system
 - all loads and sources are Y-connected (or convert them to Y-connected loads/sources)
 - no mutual inductances between phases

then


- all neutrals have the same voltage
- the phases are completely decoupled
- all corresponding network variables occur in balanced sets of the same sequence as the sources

Dr. Louie 19




Per-Phase Analysis

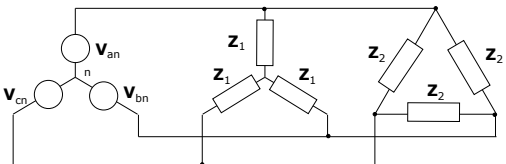- Consider the following circuit
- Is it balanced?




Dr. Louie 20




Per-Phase Analysis

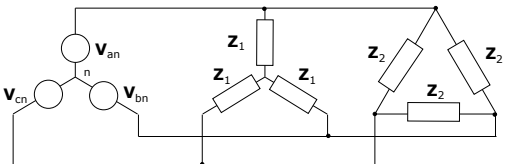- To analyze this circuit, we first need to find a per-phase equivalent
- Need to transform the delta load to Y load




Dr. Louie 21




Per-Phase Analysis

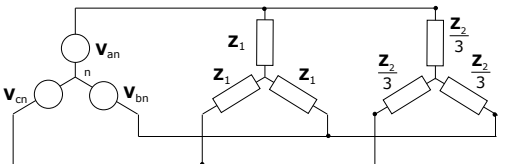- To analyze this circuit, we first need to find a per-phase equivalent
- Need to transform Delta load to Y load




Dr. Louie 22




Per-Phase Analysis

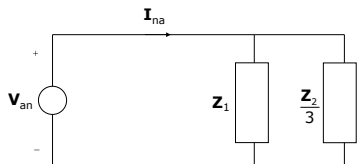
- Analyze a single phase (arbitrarily a-phase)
- Analyze this phase to find the current, power, etc



Dr. Louie 23



Numerical Example

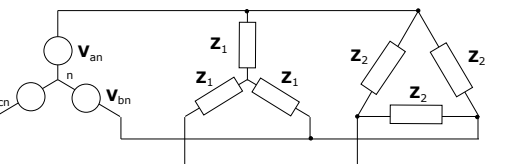

given:
 balanced 3-phase source
 $V_{an} = 120 \angle 0^\circ \text{ V}$
 $Z_1 = 10 + j2 \ \Omega$
 $Z_2 = 12 \angle 45^\circ \ \Omega$

find:
 I_{na}, I_{nb}, I_{nc}
 total power delivered to the loads

Dr. Louie 24

Example

- Solution outline
 - draw per-phase equivalent
 - solve circuit for current
 - compute single phase power
 - translate per-phase values to 3-phase

Dr. Louie 25

Example

- Convert Δ to Y $Z_2 = 2.82 + j2.82 \Omega$
- Redraw circuit

Dr. Louie 26

Example

- Redraw circuit $Z_2 = 2.82 + j2.82 \Omega$
- Draw per-phase equivalent

Dr. Louie 27

Example

- Draw per-phase equivalent
- Solve for I_{na} and S
 - $V_{an} = 120 \angle 0^\circ \text{ V}$
 - $I_{na} = 40.32 \angle -35^\circ \text{ A}$
 - $S = 3930.2 + j2822.5 \text{ VA}$

Dr. Louie 28

Example

- Shifting and solving
 - $I_{nb} = 40.32 \angle -35^\circ - 120^\circ = 40.32 \angle -155^\circ \text{ A}$
 - $I_{nc} = 40.32 \angle -35^\circ + 120^\circ = 40.32 \angle 85^\circ \text{ A}$
 - $I_n = 0 \text{ A}$
 - $S_{3\phi} = 3 \cdot 3930.19 + j2822.51 = 11790.57 + j8467.53 \text{ VA}$

Dr. Louie 29

Practical Considerations

Three phase systems and components often referred to by RMS line-line voltages e.g. 500kV, 13.6kV, 480V

Three phase systems and components often referred to by $|S_{3\phi}|$ e.g. 100 MVA transformer

Dr. Louie 30



Practical Considerations


- Neutral usually bonded to ground at service panel (see NEC for details)
- Balanced load assumption can be questionable
 - Neutral current nonzero
 - Neutral not at ground potential

Dr. Louie

31



Practical Considerations

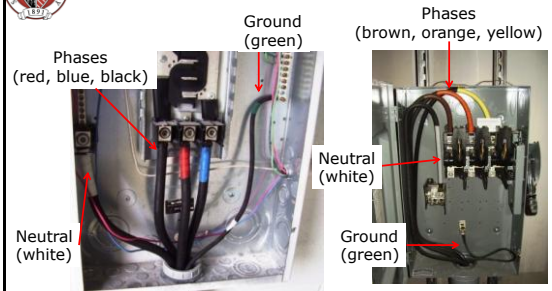Source: www.electrical-design-tutor.com/

Dr. Louie

32



Summary

- Current (voltages) sum to zero and no current flows on neutral conductor
- Total S , P , Q = three times single phase S , P , Q
- Three phase systems analysis: convert into wye connections, solve per-phase

Dr. Louie

33