

07-Measurements

ECEGR 450
Electromechanical Energy Conversion



Overview

- Power Measurements
- Two Wattmeter Method
- Impedance Measurements

Dr. Louie

2



Questions

- How can you measure the complex power consumed by a load (or supplied by a generator)?
- How can total power be measured in systems with no neutral?
- How can you measure complex impedance?

Dr. Louie

3



Power Measurements

- Next we examine how to measure the power in a circuit
 - Single phase power
 - Three phase power
- Interested in measuring P and PF (power factor)
 - S , Q can be computed from P, PF


Dr. Louie

4



Power Measurements

- Consider a single phase circuit
- To measure the P and PF of the load, we need to know \mathbf{V} and \mathbf{I}
- Consider a voltmeter connected across the load
- Voltmeters measure the RMS voltage
 - RMS voltage is $|\mathbf{V}|$
 - Voltmeters have high (Mega-Ohm) internal impedances so we are not worried about shorting the source

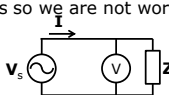


Dr. Louie

5



Power Measurements

- We can measure $|\mathbf{I}|$ with an Ammeter
- Where should we connect the Ammeter?

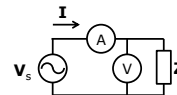


Dr. Louie

6

Power Measurements


- Ammeters measure the RMS current
 - RMS current is $|\mathbf{I}|$
 - Ammeters have low (milli-Ohm) internal impedances so we can put it in series

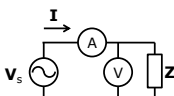

7

Power Measurements


- We now have $|\mathbf{V}|$ and $|\mathbf{I}|$, but this is not enough information to determine P and PF
- We need to know the phase difference between \mathbf{V} and \mathbf{I}
- Possible to use a single meter (or oscilloscope) to measure current, voltage and phase angle

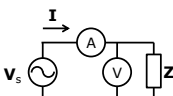

8

Power Measurements

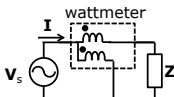
- Lets assume you do not have such an instrument, but you do have an Wattmeter
- Wattmeters measure average power P
 - Contains a current coil and voltage coil
 - Polarity is important



9

Power Measurements

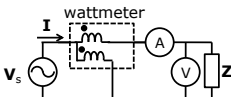
- If you use a wattmeter, voltmeter and ammeter you can determine P and PF
 - P from the Wattmeter
- How can you compute PF? Write the equation.
 - See text example 1.6 for a numerical example



10

Power Measurements


- How can you compute PF?
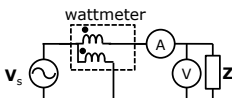
$$\frac{P}{|\mathbf{I}| |\mathbf{V}|} = \frac{P}{|\mathbf{S}|} = \text{PF}$$


11

Three Phase Power Measurements

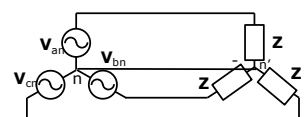- If the neutral wire is available, simply set up 3 wattmeters (each connected to a different phase and to the neutral)
 - Add the readings to find the total P
 - If the system is balanced, all wattmeters will have the same reading



12

Three Phase Power Measurements

- If the neutral is not available or if either the source or load are Delta connected the two-wattmeter method can be used
- Note: line voltages are connected to the wattmeters

Dr. Louie 13

Three Phase Power Measurements

Wattmeter 1 reads:

$$P_1 = \text{Re}\{\mathbf{V}_{ab} \mathbf{I}_{na}^*\}$$

$$= \text{Re}\{(|\mathbf{V}_{ab}| \angle 30^\circ)(|\mathbf{I}_{na}| \angle \theta_{ia})^*\}$$

$$= \text{Re}\{(\sqrt{3} |\mathbf{V}_{an}| \angle 30^\circ)(|\mathbf{I}_{na}| \angle \phi)\}$$

$$= \sqrt{3} |\mathbf{V}_{an}| |\mathbf{I}_{na}| \cos(30 + \phi)$$

Note: this is not the a-phase power

Setting θ_{an} as reference angle
 $\phi = \theta_{ia} - \theta_{ia}$
 $\theta_{ia}^* = -\theta_{ia} = \phi$

Dr. Louie 14

Power Measurements

Wattmeter 2 reads:

$$P_2 = \text{Re}\{\mathbf{V}_{cb} \mathbf{I}_{nc}^*\}$$

$$= \text{Re}\{(|\mathbf{V}_{cb}| \angle 90^\circ)(|\mathbf{I}_{nc}| \angle \theta_{ia} + 120^\circ)^*\}$$

$$= \text{Re}\{(\sqrt{3} |\mathbf{V}_{cn}| \angle 90^\circ)(|\mathbf{I}_{nc}| \angle \phi - 120^\circ)\}$$

$$= \sqrt{3} |\mathbf{V}_{cn}| |\mathbf{I}_{nc}| \cos(-30 + \phi)$$

$$= \sqrt{3} |\mathbf{V}_{cn}| |\mathbf{I}_{nc}| \cos(30 - \phi)$$

Note: this is not the c-phase power

Dr. Louie 15

Power Measurements

- Adding the readings:

$$P_{3\phi} = P_1 + P_2$$

$$= \sqrt{3} |\mathbf{V}_{an}| |\mathbf{I}_{na}| \cos(30 + \phi) + \sqrt{3} |\mathbf{V}_{cn}| |\mathbf{I}_{nc}| \cos(30 - \phi)$$

$$= \sqrt{3} |\mathbf{V}_{cn}| |\mathbf{I}_{nc}| (\cos(30 + \phi) + \cos(30 - \phi))$$

using: $\cos(30 + \phi) = \cos(30)\cos(\phi) - \sin(30)\sin(\phi)$
 $\cos(30 - \phi) = \cos(30)\cos(\phi) + \sin(30)\sin(\phi)$
 $\Rightarrow \cos(30 + \phi) + \cos(30 - \phi) = 2\cos(30)\cos(\phi)$

$$P_{3\phi} = \sqrt{3} |\mathbf{V}_{an}| |\mathbf{I}_{na}| 2 \frac{\sqrt{3}}{2} \cos(\phi)$$

$$= 3 |\mathbf{V}_{an}| |\mathbf{I}_{na}| \cos(\phi)$$

This is the 3 times the per-phase power so the two wattmeter method works

Dr. Louie 16

Power Measurements

- Adding the two readings on the wattmeters equals the total power due to:

$$P_{3\phi} = 3 |\mathbf{V}_{an}| |\mathbf{I}_{na}| \cos(\phi)$$

$$P_{3\phi} = \sqrt{3} |\mathbf{V}_l| |\mathbf{I}_l| \cos(\phi)$$

- V_l : line-line voltage
- I_l : line current

- Depending on the source/load configuration either

$$|\mathbf{V}_l| = \sqrt{3} |\mathbf{V}_a| \text{ and } |\mathbf{I}_l| = |\mathbf{I}_a|$$

or

$$|\mathbf{V}_l| = |\mathbf{V}_a| \text{ and } |\mathbf{I}_l| = \sqrt{3} |\mathbf{I}_a|$$

Dr. Louie 17

Example

- Let the line-line voltage be 480
- Let $\mathbf{Z} = 6 + 12j$
- The voltage coil of wattmeter 1 is place from a phase to b phase and its current coil is connected to a phase
- The voltage coil of wattmeter 2 is place from c phase to b phase and its current coil is connected to c phase
- Find P_1 , P_2 and the total power to the load

Dr. Louie 18

Example

- First find the line currents for a-phase and c-phase (let V_{an} be the reference)

$$I_{na} = \frac{480/\sqrt{3}}{2 + 4j} = 27.7 - j55.42 = 61.97 \angle -63.4^\circ$$

$$I_{nc} = 61.97 \angle 56.6^\circ$$

Dr. Louie 19

Example

- Power read by wattmeter 1 is:

$$V_{ab} = V_{an} - V_{bn} = 480 \angle 30^\circ$$

$$P_1 = \text{Re}\{(480 \angle 30^\circ)(61.97 \angle -63.4^\circ)^*\} = -1782W$$

- Power read by wattmeter 2 is:

$$V_{cb} = V_{cn} - V_{bn} = 480 \angle 90^\circ$$

$$P_2 = \text{Re}\{(480 \angle 90^\circ)(61.97 \angle 56.6^\circ)^*\} = -24,822W$$

- Total power is:

$$P_{3\phi} = P_1 + P_2 = 23,040W$$


Dr. Louie 20

Example

- We can verify by examining the per-phase equivalent:

$$I_a = \frac{277 \angle 0^\circ}{2 + 4j} = 61.9 \angle -63.4^\circ$$


$$P_a = \text{Re}\{(277 \angle 0^\circ)(61.9 \angle -63.4^\circ)^*\} = 7680W$$
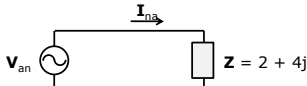
$$P_{3\phi} = 3 \times 7680 = 23,040W \quad \text{values match}$$


Dr. Louie 21

Impedance Measurements

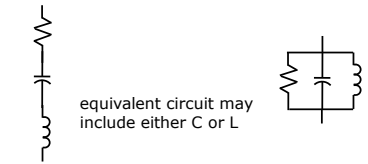- We are interested in modeling the impedance of unknown loads as well as machines
- Want to develop an equivalent circuit model
 - Series model
 - Parallel model




equivalent circuit may include either C or L

Dr. Louie 22

Impedance Measurements

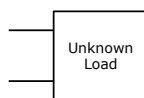
- Consider a single-phase load with unknown components
 - Assume we know the rated voltage and frequency
- How should be determine its equivalent series or parallel equivalent?



Dr. Louie 23

Impedance Measurements

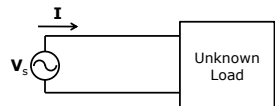
- Connect an AC source of known rated voltage and frequency
- Measure the current and power (we already know voltage)



Dr. Louie 24

Impedance Measurements

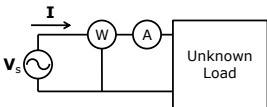- Need to know if current leads or lags the voltage
 - Use a two-channel oscilloscope (not shown)



Dr. Louie **25**

Impedance Measurements

- We know P , $|\mathbf{V}|$, $|\mathbf{I}|$, ϕ and if the load is leading or lagging
- We can compute:
 - $|\mathbf{S}| = |\mathbf{V}| |\mathbf{I}|$
 - $\phi = \cos^{-1}(P / |\mathbf{S}|)$ (if current lags voltage)
 - $\phi = -\cos^{-1}(P / |\mathbf{S}|)$ (if current leads voltage)
- Assuming voltage is taken as reference
 - $\mathbf{V} = |\mathbf{V}_s| \angle 0^\circ$

Dr. Louie **26**

Impedance Measurements

- To determine the equivalent series impedance
 - $\mathbf{Z}_s = \frac{\mathbf{V}}{\mathbf{I}} = R_s \pm jX_s$ (need to know \mathbf{I})
 - \mathbf{Z}_s : equivalent series impedance (Ohms)
 - R_s : equivalent series resistance (Ohms)
 - X_s : equivalent series reactance (Ohms)
- $|\mathbf{I}|$ is measured by the ammeter, how do we find \mathbf{I} ?

Dr. Louie **27**

Impedance Measurements

- Note that the current phasor:
 - $\mathbf{I} = |\mathbf{I}| \angle \pm \phi = |\mathbf{I}| \cos \phi \pm j |\mathbf{I}| \sin \phi$
 - can be resolved into
 - $\mathbf{I} = i_r \pm j i_x$
 - through substitution:
 - $i_r = |\mathbf{I}| \cos \phi$
 - $i_x = |\mathbf{I}| \sin \phi$
- Note: i_r and i_x are not phasors

Dr. Louie **28**

Impedance Measurements

- The plus/minus in the previous slide is set based upon the observed phase between voltage and current from the oscilloscope
- If the current leads the voltage, what should the sign be?
 - $\mathbf{I} = |\mathbf{I}| \cos \phi \pm j |\mathbf{I}| \sin \phi$

Dr. Louie **29**

Impedance Measurements

- The plus/minus in the previous slide is set based upon the observed phase between voltage and current from the oscilloscope
- If the current leads the voltage, what should the sign be?
 - $\mathbf{I} = |\mathbf{I}| \cos \phi \pm j |\mathbf{I}| \sin \phi$
 - Positive.
 - A capacitive circuit
 - ELI the ICE man

Dr. Louie **30**

Impedance Measurements

- Comparing:

$$\mathbf{Z}_s = \frac{\mathbf{V}}{\mathbf{I}} = R_s \pm jX_s \text{ and } \mathbf{I} = i_r \pm ji_x$$
- We can solve:

$$\mathbf{Z}_s = \frac{\mathbf{V}}{\mathbf{I}} = R_s \pm jX_s$$

$$R_s = \text{Re}\{\mathbf{V} / \mathbf{I}\}$$

$$X_s = \text{Im}\{\mathbf{V} / \mathbf{I}\}$$

$$L = \frac{X_s}{\omega}$$

31

Summary

- $|\mathbf{V}|$: given by applied voltage source
- ω : given by applied voltage source
- θ_v : set to 0 degrees
- P: measured by wattmeter
- $|\mathbf{I}|$: measured by ammeter
- $|\mathbf{S}|$: computed
- ϕ : magnitude computed, sign determined by oscilloscope
- $$\mathbf{Z}_s = \frac{\mathbf{V}}{\mathbf{I}} = R_s \pm jX_s$$

$$R_s = \text{Re}\{\mathbf{V} / \mathbf{I}\}$$

$$X_s = \text{Im}\{\mathbf{V} / \mathbf{I}\}$$

$$L = \frac{X_s}{\omega}$$

$$\begin{cases} |\mathbf{S}| = |\mathbf{V}| |\mathbf{I}| \\ \phi = \cos^{-1}(P / |\mathbf{S}|) \\ \phi = -\cos^{-1}(P / |\mathbf{S}|) \end{cases}$$

32


Impedance Measurements

- In a parallel circuit the real portion of the current must flow through R , and the reactive through X
- Since \mathbf{V} is applied in parallel to both:

$$R_p = \frac{|\mathbf{V}|}{i_r}$$

$$X_p = \frac{|\mathbf{V}|}{i_x}$$

$$C = \frac{1}{X_p \omega}$$

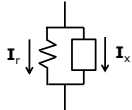

33

Impedance Measurements

- See text Example 1.9 for how these concepts are applied to three phase loads

34

Summary

- Voltage and current magnitude and phase information is needed to compute complex power
- Measuring and computing impedances are useful in testing electrical machines

35