

# 09-Circuit Theorems

Text: 4.1 - 4.3, 4.8

ECEGR 210

Electric Circuits I



# Overview

- Introduction
- Linearity
- Superposition
- Maximum Power Transfer



# Introduction

- Nodal and mesh analysis can be tedious to apply to large circuits, especially with multiple sources
- Linearity of the circuits considered can be exploited to simplify analysis




# Linearity

- Circuits considered in the this class are linear
- An equation  $f(x)$  or system is linear iff
  - Homogeneity:  $f(ax) = af(x)$
  - Additivity:  $f(x + y) = f(x) + f(y)$


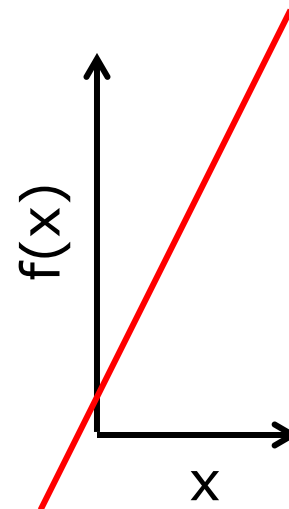
# Linearity

- Is  $f(x) = 2x + 1$  linear?
- Check homogeneity:  $f(ax) = af(x)$   
 $2ax + 1 \neq a(2x + 1)$
- Check additivity :  $f(x + y) = f(x) + f(y)$   
 $2(x + y) + 1 \neq 2x + 1 + 2y + 1$
- No. This is an affine function





# Linearity

- What about Ohm's Law ( $V=IR$ )? Let  $I$  be the argument so that  $f(x) = V(I)$
- Check homogeneity:  $f(ax) = af(x)$   
 $aIR = a(IR)$
- Check additivity:  $f(x + y) = f(x) + f(y)$   
 $(I_a + I_b)R = I_aR + I_bR$
- Yes. A circuit is linear if it consists only of linear elements, linear dependent sources and independent sources



# Linearity


- What about  $P=IV$ ?
  - Careful.  $V = IR$ , so  $P = I^2R$
- Check homogeneity:  $f(ax) = af(x)$   
 $(aI)^2R \neq aI^2R$
- Check additivity:  $f(x + y) = f(x) + f(y)$   
 $(I_1 + I_2)^2R \neq I_1^2R + I_2^2R$
- No. The power dissipated by a resistor is not linear.


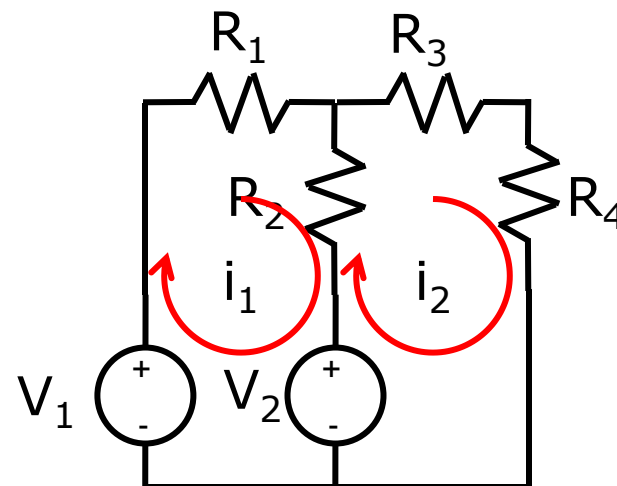
# Significance of Linearity

- The mesh currents for the shown circuit can be written as (by inspection):

$$\underbrace{\begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 + R_4 \end{bmatrix}}_{\mathbf{A} \text{ (matrix)}} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 - V_2 \\ V_2 \end{bmatrix}$$



$$\mathbf{A} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 - V_2 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \mathbf{A}^{-1} \begin{bmatrix} V_1 - V_2 \\ V_2 \end{bmatrix}$$

Solving for  $i_1, i_2$






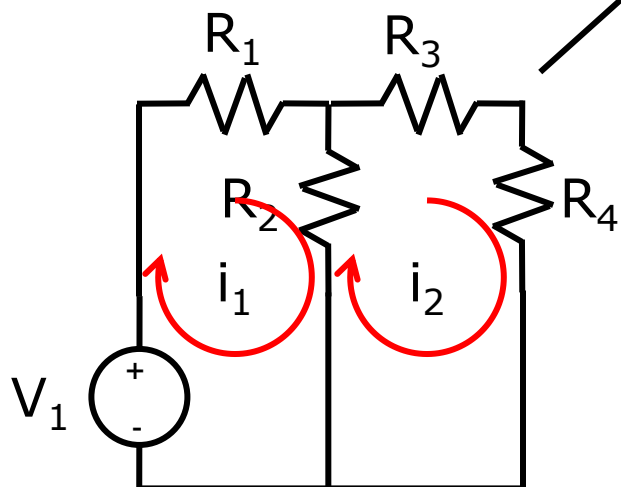
# Significance of Linearity

- Observing that:

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \mathbf{A}^{-1} \begin{bmatrix} V_1 - V_2 \\ V_2 \end{bmatrix} = \underbrace{\mathbf{A}^{-1} \begin{bmatrix} V_1 - 0 \\ 0 \end{bmatrix}} + \underbrace{\mathbf{A}^{-1} \begin{bmatrix} 0 - V_2 \\ V_2 \end{bmatrix}}$$



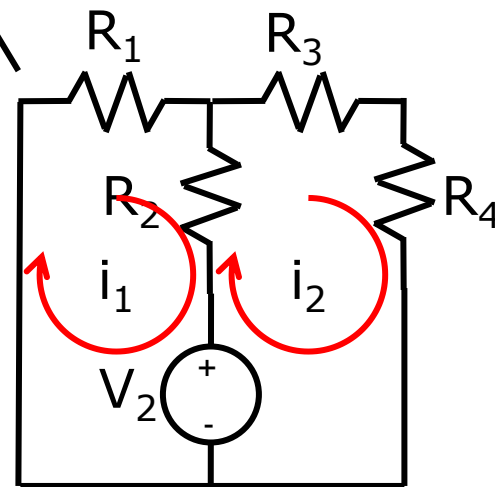
We can solve two  
"easier" circuits,  
and add the  
results!




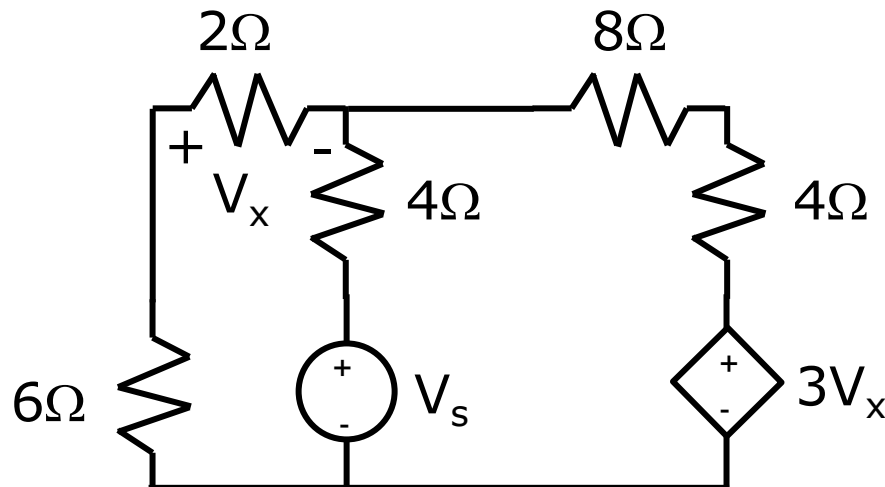
# Significance of Linearity

- Find the current out of the dependent voltage source if  $V_s = 12V$ , and if  $V_s = 24V$ 
  - Should we use nodal or mesh analysis?






# Significance of Linearity

- since  $V_s = 12V$

$$0 = 12i_1 - 4i_2 + V_s \text{ (mesh 1)}$$

$$0 = -4i_1 + 16i_2 - 3V_x \text{ (mesh 2)}$$

$$v_x = 2i_1$$

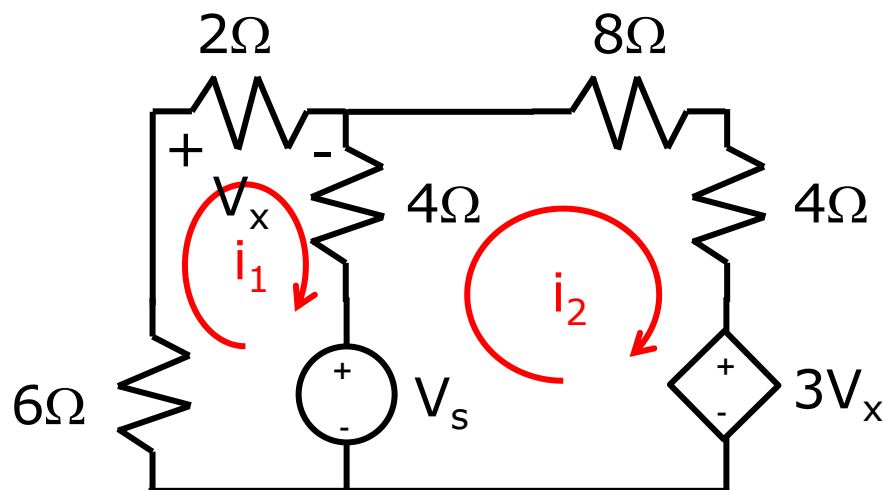



# Significance of Linearity

$$V_s = 12V$$

$$0 = 12i_1 - 4i_2 + V_s$$

$$0 = -10i_1 + 16i_2$$

adding...


$$2i_1 + 12i_2 = 0$$

$$i_1 = -6i_2$$

via substitution

$$-76i_2 + V_s = 0$$

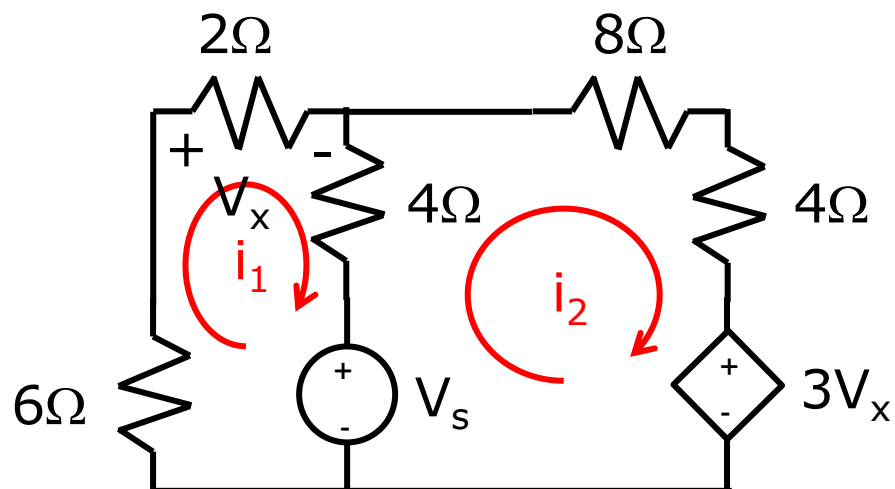
$$i_2 = \frac{V_s}{76} = \frac{12}{76} = 0.158A$$




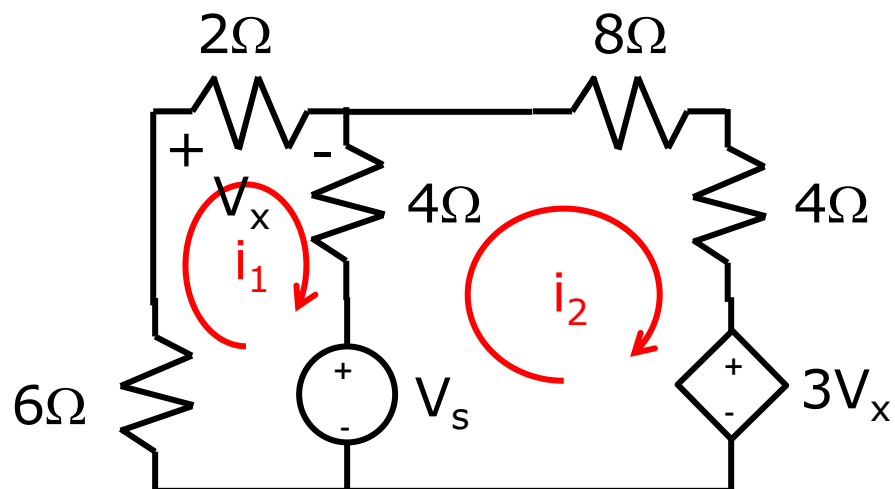
# Significance of Linearity

- By linearity: if  $V_s = 24V$  (voltage doubled)
  - $i_2 = 2 \times 0.158A = 0.316A$  (current doubled)
- No need to re-solve the circuit
- Behold, the power of linearity!





# Superposition


- One of the most important circuit analysis benefits of linearity is that superposition can be applied
- Very useful for circuits with multiple independent sources
- Basic idea: analyze the circuit considering only one source at a time, and sum the results once all sources have been considered
  - Valid for all circuit analysis techniques: Nodal, mesh, Ohm's Law, etc.



# Superposition

- Simple example with  $V_1 = 10V$ ,  $V_2 = 15V$
- Find  $I$


$$I = \frac{V_1 - V_2}{R} = -1A$$

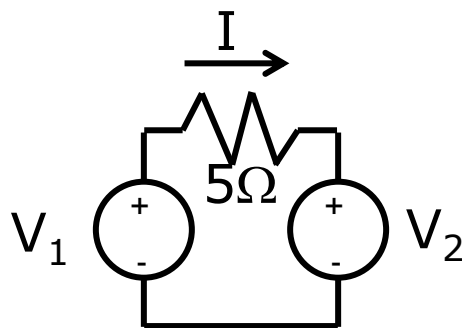


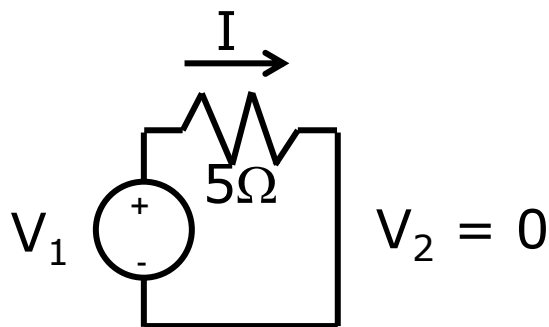
# Superposition

- Now solve using superposition
- Consider  $V_1$  only
  - Remove contribution from  $V_2$  (set source to 0, a short circuit)
  - $I_{V_1} = 2A$







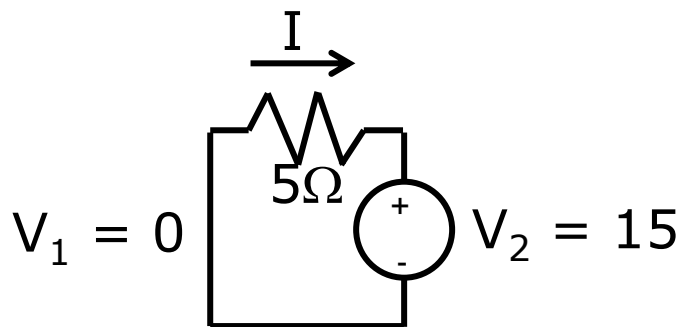
# Superposition

- Consider  $V_2$  only
  - Remove contribution from  $V_1$  (set source to 0, a short circuit)
  - $I_{V_2} = -3A$





# Superposition

- Combining
  - $I = I_{V_2} + I_{V_2} = -1A$
  - Same result as solving the circuit simultaneously




# Superposition

- Analyze circuit with only one independent source at a time
- Independent voltage sources are ignored by replacing them with a short (voltage source where  $V_s = 0$ )
- Independent current sources are ignored by replacing them with an open circuit (current source where  $I_s = 0$ )
- Dependent sources are not ignored
- Sum individual results to analyze circuit



# Example



- Find  $V_R$  using superposition.

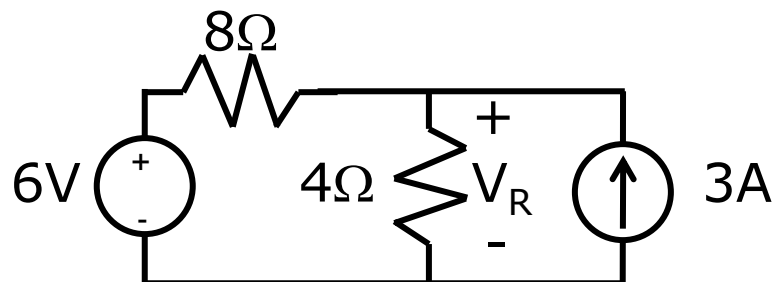


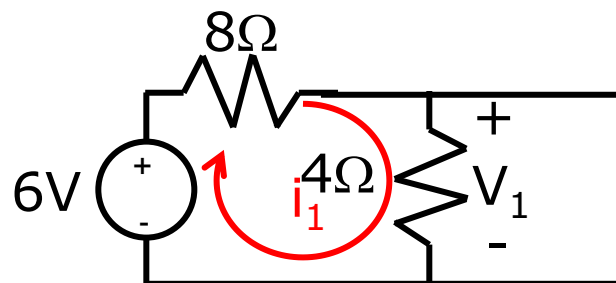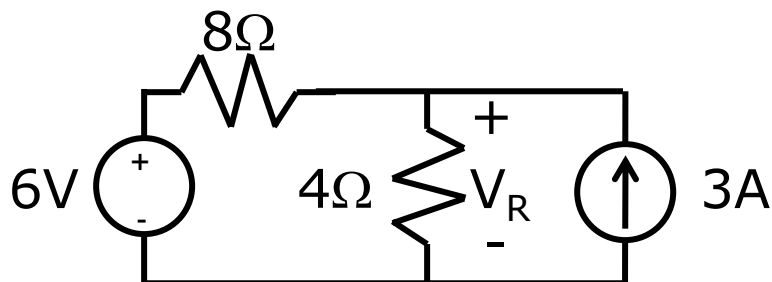
## Example



- Consider the voltage source first. Set current source to 0A (open circuit)
- By KVL:
  - $12i_1 - 6 = 0$
  - $i_1 = 0.5A$
  - $V_1 = 2V$  ( $V_R$  due to voltage source)




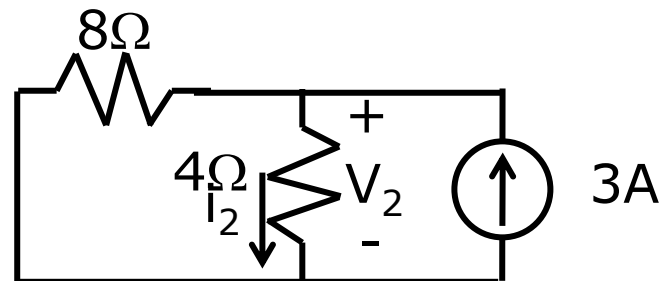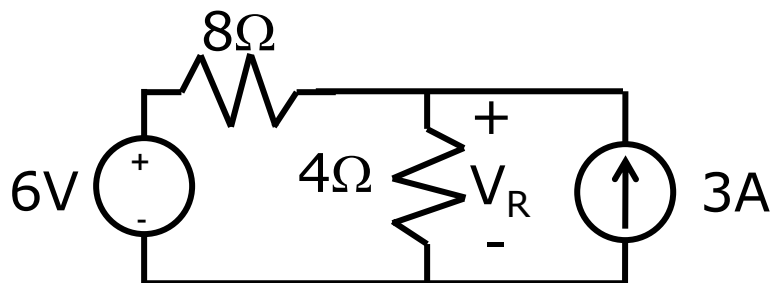
## Example

- Now consider the current source. Set voltage source to 0V (short circuit)
- By current division:
  - $i_2 = (3 \times 8) / (12) = 2A$
  - $V_2 = 8V$  ( $V_R$  due to current source)






## Example

- Now sum results:
  - $V_R = V_1 + V_2 = 10V$
- Note:
  - $i_R = i_1 + i_2 = 2.5A$
  - $P_R = i_R^2 R = (i_1 + i_2)^2 R = 31.25W$
  - $P_R \neq P_1^2 + P_2^2$
  - Any power calculations must be done after all sources considered



# Example

- Use superposition to find  $V_x$

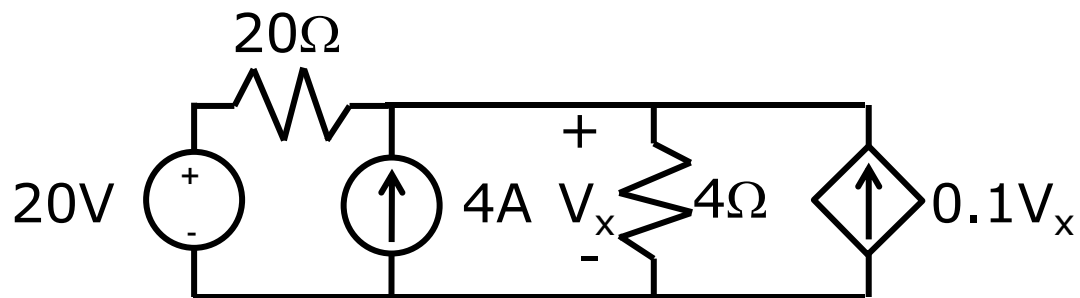







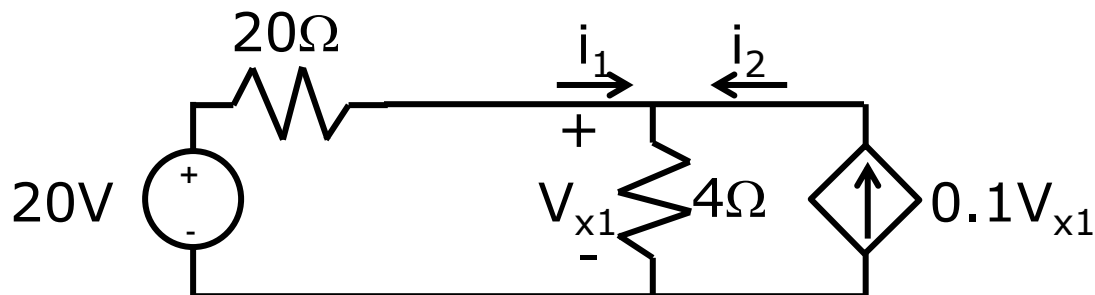
## Example

- First consider voltage source.
- Use nodal analysis
  - Trying to find node voltage
  - Only one node with unknown voltage
  - Many elements in parallel





## Example

- KCL of node


$$i_{x1} = i_1 + i_2$$

via substitution:

$$\frac{V_{x1}}{4} = \frac{20 - V_{x1}}{20} + 0.1V_{x1}$$

$$V_{x1} - 0.4V_{x1} + 0.2V_{x1} = 4$$



$$V_{x1} = 5V$$

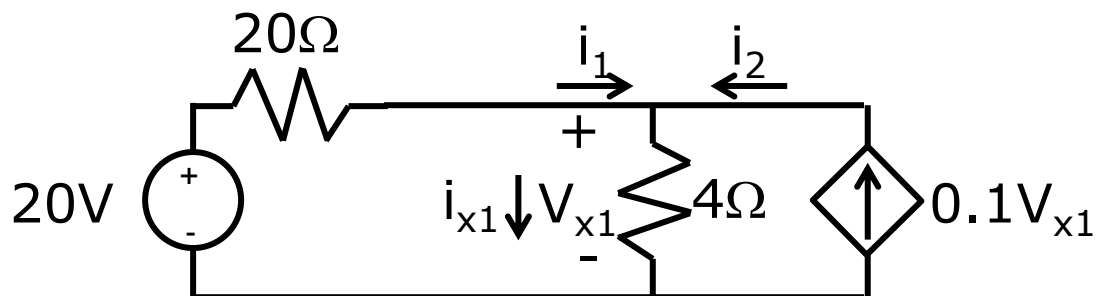


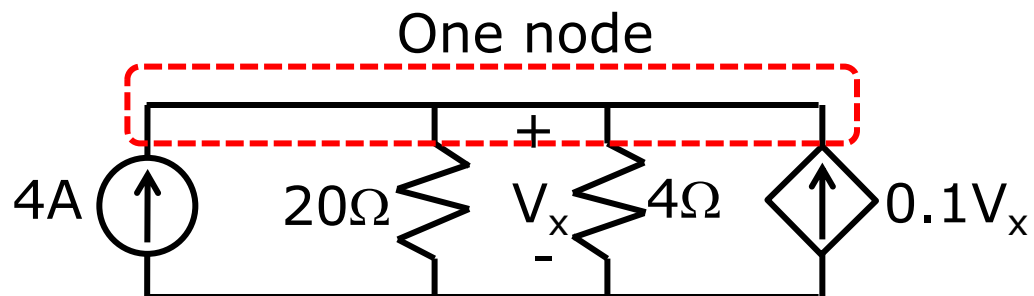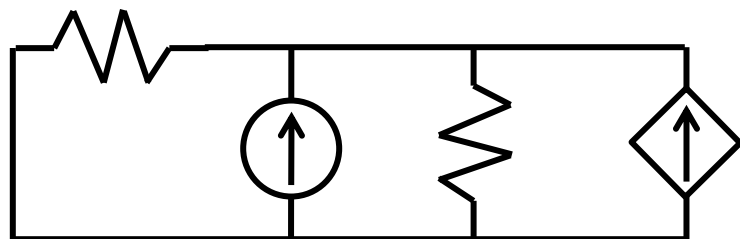
## Example

- Now consider current source.
- Rearrange parallel elements for clarity
- Use nodal analysis
  - Trying to find node voltage
  - Only one node with unknown voltage
  - Many elements in parallel





## Example

- Now consider current source:



$$4 + 0.1V_{x2} = i_{20} + i_{x2}$$

via substitution:

$$4 + 0.1V_{x2} = \frac{V_{x2}}{20} + \frac{V_{x2}}{4}$$

$$4 = 0.05V_{x2} + 0.25V_{x2} - 0.1V_{x2}$$

$$V_{x2} = 20V$$

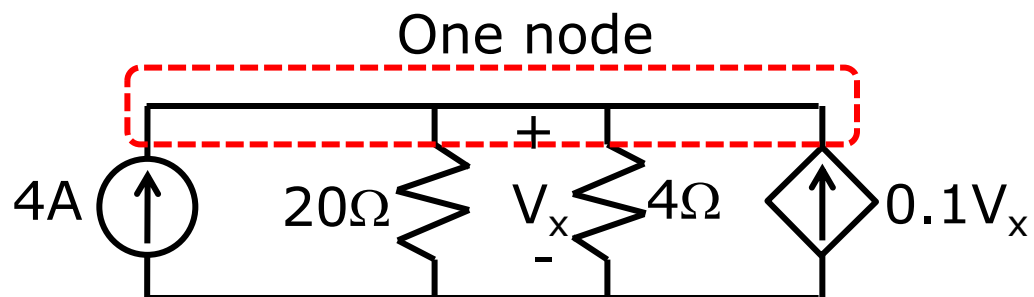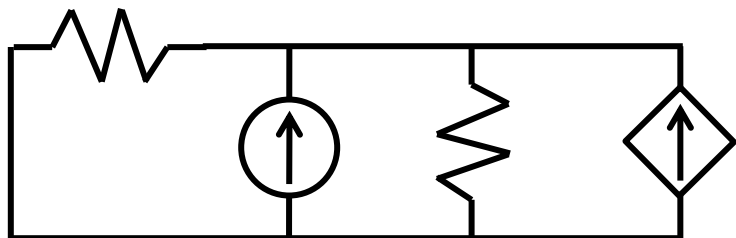



## Example


- Summing results:
  - $V_x = V_{x1} + V_{x2} = 25V$


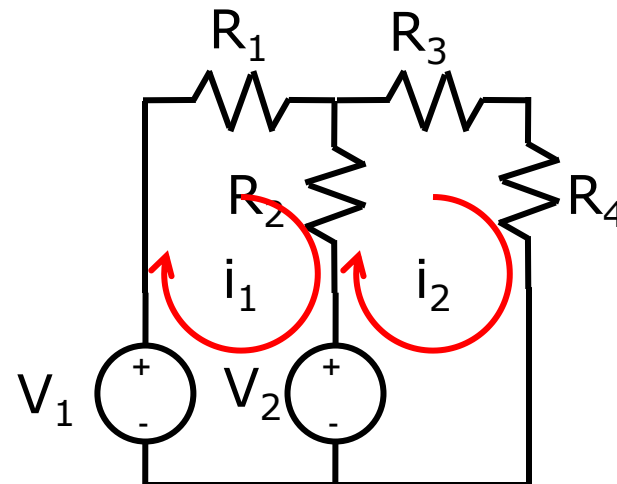
# Significance of Linearity

- Consider past example

$$\underbrace{\begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 + R_4 \end{bmatrix}}_{\mathbf{A} \text{ (matrix)}} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 - V_2 \\ V_2 \end{bmatrix}$$





# Significance of Linearity

- Assume that we solved for  $i_1$  and  $i_2$
- If the voltage sources are increased by a factor of  $x$ , what happens to  $i_1$  and  $i_2$ ?

$$\mathbf{A} \begin{bmatrix} i_1^{\text{new}} \\ i_2^{\text{new}} \end{bmatrix} = x \begin{bmatrix} V_1 - V_2 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} i_1^{\text{new}} \\ i_2^{\text{new}} \end{bmatrix} = x \underbrace{\mathbf{A}^{-1} \begin{bmatrix} V_1 - V_2 \\ V_2 \end{bmatrix}}_{\begin{bmatrix} i_1 \\ i_2 \end{bmatrix}}$$

$$\begin{bmatrix} i_1^{\text{new}} \\ i_2^{\text{new}} \end{bmatrix} = x \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \quad \text{Current also increases by } x$$






# Significance of Linearity

- If **all** the voltages are proportionally increased/decreased, then **all** current will also proportionally increase/decrease
  - What happens if all the resistances are proportionally changed?
- Useful if you have already solved the circuit and want to examine how changes will affect the solution


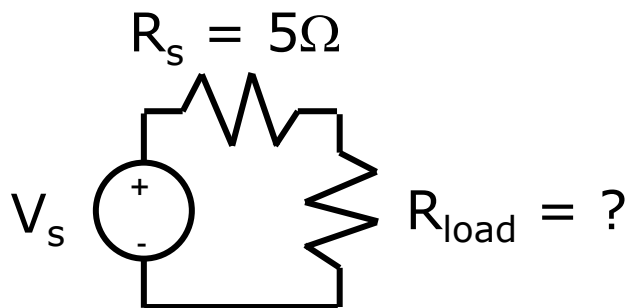
# Maximum Power Transfer


- Often interested in designing a circuit so that the maximum power is delivered (transferred) to a load
- Consider an 11V battery connected to a heater by way of a cable
- What resistance should  $R_{\text{load}}$  be to maximize the power it consumes?




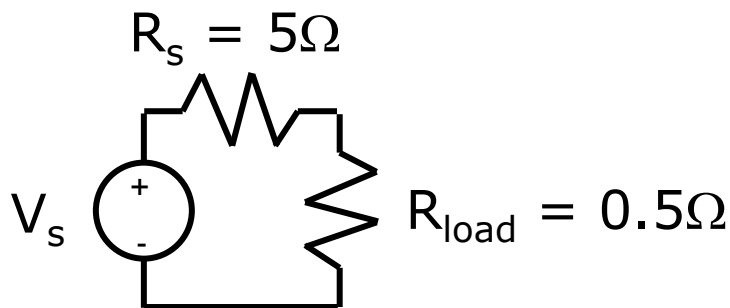
# Maximum Power Transfer

- Idea: try a small resistance in order to increase current ( $P = I^2R$ )
  - Let  $R_{\text{load}} = 0.5\Omega$
- Compute power to the load resistor and power consumed by the cable






# Maximum Power Transfer

$$P_{\text{load}} = I^2 R_{\text{load}} = \left( \frac{V_s}{R_{\text{load}} + R_s} \right)^2 R_{\text{load}} = \left( \frac{11}{0.5 + 5} \right)^2 0.5 = 2\text{W}$$

$$P_s = I^2 R_{\text{load}} = \left( \frac{11}{0.5 + 5} \right)^2 5 = 10\text{W}$$

- More power is consumed by the cable than the load
- Only small portion of applied voltage is across the load


- $V_{\text{load}} = 1\text{V}$

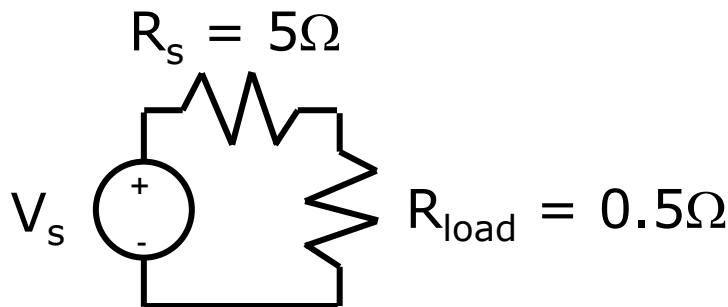


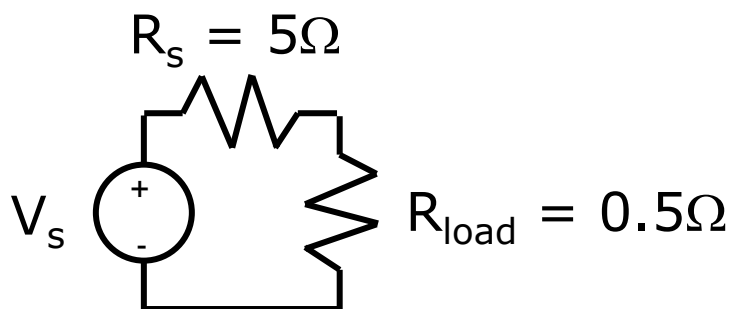
# Maximum Power Transfer

- New idea: try large resistance so a large voltage appears across the load ( $P = V^2/R$ )
  - Let  $R_{\text{load}} = 50\Omega$
- Compute power to the load resistor and power consumed by the cable






# Maximum Power Transfer

$$P_{\text{load}} = I^2 R_{\text{load}} = \left(\frac{11}{5 + 50}\right)^2 50 = 2\text{W}$$

$$P_s = I^2 R_{\text{load}} = \left(\frac{11}{5 + 50}\right)^2 5 = 10\text{W}$$

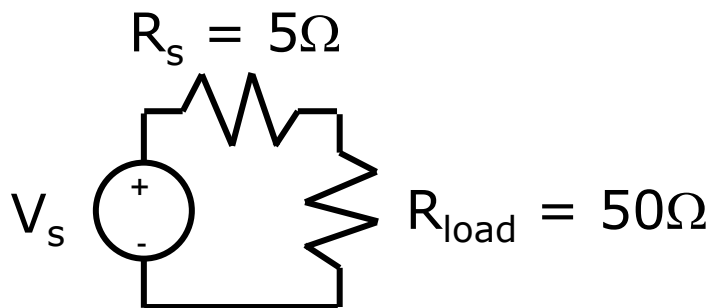- More power is consumed by the cable than the load
- Small amount of current flows
  - $I = 0.2\text{A}$





# Maximum Power Transfer

- Trade-off between voltage across load and current through load resistor
- Try  $R_{\text{load}} = R_s$




# Maximum Power Transfer

$$P_{\text{load}} = I^2 R_{\text{load}} = \left(\frac{11}{5+5}\right)^2 5 = 6.05\text{W}$$

$$P_s = I^2 R_{\text{load}} = \left(\frac{11}{5+5}\right)^2 5 = 6.05\text{W}$$

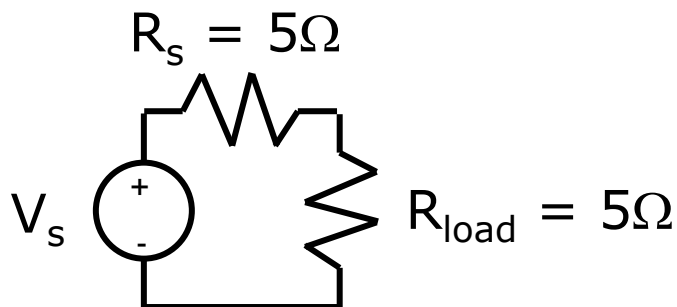- Power to load is increased
  - $V_{\text{load}} = 5.5\text{V}$
  - $I = 1.1\text{A}$







# Maximum Power Transfer

- Maximum power transfer occurs when  $R_{\text{load}} = R_s$
- Load and source (with series impedance) are said to be “matched”
- Observations
  - Voltage across load is one half applied power
  - Relationship between  $R_{\text{load}}$  and  $P_{\text{load}}$  must be non-linear



# Maximum Power Transfer

- Proof:

$$P_{\text{load}} = I^2 R_{\text{load}} = \left( \frac{V_s}{R_{\text{load}} + R_s} \right)^2 R_{\text{load}}$$

at maximum power transfer  $\frac{dP_{\text{load}}}{dR_{\text{load}}} = 0$

solving

$$\frac{dP_{\text{load}}}{dR_{\text{load}}} = \frac{V_s^2}{(R_{\text{load}} + R_s)^2} + \frac{-2V_s^2 R_{\text{load}}}{(R_{\text{load}} + R_s)^3}$$

$$\frac{dP_{\text{load}}}{dR_{\text{load}}} = V_s^2 \frac{R_{\text{load}} + R_s - 2R_{\text{load}}}{(R_{\text{load}} + R_s)^3} = 0$$

therefore

$$R_{\text{load}} = R_s$$



# Maximum Power Transfer

