

## 10-Combinational Circuit Design

Text: Unit 8

ECEGR/ISSC 201  
Digital Operations and Computations  
Winter 2011



## Overview

- Gates with Limited Fan-in
- Delays and Timing
- Other Hazards

Dr. Louie

2



## Limited Fan-in

- Practical logic gates are limited by the number of inputs they can handle (fan-in)
- Similar constraints on the number of gates the output can be connected to (fan-out)
- Solution to limited fan-in: factor into a multi-level expression
- Solution to limited fan-out: use buffers (discussed in the next lecture)

Dr. Louie

3



## Limited Fan-in

- Consider  $F(A, B, C, D) = \sum m(0, 3, 4, 5, 8, 9, 10, 14, 15)$
- Design using NOR gates

	AB			
CD	00	01	11	10
00	1	1	0	1
01	0	1	0	1
11	1	0	1	0
10	0	0	1	1

Dr. Louie

4



## Limited Fan-in

- Recall NOR-NOR requires starting with PoS form
- $F' = A'B'C'D + AB'CD + ABC' + A'BC + A'CD'$

	AB			
CD	00	01	11	10
00	1	1	0	1
01	0	1	0	1
11	1	0	1	0
10	0	0	1	1

Dr. Louie

5



## Limited Fan-in

$$F' = A'B'C'D + AB'CD + ABC' + A'BC + A'CD'$$

$$F = (A'B'C'D + AB'CD + ABC' + A'BC + A'CD')'$$

$$F = (A+B+C+D')(A'+B+C'+D')(A'+B'+C)(A+B'+C')(A+C'+D)$$

Next  $F = \{(F)'\}'$

$$F = \{(A+B+C+D)' + (A'+B+C'+D)'\} + (A'+B'+C)' + (A+B'+C)' + (A+C'+D)'\}'$$

Dr. Louie

6

**Limited Fan-in**

- $F = \{(A+B+C+D)'\} + (A'+B+C'+D)'\} + (A'+B'+C) + (A+B'+C') + (A+C'+D)'\}$
- This requires:
  - Three, 3-input NOR
  - Two, 4-input NOR
  - One, 5-input NOR
- What if we are limited to 3-input NORs only?

Dr. Louie 7

**Limited Fan-in**

- Start with:  
 $F' = A'B'C'D + AB'CD + ABC' + A'BC + A'CD'$
- Factor to:  
 $F' = B'D(A'C' + AC) + A'C(B+D') + ABC'$
- Convert this to NOR-NOR form

Dr. Louie 8

**Limited Fan-in**

$F' = B'D(A'C' + AC) + A'C(B+D') + ABC'$   
 $F = [B+D' + (A+C)(A'+C')][A+C'+B'D][A'+B'+C]$   
 Next  $F = \{(F)'\}$

Dr. Louie 9

**Limited Fan-in**

$F = [B+D' + (A+C)(A'+C')][A+C'+B'D][A'+B'+C]$   
 Next  $F = \{(F)'\}$   
 $F = \{[B+D' + (A+C)(A'+C')][A+C'+B'D][A'+B'+C]\}'$   
 $F = \{[B+D' + (A+C)(A'+C')]' + [A+C'+B'D]' + [A'+B'+C]'\}$   
 Using  $(A+C)(A'+C') = \{[(A+C)(A'+C')]\}'$  and  $B'D = [(B'D)']'$  yields:  
 $F = \{[B+D' + ((A+C)' + (A'+C)')] + [A+C' + (B+D)'] + [A'+B'+C]\}'$

Dr. Louie 10

**Limited Fan-in**

Build the circuit of  
 $F = \{[B+D' + ((A+C)' + (A'+C)')] + [A+C' + (B+D)'] + [A'+B'+C]\}'$

Dr. Louie 11

**Limited Fan-in**

$F' = B'D(A'C' + AC) + A'C(B+D') + ABC'$   
 Recall that you can build:  
 $F = [B+D' + (A+C)(A'+C')][A+C'+B'D][A'+B'+C]$

Dr. Louie 12

### Limited Fan-in

$F = [B+D' + (A+C)(A'+C')][A+C'+B'D][A'+B'+C]$

And replace the gates with NORs, and invert the single literal inputs to levels 1, 3, 5 etc (see text page 188)

Dr. Louie 13

### Limited Fan-in

- Design procedure for multi-output circuits
  - Minimize individually (common terms are usually lost when factoring)
  - Factor individually as needed to meet fan-in requirements

Dr. Louie 14

### Gate Delays

- Output changes do not occur instantaneously
- Propagation delay,  $\epsilon$
- On the order of 1 nanosecond
- Propagation delay is not symmetric
  - 0 to 1  $\epsilon_1$
  - 1 to 0  $\epsilon_2$
- In multi-level circuits, the delay can be important

Dr. Louie 15

### Gate Delays

- Example of an inverter propagation delay

Dr. Louie 16

### Example

- Assume the delays are 20 ns for each gate
- Let  $B = 1$  and  $C = 0$ , A changes as shown

Dr. Louie 17

### Example

- Draw the timing diagram if the delay for gate 1 is 10 ns and gate 2 is 15 ns
- Assume
  - A is low from 0 to 10ns and high from 10 ns to 30 ns
  - B = 0, and C = 1

Dr. Louie 18

**Example**

- Draw the timing diagram if the delay for gate 1 is 10 ns and gate 2 is 15 ns

time (ns)

Dr. Louie 19

**Hazards in Combinational Logic**

- Transients can occur if propagation delays are different for the various IC
- Static 1-hazard: when the output should be a 1 but it momentarily goes to 0 in response to an input change
- Static 0-hazard: when the output should be a 0 but it momentarily goes to 1 in response to an input change

Dr. Louie 20

**Hazards in Combinational Logic**

- Dynamic hazard: when the output is supposed to change from 1 to 0 or 0 to 1 and the change occurs three or more times

time

Dr. Louie 21

**Hazards in Combinational Logic**

- Consider:  $F = AB' + BC$
- Assume that
  - A=1
  - C=1
- Then:  $F = B' + B = 1$
- F should remain at 1 when B changes from 0 to 1 or 1 to 0

Dr. Louie 22

**Hazards in Combinational Logic**

- Timing diagram:

time (ns)

Dr. Louie 23

**Hazards in Combinational Logic**

- Is this a static 1 or static 0 hazard?
- Static 1 hazard

time (ns)

Dr. Louie 24



### Hazards in Combinational Logic

- We can identify potential hazards by examining K-maps
- No single loop covers  $ABC$  and  $AB'C$
- If  $A=C=1$  and  $B$  changes, both can momentarily go to 0

	A	
BC	0	1
00	0	1
01	0	1
11	1	1
10	0	0

Dr. Louie

25



### Hazards in Combinational Logic

- Procedure for examining K-maps for hazards
  - Write down SoP form of expression
  - Plot each term on the K-map and loop as necessary
  - If any two adjacent 1s are not covered by the same loop, a static 1 hazard exists for the transition between the two 1s
  - For an n-variable k-map, the transition occurs when one variable changes and the other n-1 variables are held constant

Dr. Louie

26



### Hazards in Combinational Logic

- To remove the hazard

	A	
BC	0	1
00	0	1
01	0	1
11	1	1
10	0	0


Dr. Louie

27



### Hazards in Combinational Logic

- Circuit with the hazard removed

 

Dr. Louie

28



### Hazards in Combinational Logic

- Static 0-hazards occur analogously with 0s on the K-map
- Procedure for the removal of static 1-hazards is analogous to removal of static 1-hazards

Dr. Louie

29



### Hazards in Combinational Logic

- Design of circuits without static hazards:
  - Find a SoP expression of  $F$  in which every pair of adjacent 1s is covered by a 1-term
    - This can be done by summing all the prime implicants
    - A two-level AND-OR circuit will be free of 1- and 0-static hazards and dynamic hazards
  - If a different form of  $F$  is needed, algebraically manipulate  $F$ , but treat literals and their complements as independent variables

Dr. Louie

30



### Example

- Derive an expression for F that eliminates static 0-hazards

	AB			
CD	00	01	11	10
00	0	0	1	1
01	0	0	0	0
11	1	1	0	0
10	1	0	0	1

Dr. Louie

31



### Example

- Derive an expression for F that eliminates static 0-hazards

$$F = (A+C)(A'+D')(B'+C'+D)(C+D')(A+B'+D)(A'+B'+C')$$

	AB			
CD	00	01	11	10
00	0	0	1	1
01	0	0	0	0
11	1	1	0	0
10	1	0	0	1

Dr. Louie

32