

# 10-Source Transformations

Text: 4.4 – 4.6

ECEGR 210

Electric Circuits I



# Overview


- Introduction
- Source Transformation
- Thevenin's Theorem
- Norton's Theorem




# Introduction

- Consider the two circuits (A and B) shown below
- Compute the voltage across the  $2\Omega$  resistor in each circuit

Circuit A

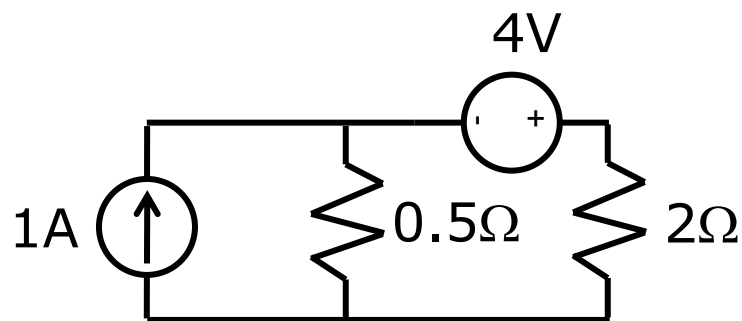



Circuit B

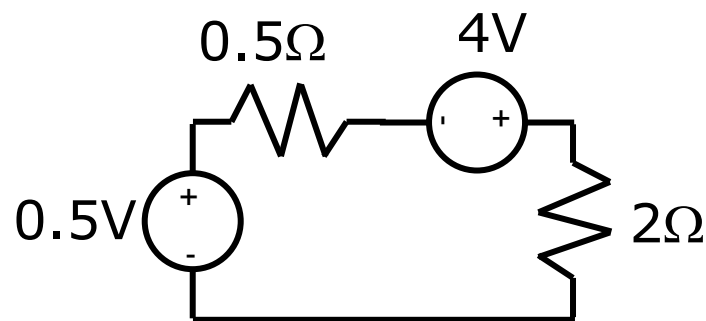


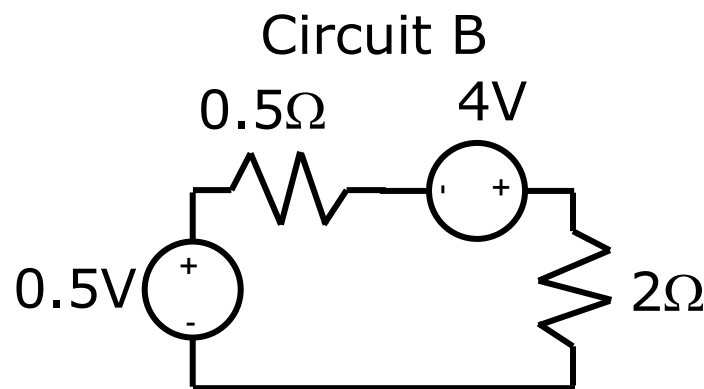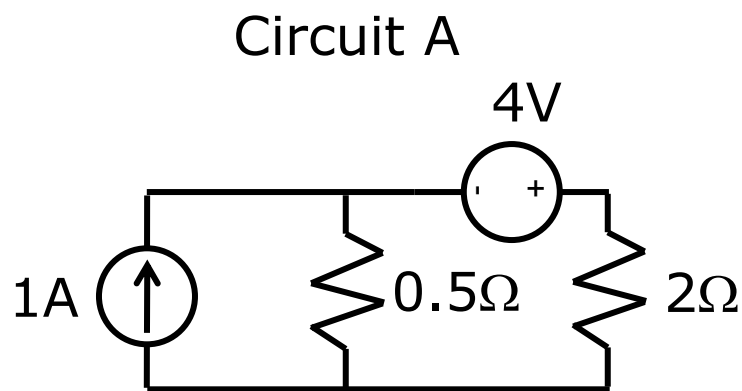
# Introduction



- Circuit A (superposition):
  - $V_{R1} = 2I_{R1} = 2 \times 1(0.5/2.5) = 0.4V$  (current source)
  - $V_{R2} = 4(2/2.5) = 3.2V$  (voltage source)
  - $V_R = V_{R1} + V_{R2} = 0.4 + 3.2 = 3.6V$
- Circuit B:  $V_R = 4.5(2/2.5) = 3.6V$  (voltage divider)




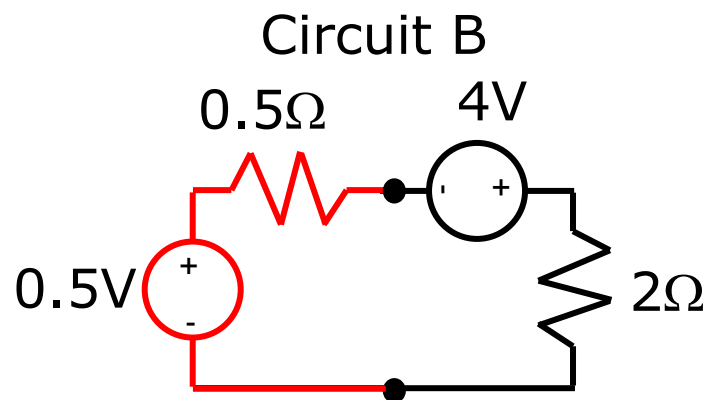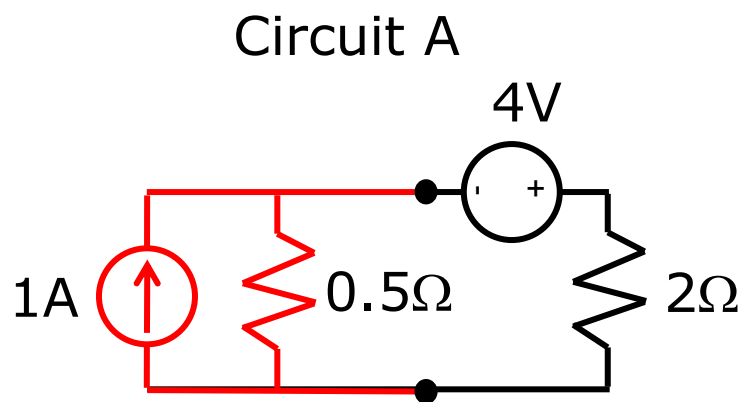
# Introduction


- Solving Circuit B was much easier
- Same voltage across (current through) the resistor
- Circuits are equivalent looking into the terminals




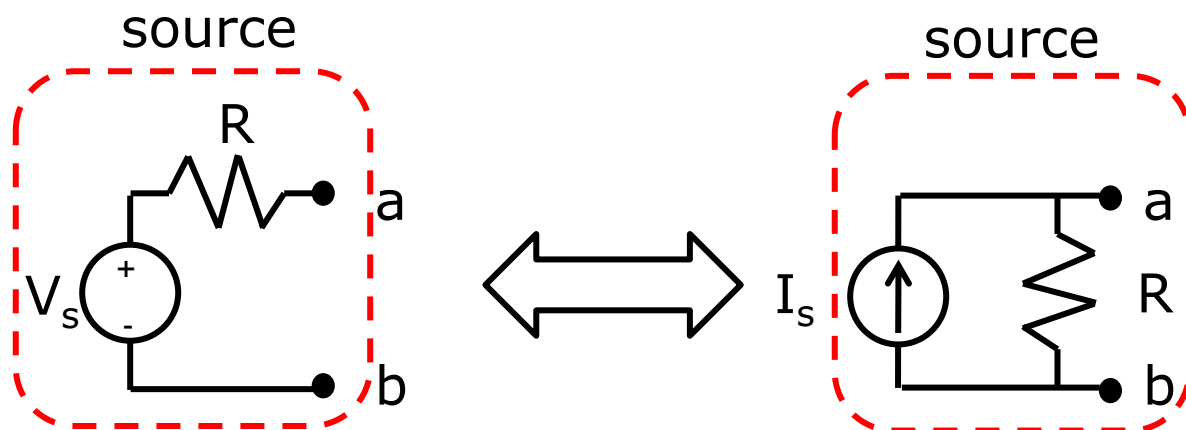
# Introduction


- Clearly there can be advantageous of transforming sources
- Source transformations and equivalence are the focus of this lecture





# Introduction


- Two ways of modeling real (non-ideal) voltage and current sources are shown
  - $R_s$ : small value, prevents infinite current from flowing if terminals (a,b) are shorted
  - $R_{||}$ : large value, prevents infinite voltage at the terminals (a,b) under open circuit conditions
- Generically: can be any voltage source in series with resistance, or any current source in parallel with resistance

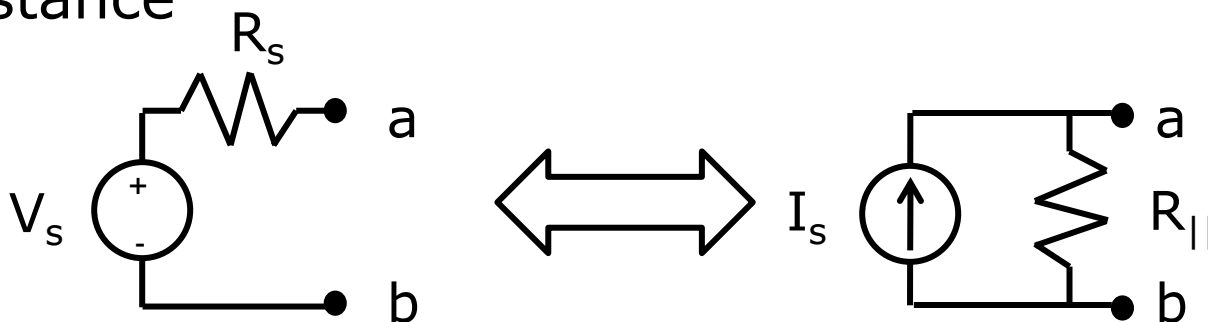



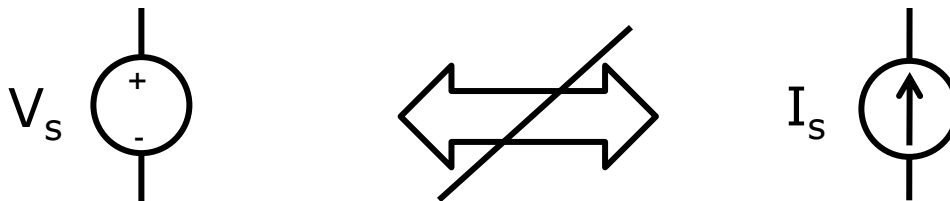
# Source Transformation

- Not possible to transform current (voltage) sources to voltage (current) sources directly



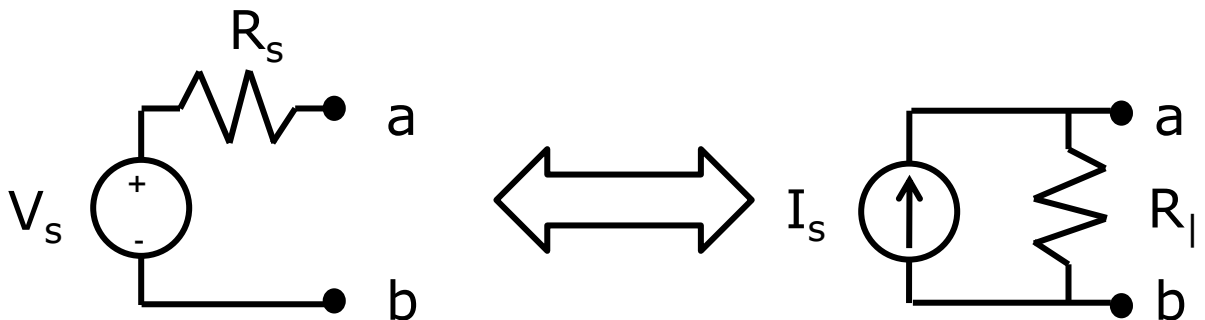- But we can transform sources with series or parallel resistances as seen by terminals








# Source Transformations


- For the two circuits to be equivalent, they must have the same i-v characteristics at their terminals under all external circuit connections
  - Due to linearity, only need to verify i-v characteristics under two different external connections (short, open circuit)
- How are  $V_s$ ,  $I_s$ ,  $R_s$  and  $R_{||}$  related?

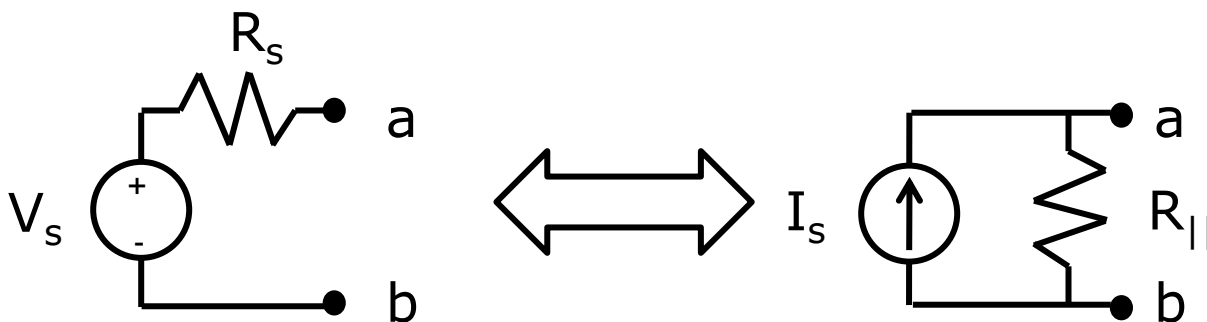


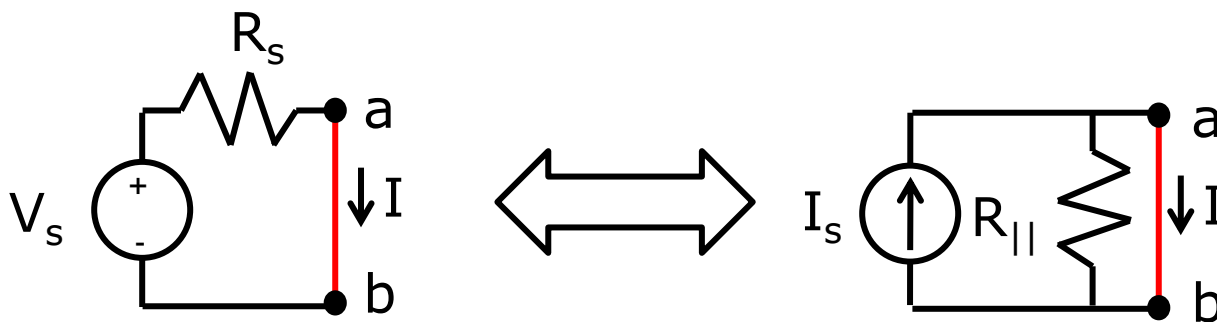
# Source Transformation


- Consider when the external circuit is a short
- Both circuits must have same short current out of their terminals
- $I_{sc} = V_s/R_s$
- $I_{sc} = I_s$
- Therefore:  $I_s = V_s/R_s$





# Source Transformations

- Consider an open circuit
- Both circuits must same open circuit voltage  $V_{oc}$
- $V_{oc} = V_s$
- $V_{oc} = R_{||} I_s$
- Therefore:  $I_s = V_s / R_{||}$

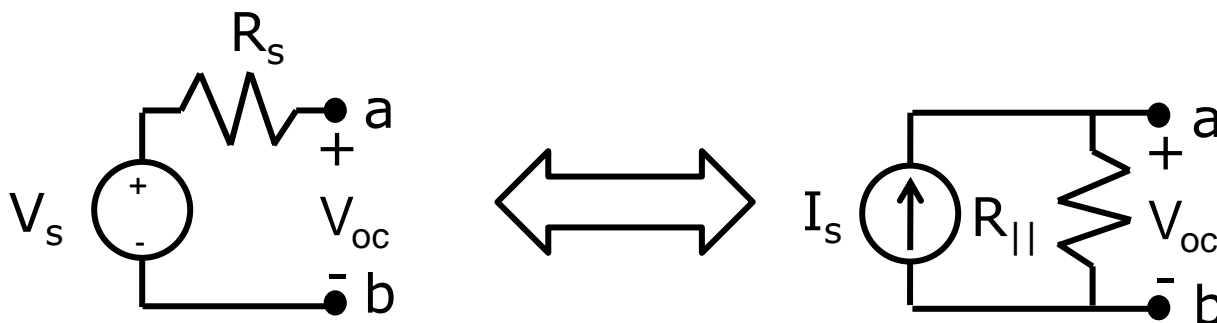



# Source Transformations

- Relationships:

- $I_s = V_s/R_{||}$

- $I_s = V_s/R_s$


- Therefore

- $R_s = R_{||} = R$

- $I_s = V_s/R$

- $V_s = I_s R$

} Source transformation equations

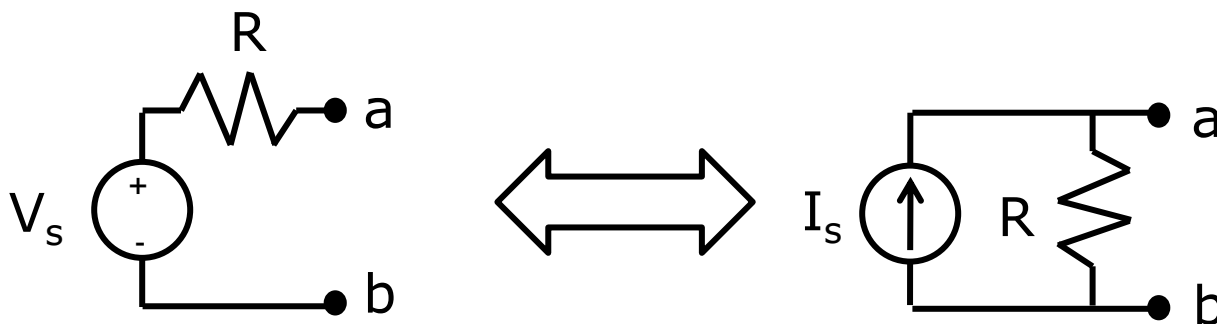





# Source Transformations

- Verify the results hold for Circuit A and Circuit B

Circuit A

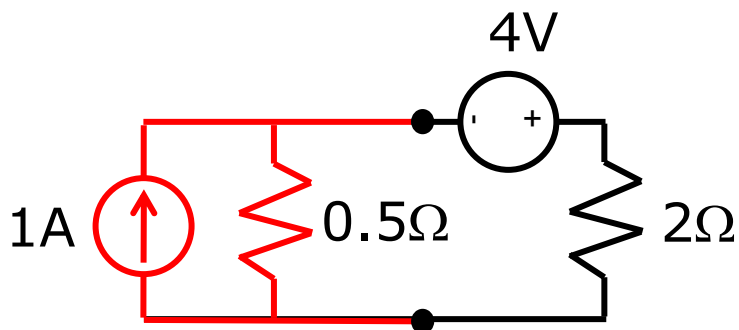


Circuit B

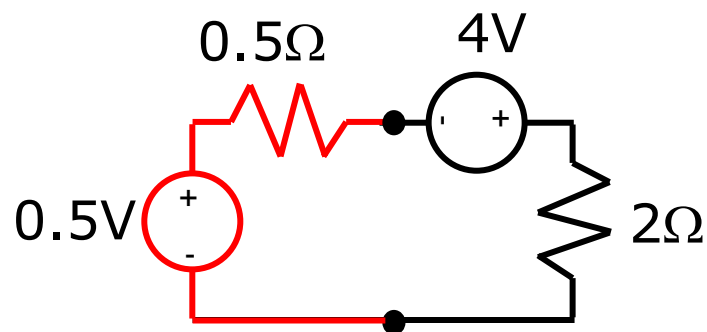


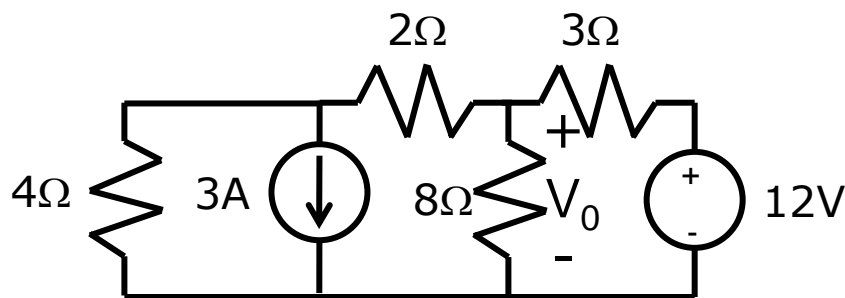
## Example


- Use source transformations to find  $V_0$ 
  - Consider the current source first. Which resistor can we associate it with?
    - $4\Omega$  (they are in parallel)
  - Should we transform them?
    - Yes, the resistor will be in series with the  $2\Omega$  resistor, and we can combine the two




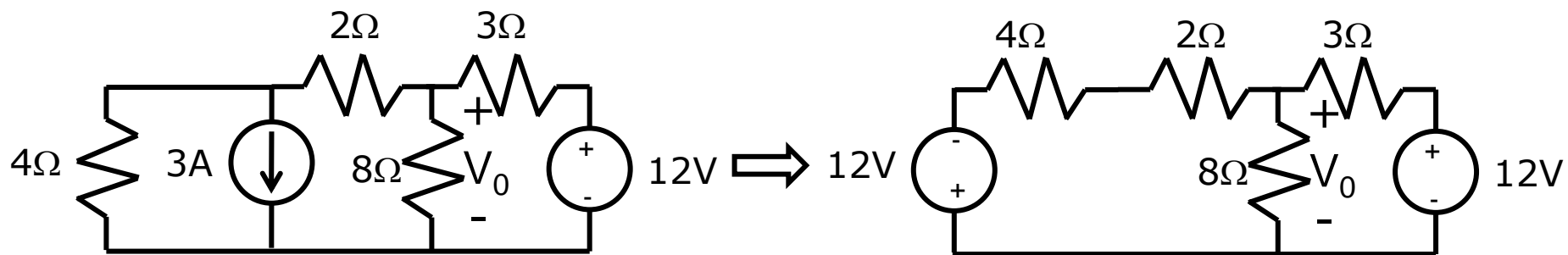
## Example


- Transform the source:
  - $R = 4\Omega$
  - $V_s = I_s R = 3 \times 4 = 12V$
- Pay careful attention to the polarity




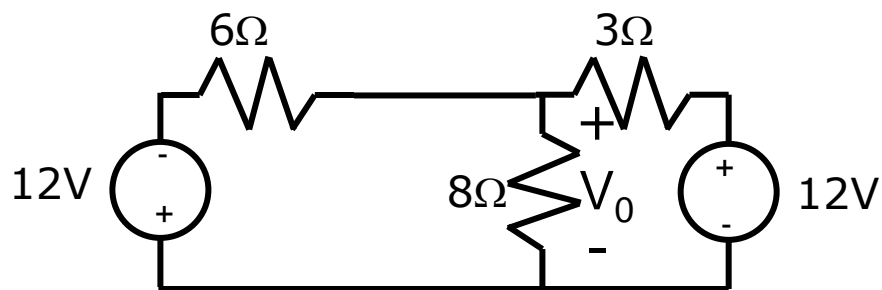
## Example

- Transform the 12V source (on the right), if it is beneficial




After combining series resistance




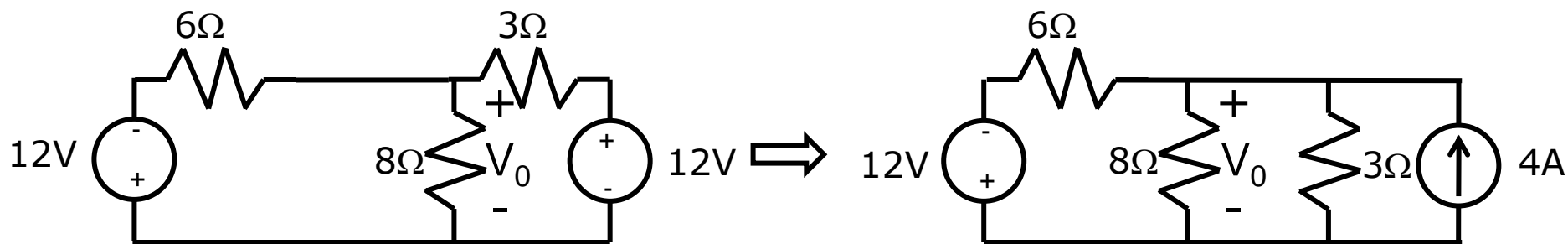
## Example


- Yes, beneficial (results in parallel combination with  $V_0$ ). Combine with  $3\Omega$  resistor to get:
  - $R = 3\Omega$
  - $I_s = V_s/R = 12/3 = 4A$




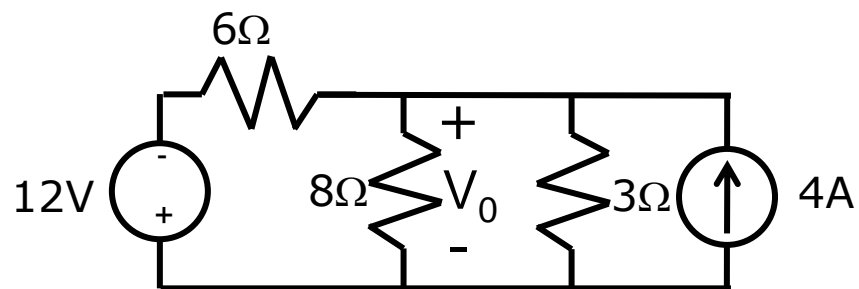
# Example


- Now transform voltage source with  $6\Omega$  resistor




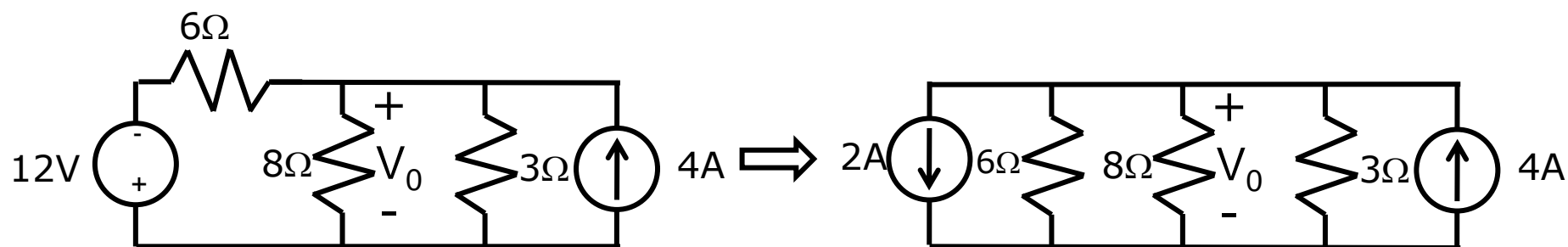
## Example


- Result:
  - $R = 6\Omega$
  - $I_s = V_s/R = 12/6 = 2A$




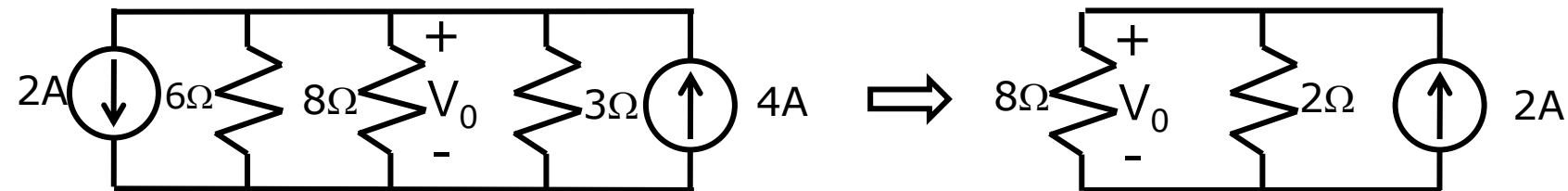
## Example

- The rest is easy.
- Current division:  $I_0 = (4-2) \times (2/10) = 0.4A$
- $V_0 = 3.2V$






# Source Transformations

- Dependent sources are handled using the same procedure
- Be careful


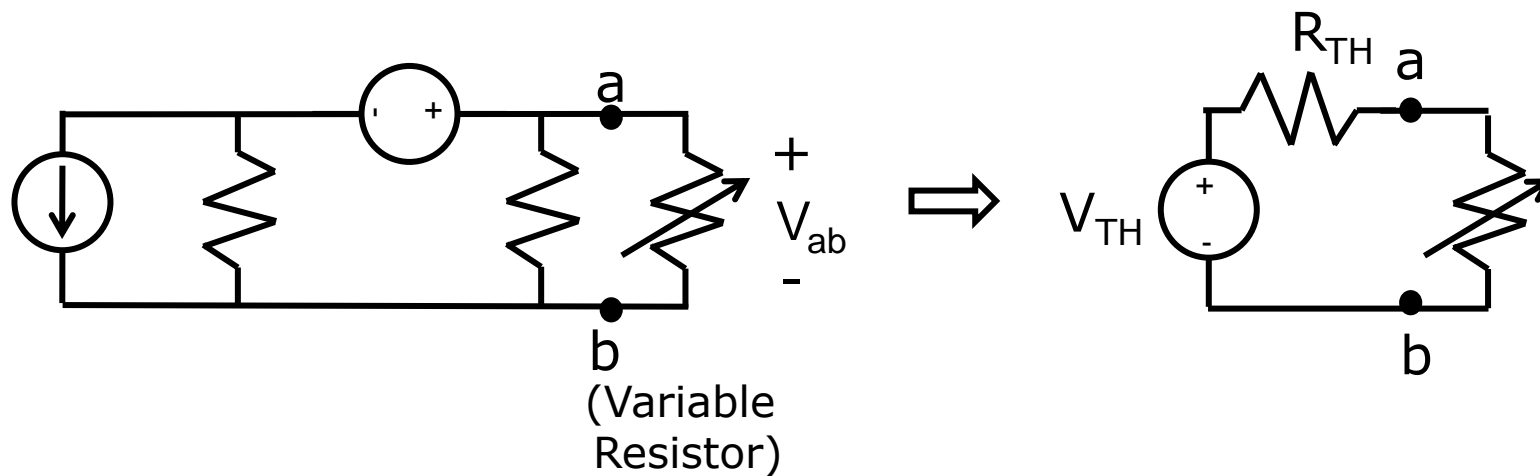
# Thevenin's Theorem


- Often, most elements of a circuit are fixed and only one element (the load) changes
- Do not want to re-solve the entire circuit every time the load changes
- Better approach: represent unchanging part of circuit with voltage source with series resistance




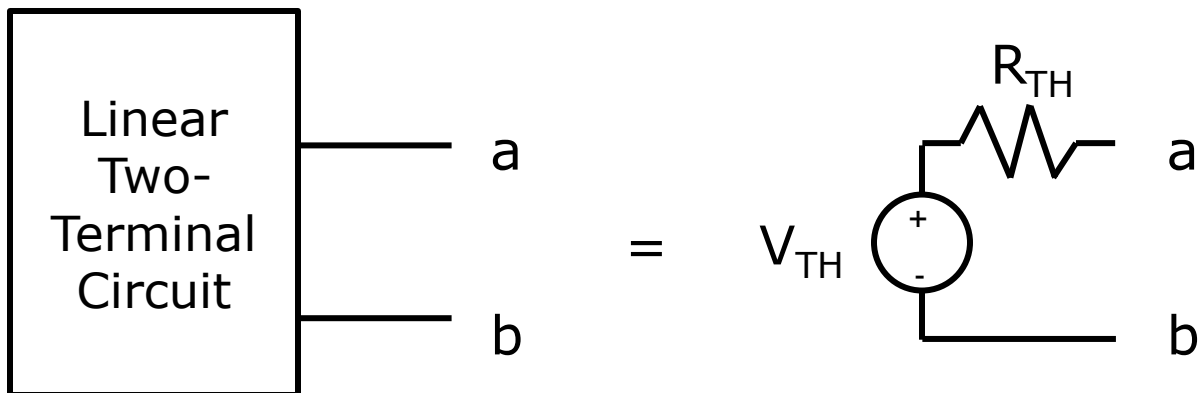
# Thevenin's Theorem



- Thevenin's Theorem: a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source in series with a resistor
- $R_{TH}$ : Thevenin Resistance
- $V_{TH}$ : Thevenin Voltage




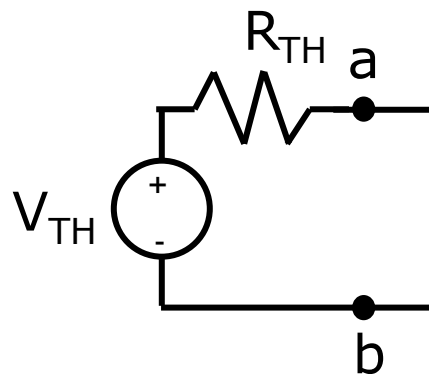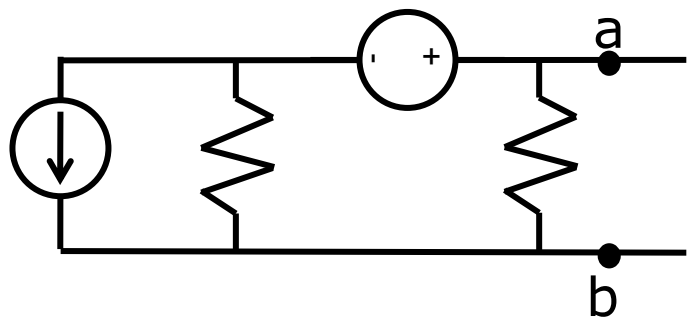
# Thevenin's Theorem

- How do we find  $V_{TH}$  and  $R_{TH}$ ?
- One way: keep applying resistance and source transformations until there is a voltage source in series with a resistance between the terminals








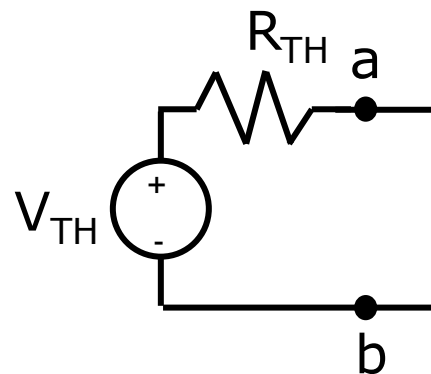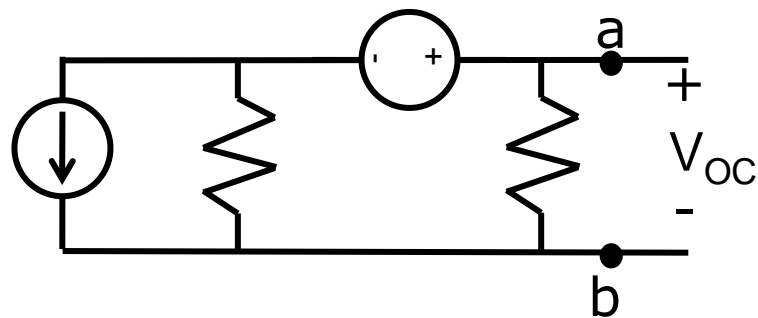
# Thevenin's Theorem

- Better way: recognize that
  - $V_{TH} = V_{OC}$  and
  - $R_{TH}$  = input resistance (looking into terminals a, and b), or  $R_{TH} = V_{OC}/I_{SC}$






# Finding Thevenin Resistance

- No Dependent Sources:
  - short all voltage sources
  - open all current source
  - then find equivalent resistance  $R_{TH} = R_{eq}$
- Dependent Sources:
  - short all voltage sources
  - open all current source
  - Apply test voltage  $V_0$ , compute current  $I_0$
  - $R_{TH} = V_0/I_0$


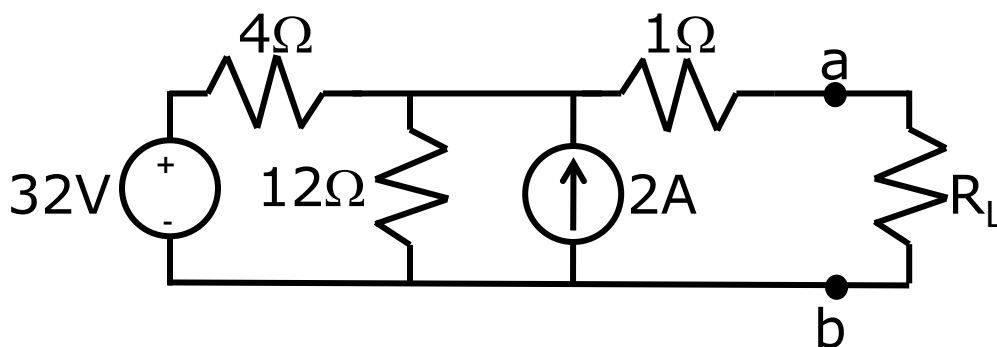
## Example


- Find the current through the load resistor if  $R_L$  is 6, 16 and  $36\Omega$
- Perfect situation for Thevenin Equivalent
  - Find Thevenin Equivalent, then solve equivalent circuit for various values of  $R_L$




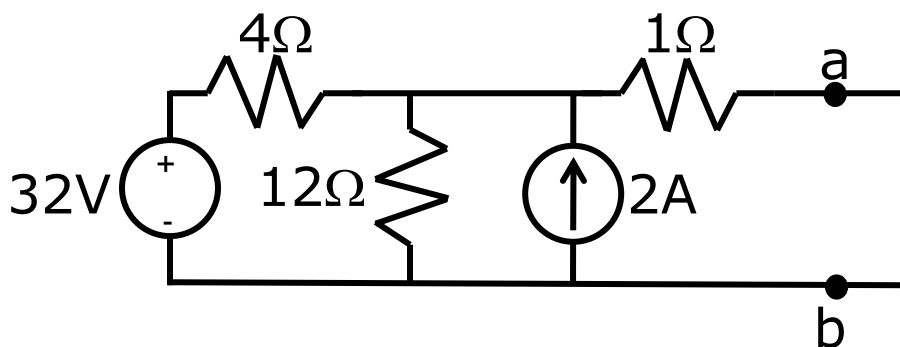
## Example


- Start with finding the Thevenin voltage
  - $V_{TH} = V_{OC}$
- By superposition (or mesh analysis)
  - $V_{OC1} = 32(12/16) = 24V$
  - $V_{OC2} = 4 \times 2 \times (12/16) = 6V$
  - $V_{TH} = V_{OC1} + V_{OC2} = 30V$




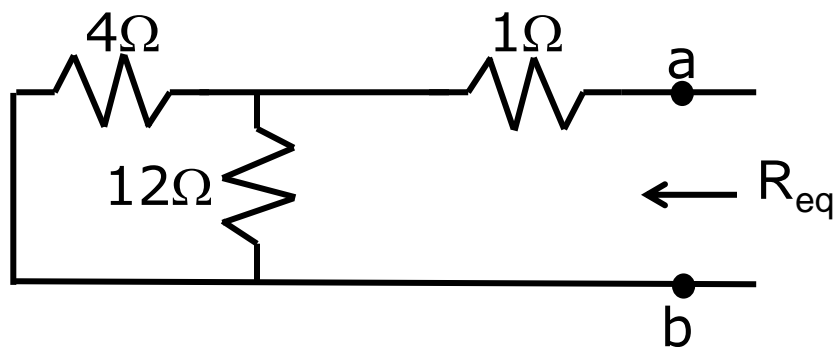
# Example


- Now find the Thevenin resistance
  - $R_{TH} = R_{eq}$
  - deactivate all sources
  - $R_{eq} = 1 + (4 \times 12) / 16 = 4 \Omega$




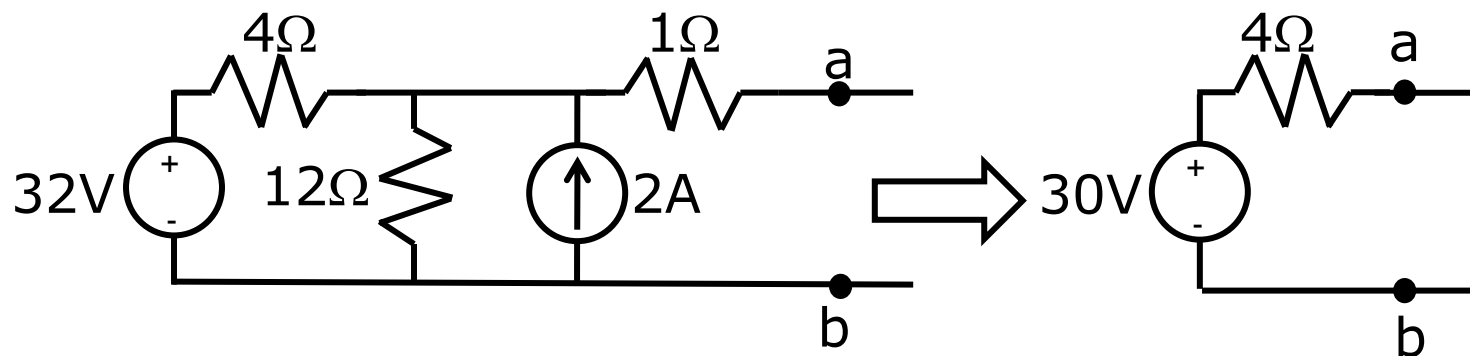
## Example


- Thevenin equivalent circuit is shown below
- Current through various load resistances can be easily computed




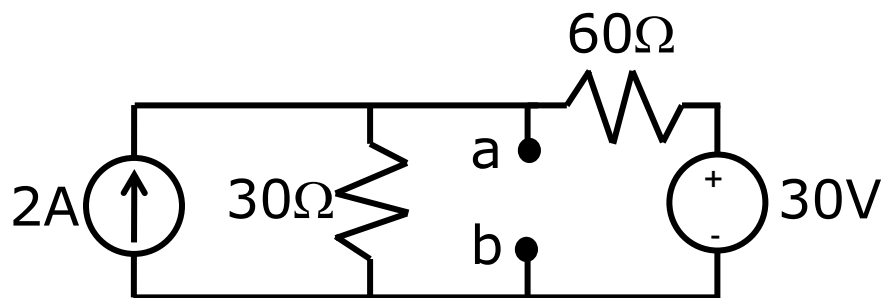
## Example


- Find the Thevenin Equivalent of the circuit between the terminals a, b




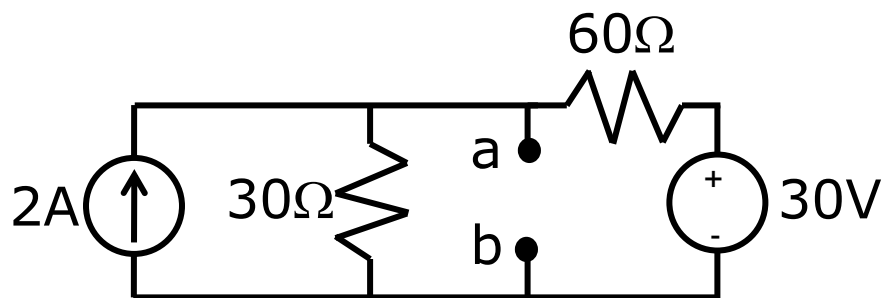
## Example

- Via superposition
  - $V_{OC1} = 30 \times (30/90) = 10V$
  - $V_{OC2} = 30 \times 2(60/90) = 40V$
- $V_{TH} = V_{OC1} + V_{OC2} = 50V$







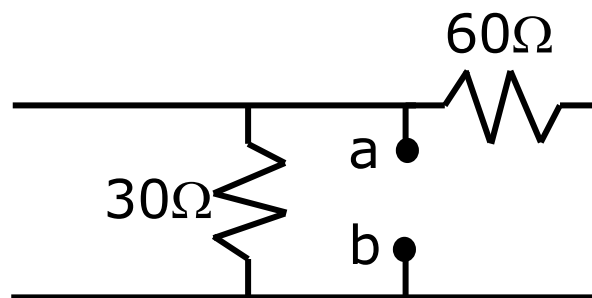
## Example


- Now find  $R_{TH}$ 
  - $R_{TH} = (30 \times 60) / (30 + 60) = 20 \Omega$




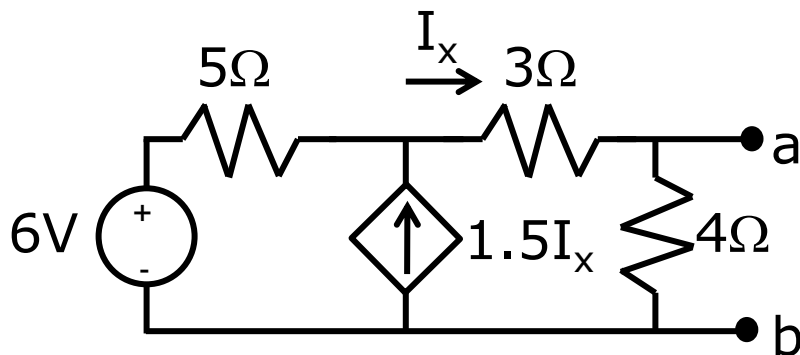
# Thevenin's Theorem

- Find the Thevenin equivalent
  - Note the dependent source
- Finding  $V_{TH}$  is the same procedure as before





# Thevenin's Theorem


- Mesh Analysis
  - $6 = 5I_1 + 7I_x$  (Supermesh)
  - $1.5I_x + I_1 = I_x$  (current source constraint equation)

Solving...

$$I_x = 1.33A$$

Therefore

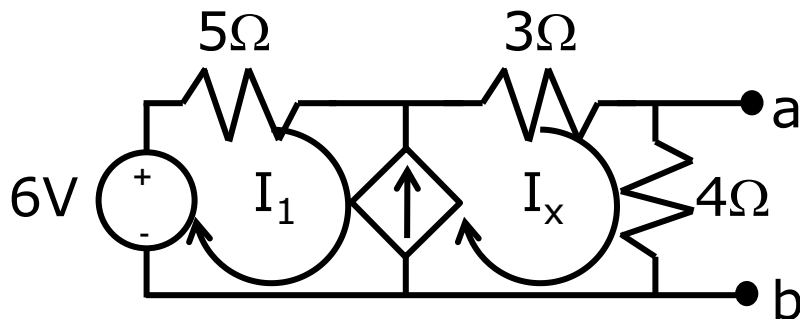
$$V_{OC} = 1.33 \times 4 = 5.33V = V_{TH}$$




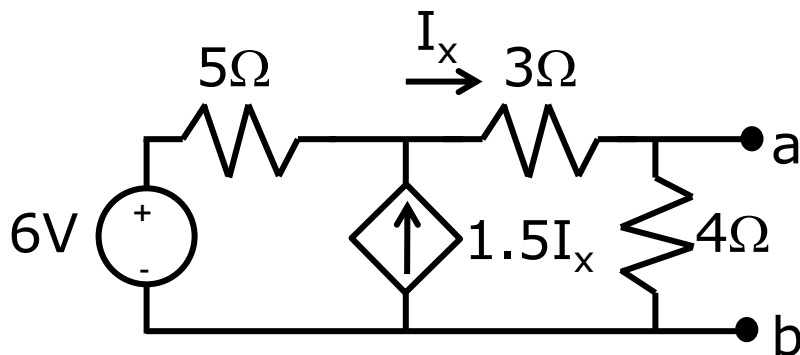
# Thevenin's Theorem


- To find  $R_{TH}$ 
  - apply either test voltage or current to the terminals
  - deactivate independent sources
  - compute either terminal current or voltage
  - $R_{TH} = V_0/I_0$




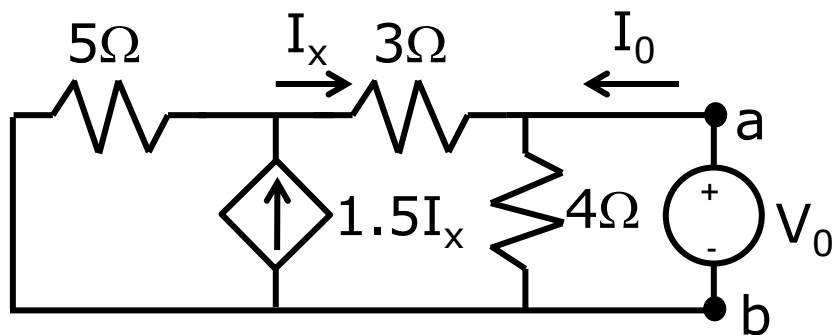
# Thevenin's Theorem


- Apply a test voltage  $V_0$
- Let  $V_0 = 1V$
- Now find  $I_0$  (note polarity if  $I_0$ )




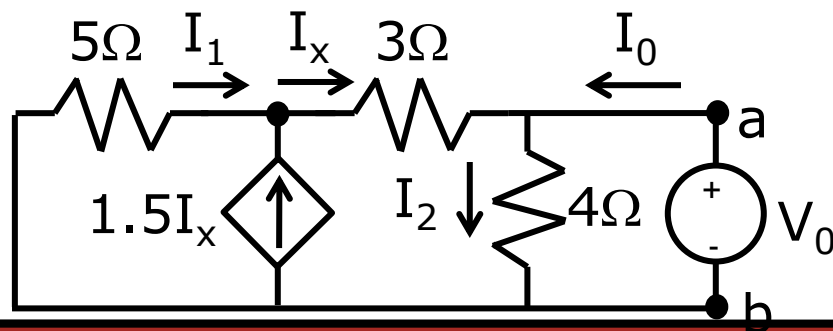
# Thevenin's Theorem


- $I_1 + 1.5I_x = I_x$  (Nodal Analysis)
  - $I_1 + 0.5I_x = 0$
  - $-0.2V_1 + 0.5(V_1 - 1)/3 = 0$
  - $-0.0333V_1 - 0.16667 = 0$
  - $V_1 = -5V$
  - $I_x = -2A$  (Ohm's Law)
  - $I_2 = 0.25A$  (Ohm's Law)
  - $I_0 = 2.25A$  (KCL)




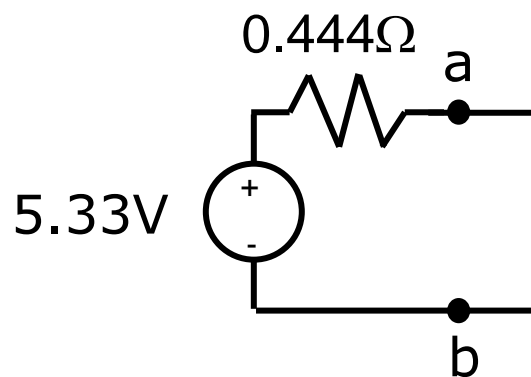
# Thevenin's Theorem

- Therefore  $R_{TH} = V_0/I_0 = 1/2.25 = 0.444\Omega$








# Norton's Theorem

- Thevenin equivalent circuit can be transformed into current source in parallel with a resistor
- From discussion on source transformation:
  - $R_N = R_{TH}$

Thevenin Equivalent

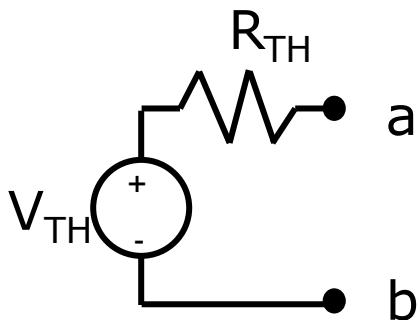

Norton Equivalent

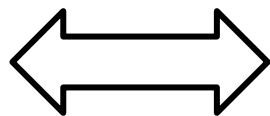
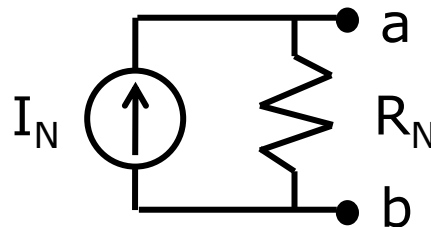





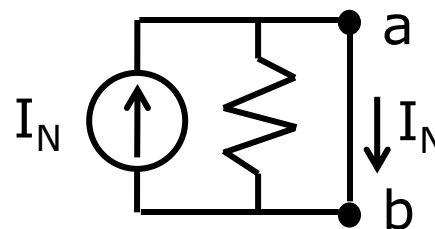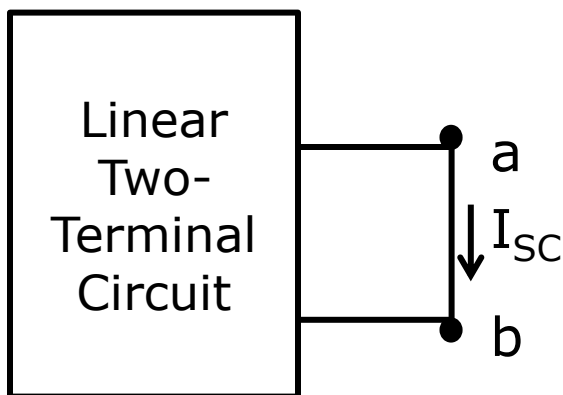
# Norton's Theorem

- $I_N$  is found by shorting the terminals of the circuit
  - $I_N = I_{SC}$







# Norton's Theorem

- Process for finding  $R_{TH}$  is identical to that for Thevenin's theorem
- No Dependent Sources:
  - short all voltage sources
  - open all current source
  - then find equivalent resistance  $R_{TH} = R_{eq}$
- Dependent Sources:
  - short all voltage sources
  - open all current source
  - Apply test voltage  $V_0$  (or current), compute current  $I_0$  (or voltage)
  - $R_{TH} = V_0/I_0$



# Practical Sources

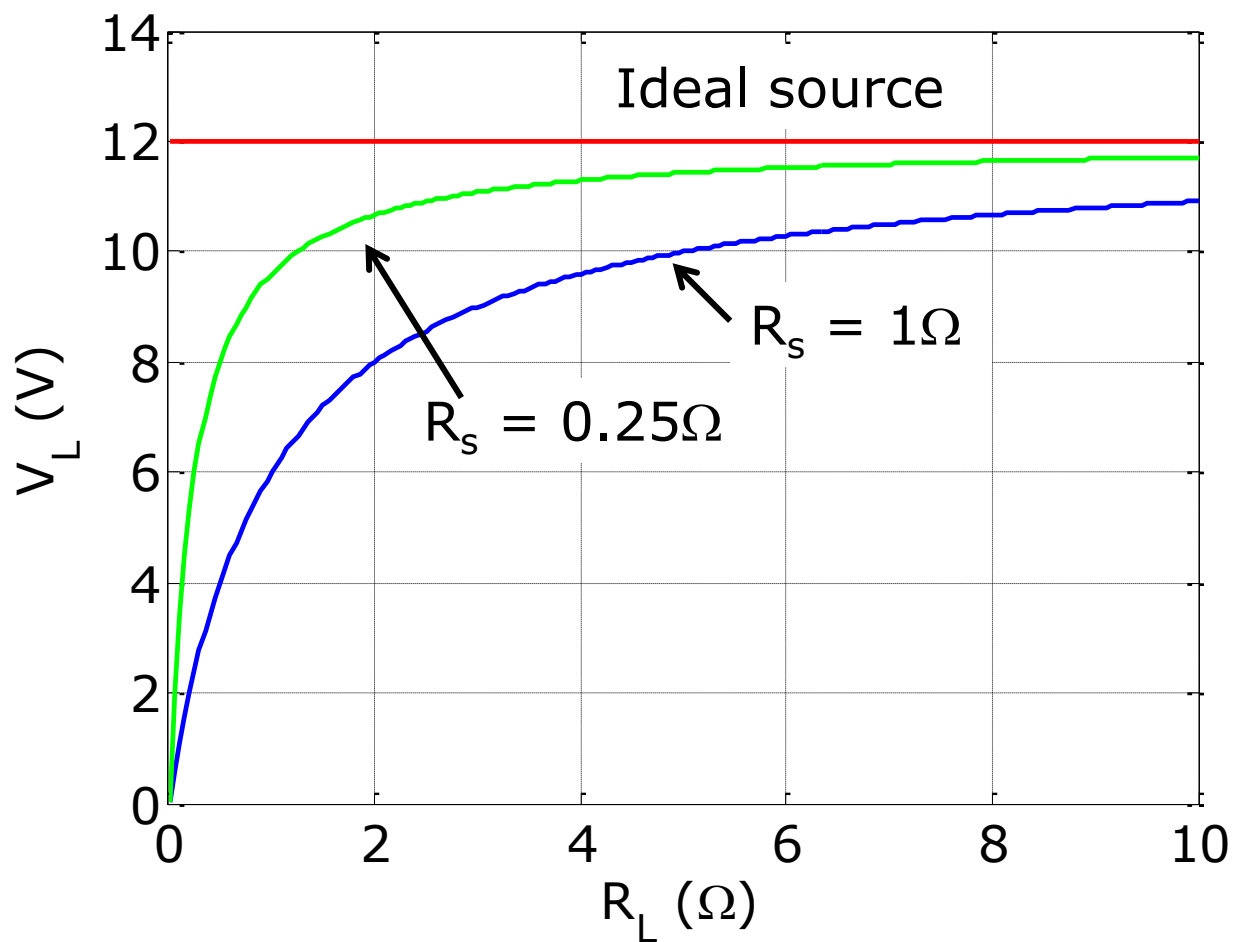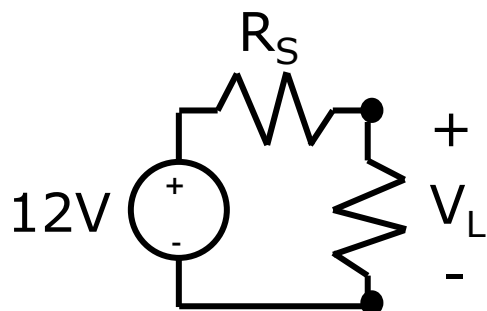



# Practical Sources

