

11-Multiplexers, Decoders, Encoders and Read-Only Memory

Text: Unit 9

ECEGR/ISSC 201
Digital Operations and Computations
Winter 2011



Overview

- Multiplexers
- Three-State Buffers
- Decoders/Encoders
- Read Only Memory

Dr. Louie

2



Introduction

- Basic building blocks have been discussed thus far: NOT, AND, OR, NOR, NAND, etc gates
- Often, multiple gates are available in single integrated circuits
- We will next study some common types of these ICs

Dr. Louie

3



Introduction

- Nomenclature
 - Small scale integrated (SSI): NAND, NOR, NOT, AND, OR and Flip-Flops
 - Medium scale integrated (MSI): adders, multiplexers, decoders, registers, etc
 - Large scale integration (LSI): 12-100 gates
 - Very Large Scale Integration (VLSI): 100-1000s of gates

Dr. Louie

4



Multiplexers (MUX)

- A data selector
 - Data inputs
 - Control input(s)
- Acts as a multi-pole switch
- Example: source selection in a home stereo
- Widespread use in telecommunications


Dr. Louie

5



Multiplexers (MUX)

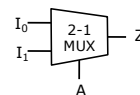- Acts as a multi-pole switch
- Example 2-to-1 MUX



Dr. Louie

6

Multiplexers (MUX)

- If $A = 0$, then $Z = I_0$
- If $A = 1$, then $Z = I_1$
- $Z = A'I_0 + AI_1$

Dr. Louie 7

Multiplexers (MUX)

- In a 4-to-1 MUX, 2 control signals are needed, A and B
- $Z = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$
- Other MUXs are possible
 - 8-to-1
 - 2^n -to-1

Dr. Louie 8

Example

- Write equation describing the operation of an 8-to-1 MUX
- $Z = ?$

Dr. Louie 9

Example

- Write equation describing the operation of an 8-to-1 MUX
- $Z = A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3 + ABC'I_4 + ABCI_5 + ABC'I_6 + ABCI_7$
- What is the output when $A = B = 0, C = 1$?

Dr. Louie 10

Example

- Write equation describing the operation of an 8-to-1 MUX
- $Z = A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3 + ABC'I_4 + ABCI_5 + ABC'I_6 + ABCI_7$
- What is the output when $A = B = 0, C = 1$?
 - $Z = I_1$

Dr. Louie 11

Multiplexers (MUX)

- Internal gates of a 4-to-1 MUX

Dr. Louie 12

Multiplexers (MUX)

- MUXs are often used to select multi-bit words from a single control signal

Dr. Louie 13

Multiplexers (MUX)

- If $A = 0$, then the output word is $X_0X_1X_2X_3$

Dr. Louie 14

Multiplexers (MUX)

- Bus representation

Often, a single thick line is used to indicate a bus

Dr. Louie 15

Multiplexers (MUX)

Dr. Louie 16

Multiplexers (MUX)


Dr. Louie 17


Buffers

- Complications can arise when the output of a gate is connected to several devices

Dr. Louie 18

Buffers

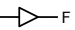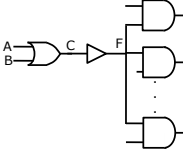
- Solution: use a buffer (non-inverting)
- $F = C$ 



Dr. Louie 19

Three-State Buffers

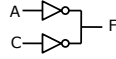
- Consider the case in which the output of two gates are tied together
- Develop the truth table for F



Dr. Louie 20

Three-State Buffers

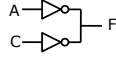- Conflicts occur when A and C are not the same
- An unknown value (X) occurs
- How do we prevent this?



A	C	F
0	0	1
0	1	(X)
1	0	(X)
1	1	0

Dr. Louie 21



Three-State Buffers

- Complications can arise when the outputs of two or more logic gates are connected together
- Voltage levels can vary resulting in indeterminate values (not 0, not 1)
- Solution: use three-state buffers

Dr. Louie 22

Three-State Buffers


- Three-state buffer
 - When $B = 1$; $C = A$
 - When $B = 0$; C acts as an open circuit (Hi Z)
- Open circuit: no flow of current

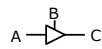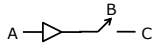
Dr. Louie 23

Three-State Buffers

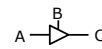
- Truth tables for various types of buffers




B	A	C
0	0	Z
0	1	Z
1	0	0
1	1	1

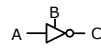

B	A	C
0	0	Z
0	1	Z
1	0	1
1	1	0

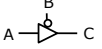

B	A	C
0	0	0
0	1	1
1	0	Z
1	1	Z

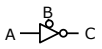

B	A	C
0	0	1
0	1	0
1	0	Z
1	1	Z

Dr. Louie 24

Three-State Buffers

- Analyze the following circuit
- Two, three-state buffers controlled by B
- Coupled output D

Dr. Louie 25

Three-State Buffers

- When B = 0, what is D?
 - Top behaves as a non-inverting buffer, so D = A
 - Bottom state is Hi-Z, so C is not fed through

Dr. Louie 26

Three-State Buffers

- When B = 1, what is D?
 - Top state is Hi-Z, so A is not fed through to D
 - Bottom behaves as a non-inverting buffer, so D = C

Dr. Louie 27

Three-State Buffers

- When B = 0, D = A
- When B = 1, D = C
- What does this type of operation remind you of?

Dr. Louie 28

Three-State Buffers

- A 2-to-1 MUX!

Dr. Louie 29

Three-State Buffers

- Three-state buffers are also used in ICs with bi-directional pins (same pin can be used for input or output)

Dr. Louie 30


Decoders and Encoders

- We have used decoders and encoders in the labs
- What do they do?

Dr. Louie 31

Decoders

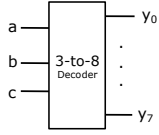- Decoders are a commonly used type of IC
- Decodes n-bit input code into m-bit output code



Dr. Louie 32

Decoders

- There may be unused input combinations
- We discuss "Line Decoders"
- Outputs minterms based on inputs

Dr. Louie 33

Decoders


- A simple 1-to-2 decoder
 - 1 input: A
 - 2 outputs: D_0 and D_1
- Assume we want the outputs to behave according to the following truth table
- How can we build this?

A	D_0	D_1
0	1	0
1	0	1

Dr. Louie 34

Decoders

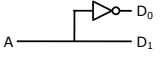- A simple 1-to-2 decoder
 - 1 input: A
 - 2 outputs: D_0 and D_1



A	D_0	D_1
0	1	0
1	0	1

Dr. Louie 35

Decoders

- Assume that we have a system that accepts input binary numbers between 0 and 3
- Want to light four different colored bulbs depending on the input value
 - If input is 0, red bulb lights
 - If input is 1, yellow bulb lights
 - If input is 2, blue bulb lights
 - If input is 3, green bulb lights
- Design the decoder

Dr. Louie 36

Decoder

- Assign
 - If input is 0, red bulb =>D₀
 - If input is 1, yellow bulb =>D₁
 - If input is 2, blue bulb =>D₂
 - If input is 3, green bulb =>D₃

A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Dr. Louie 37

Decoders

- 3-to-8 decoder

a	b	c	Y ₀	Y ₁	Y ₂	Y ₃	Y ₄	Y ₅	Y ₆	Y ₇
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

The remaining entries are 0

Dr. Louie 38

Decoders

- A general n-to-2ⁿ decoder generates all 2ⁿ minterms (or maxterms) of the n input variables
 - y_i = m_i for i = 0 to 2ⁿ - 1 (noninverted outputs)
 - y_i = m_i' = M_i for i = 0 to 2ⁿ - 1 (inverted outputs)

Dr. Louie 39

Encoders

- Encoders perform the opposite function as a decoder
- Outputs generate binary code corresponding to input

Dr. Louie 40

Encoders

- Octal-to-Binary Encoder

Dr. Louie 41

Encoders

- Octal-to-Binary Encoder
- Write the equations for a, b and c

Dr. Louie 42

Encoders

- Octal-to-Binary Encoder
- Write the equations for a, b and c
 - $a = Y_4 + Y_5 + Y_6 + Y_7$
 - $b = Y_2 + Y_3 + Y_6 + Y_7$
 - $c = Y_1 + Y_3 + Y_5 + Y_7$

Dr. Louie 43

Encoders

- Priority Encoder: if more than one input is 1, the most significant 1 takes precedent
- V: valid output indicator, needed to distinguish all 0 input from all 0 input except D₀

D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

Dr. Louie 44

Read-Only Memories

- Read-Only Memory (ROM): array of semiconductor devices that are interconnected to store an array of binary data
- Data can be read, but it cannot be changed (easily)
- Non-volatile

Dr. Louie 45

Read-Only Memories

- Consider ROM that holds 8, 4-bit words
- Each of the 8 words has a unique address (example: 000, 110, 111, etc.)
- Need three input lines to select an address (a, b, c)
- Four output lines (one for each word bit)

Dr. Louie 46

Read-Only Memories

- Truth Table

A	B	C	F ₀	F ₁	F ₂	F ₃
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

DATA

Dr. Louie 47

Example

- What is the output word if A = B = 1, C = 0?

A	B	C	F ₀	F ₁	F ₂	F ₃
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

Dr. Louie 48

Example

- What is the output word if A = B = 1, C = 0?
- 1111

A	B	C	F ₀	F ₁	F ₂	F ₃
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

Dr. Louie 49

Example

- Design (determine the number of inputs and outputs) for a 256-word, 16 bit ROM

Dr. Louie 50

Example

- Design (determine the number of inputs and outputs) for a 256-word, 16 bit ROM
- Inputs $2^x = 256 \Rightarrow x = 8$
- Outputs 16

Dr. Louie 51

Read-Only Memory

- Basic components of a ROM are a decoder and memory array

Dr. Louie 52

Read-Only Memory




Dr. Louie 53

Example

- Draw the switching elements on the ROM to realize the following truth table

A	B	C	F ₀	F ₁	F ₂	F ₃
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

Dr. Louie 54

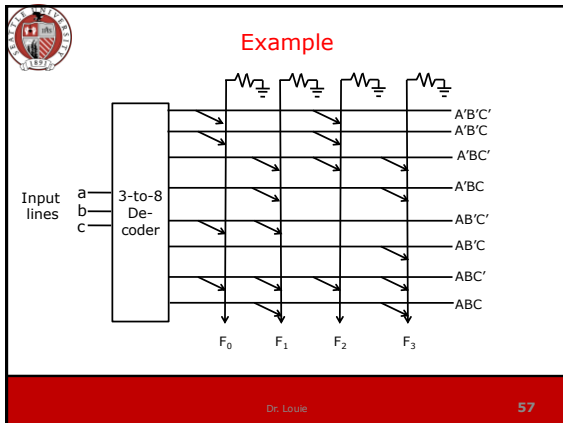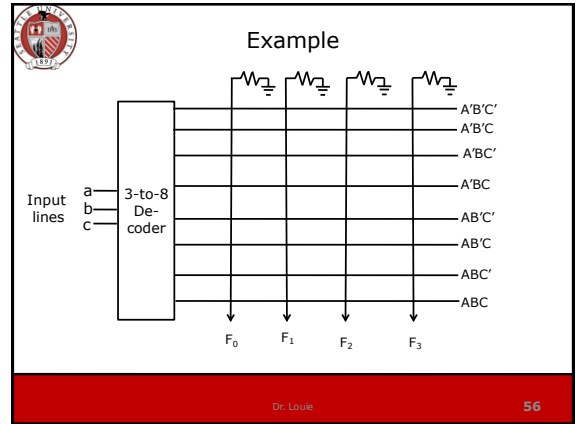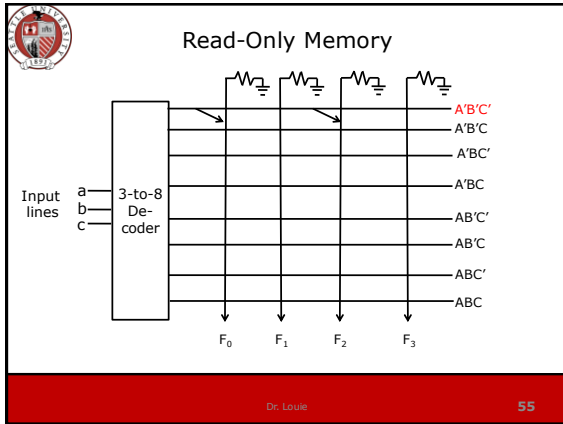

- Read-Only Memory**
- Common Types of ROM
 - Mask-Programmable ROMs
 - Programmable ROMs (PROMs)
 - Electrically erasable programmable ROMs (EEPROMs)
- Dr. Louie 58

- Read-Only Memory**
- Mask-Programmable ROMs
 - Data is permanently stored at time of manufacture
 - A special mask is required, which is expensive
 - Usually selected if several thousand duplicates are used
- Dr. Louie 59

- Read-Only Memory**
- Electrically erasable programmable ROMs (EEPROMs)
 - Allows for the ROM data to be erased and new data stored
 - Used in developmental stages of a digital system
 - Similar to flash memory, but there is a different underlying mechanism
- Dr. Louie 60