

11-Transmission Line Models Part 2

Text: 4.4-4.5

ECEGR 451
Power Systems

Dr. Henry Louie

1

Overview

- Transmission Line Matrix
- Long Line Model
- Medium Line Model
- Short Line Model

Dr. Henry Louie

2

Transmission Matrix

$$\left. \begin{aligned} \mathbf{V}_1 &= \mathbf{V}_2 \cosh \gamma X + \mathbf{Z}_c \mathbf{I}_2 \sinh \gamma X \\ \mathbf{I}_1 &= \frac{\mathbf{V}_2}{\mathbf{Z}_c} \sinh \gamma X + \mathbf{I}_2 \cosh \gamma X \end{aligned} \right\} \text{General solution for distributed impedance line}$$

Can be expressed in the form

$$\mathbf{V}_1 = \mathbf{A}\mathbf{V}_2 + \mathbf{B}\mathbf{I}_2$$

$$\mathbf{I}_1 = \mathbf{C}\mathbf{V}_2 + \mathbf{D}\mathbf{I}_2$$

Where:

$$\left. \begin{aligned} \mathbf{A} &= \cosh \gamma X & \mathbf{C} &= \frac{1}{\mathbf{Z}_c} \sinh \gamma X \\ \mathbf{B} &= \mathbf{Z}_c \sinh \gamma X & \mathbf{D} &= \cosh \gamma X \end{aligned} \right\} \text{transmission parameters}$$

Dr. Henry Louie

3


Transmission Matrix

- Transmission matrix:

$$\mathbf{T} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix}$$

- The sending and receiving end voltages and currents are concisely related as:
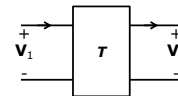
$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \mathbf{T} \begin{bmatrix} \mathbf{V}_2 \\ \mathbf{I}_2 \end{bmatrix}$$



Dr. Henry Louie

4

Example

Write the transmission matrix for a transmission line with the following parameters:

$$\mathbf{z} = 0.8431 \angle 79.04^\circ \Omega/\text{mi}$$

$$\mathbf{y} = 5.105 \times 10^{-6} \angle 90^\circ \text{ S/mi}$$

$$X = 230 \text{ miles}$$

$$\text{Hint: } \gamma \triangleq \mathbf{yz}^{1/2}$$

$$\mathbf{Z}_c = \sqrt{\frac{\mathbf{z}}{\mathbf{y}}}$$

Dr. Henry Louie

5

Example

Write the transmission matrix for a transmission line with the following parameters:

$$\mathbf{z} = 0.8431 \angle 79.04^\circ \Omega/\text{mi}$$

$$\mathbf{y} = 5.105 \times 10^{-6} \angle 90^\circ \text{ S/mi}$$

$$\gamma = \mathbf{yz}^{1/2} = 0.0002 + j0.0021$$

$$\mathbf{Z}_c = \sqrt{\frac{\mathbf{z}}{\mathbf{y}}} = 404.5 - j38.8$$

$$\mathbf{A} = \mathbf{D} = 0.8902 + j0.0208$$

$$\mathbf{B} = 34.16 + j183.62$$

$$\mathbf{C} = -0.0000 + j0.0011$$

Dr. Henry Louie

6

Example

- Verify on your own that if

$$\mathbf{V}_2 = \frac{215,000}{\sqrt{3}} = 124,130 \angle 0^\circ \text{ V}$$

$$\mathbf{I}_2 = \frac{125,000,000}{3 \cdot 124,130} = 335.7 \angle 0^\circ \text{ A}$$
 then

$$\mathbf{V}_1 = 137,860 \angle 27.77^\circ \text{ V}$$

$$\mathbf{I}_1 = 332.31 \angle 26.33^\circ \text{ A}$$
 see previous lecture notes

7

Transmission Matrix

- If sending end voltage and current are known, the receiving end quantities can be computed using:

$$T^{-1} = \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \quad \text{inverse transmission matrix}$$

$$T^{-1} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{V}_2 \\ \mathbf{I}_2 \end{bmatrix}$$

8

Transmission Matrix

- Multiple transmission line segments can be accounted for using:

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = T_1 \begin{bmatrix} \mathbf{V}_2 \\ \mathbf{I}_2 \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{V}_2 \\ \mathbf{I}_2 \end{bmatrix} = T_2 \begin{bmatrix} \mathbf{V}_3 \\ \mathbf{I}_3 \end{bmatrix}$$
 via substitution:

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = T_1 T_2 \begin{bmatrix} \mathbf{V}_3 \\ \mathbf{I}_3 \end{bmatrix}$$

9

Lumped-Circuit Equivalent

- Another useful form of transmission model is the Lumped-circuit equivalent
 - Yields same result as transmission matrix, and general solution (i.e. not an approximation)

10

Lumped-Circuit Equivalent

- Approach: map \mathbf{Y}' and \mathbf{Z}' to A, B, C and D
- Next map A, B, C, D to \mathbf{y} and \mathbf{z} (already done)
- Express \mathbf{Y}' and \mathbf{Z}' in terms of \mathbf{y} and \mathbf{z} (approximation is introduced here)

11

Lumped-Circuit Equivalent

- Equivalent A,B,C,D parameters
- Solving the circuit for $\mathbf{V}_1, \mathbf{I}_1$:


$$\mathbf{V}_1 = \mathbf{V}_2 + \mathbf{Z}' \left(\mathbf{I}_2 + \frac{\mathbf{Y}'}{2} \mathbf{V}_2 \right)$$

$$= \left(1 + \frac{\mathbf{Z}' \mathbf{Y}'}{2} \right) \mathbf{V}_2 + \mathbf{Z}' \mathbf{I}_2$$

$$\mathbf{I}_1 = \frac{\mathbf{Y}'}{2} \mathbf{V}_1 + \frac{\mathbf{Y}'}{2} \mathbf{V}_2 + \mathbf{I}_2$$

$$= \mathbf{Y}' \left(1 + \frac{\mathbf{Z}' \mathbf{Y}'}{4} \right) \mathbf{V}_2 + \left(1 + \frac{\mathbf{Z}' \mathbf{Y}'}{2} \right) \mathbf{I}_2$$

12



Lumped-Circuit Equivalent

- Desired form

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ \mathbf{I}_2 \end{bmatrix}$$
- We then have


$$\mathbf{V}_1 = \left(1 + \frac{\mathbf{Z}'\mathbf{Y}'}{2}\right)\mathbf{V}_2 + \mathbf{Z}'\mathbf{I}_2$$

$$\mathbf{I}_1 = \mathbf{Y}'\left(1 + \frac{\mathbf{Z}'\mathbf{Y}'}{4}\right)\mathbf{V}_2 + \left(1 + \frac{\mathbf{Z}'\mathbf{Y}'}{2}\right)\mathbf{I}_2$$

$$\mathbf{A} = 1 + \frac{\mathbf{Z}'\mathbf{Y}'}{2} \quad \mathbf{B} = \mathbf{Z}'$$

$$\mathbf{C} = \mathbf{Y}'\left(1 + \frac{\mathbf{Z}'\mathbf{Y}'}{4}\right) \quad \mathbf{D} = 1 + \frac{\mathbf{Z}'\mathbf{Y}'}{2}$$

Dr. Henry Louie 13



Lumped-Circuit Equivalent

- Next determine \mathbf{Y}' and \mathbf{Z}' in terms of \mathbf{y} , \mathbf{z} (or \mathbf{Z}_c and γ)
- Start with B


$$\mathbf{B} = \mathbf{Z}_c \sinh \gamma X$$
 from the lumped equivalent circuit

$$\mathbf{B} = \mathbf{Z}$$
 therefore:

$$\mathbf{Z}' = \mathbf{Z}_c \sinh \gamma X = \sqrt{\frac{\mathbf{z}}{\mathbf{y}}} \sinh \gamma X = \mathbf{z} X \frac{\sinh \gamma X}{\gamma X}$$

$$= \mathbf{z} \frac{\sinh \gamma X}{\gamma X} \quad \text{defining } \mathbf{Z} \triangleq \mathbf{z} X$$

Dr. Henry Louie 14



Lumped-Circuit Equivalent

- We note that usually:

$$|\gamma| \ll 1$$
- therefore:

$$\frac{\sinh \gamma X}{\gamma X} \approx 1$$
 and


$$\mathbf{Z}' = \mathbf{z} \frac{\sinh \gamma X}{\gamma X}$$

$$\mathbf{Z}' \approx \mathbf{z}$$

remember, this is an approximation!
we will see later when it is appropriate to use

↙ correction factor

Dr. Henry Louie 15



Lumped-Circuit Equivalent


- Now find \mathbf{Y}'
- Let's look at A

$$\mathbf{A} = 1 + \frac{\mathbf{Z}'\mathbf{Y}'}{2} = 1 + \frac{\mathbf{Z}_c \sinh \gamma X \mathbf{Y}'}{2}$$

$$\mathbf{A} = \cosh \gamma X \quad \text{from the distributed model}$$
- Solving

$$\frac{\mathbf{Y}'}{2} = \frac{\cosh \gamma X - 1}{\mathbf{Z}_c \sinh \gamma X} = \frac{1}{\mathbf{Z}_c} \tanh\left(\frac{\gamma X}{2}\right)$$

Dr. Henry Louie 16



Lumped-Circuit Equivalent


- We can also write

$$\frac{1}{\mathbf{Z}_c} = \frac{1}{\sqrt{\mathbf{z}/\mathbf{y}}} = \frac{\mathbf{y}}{\sqrt{\mathbf{z}\mathbf{y}}} = \frac{\mathbf{y}X}{\gamma X} = \frac{\mathbf{Y}}{\gamma X} \quad \text{where } \mathbf{Y} \triangleq \mathbf{y}X$$
- So that $\frac{\mathbf{Y}'}{2} = \frac{1}{\mathbf{Z}_c} \tanh\left(\frac{\gamma X}{2}\right)$ becomes $\frac{\mathbf{Y}'}{2} = \frac{\mathbf{Y}}{2} \frac{\tanh\left(\frac{\gamma X}{2}\right)}{\gamma X/2}$
- Usually, for transmission lines $|\gamma X| \ll 1$

$$\left(\frac{\tanh\left(\frac{\mathbf{y}X}{2}\right)}{\left(\frac{\mathbf{y}X}{2}\right)} \right) \approx 1 \quad \text{so} \quad \frac{\mathbf{Y}'}{2} \approx \frac{\mathbf{Y}}{2}$$

Remember, this is an approximation!
We will see later when it is appropriate to use

Dr. Henry Louie 17



Simplified Models

- We don't always need the details of the distributed or equivalent lumped parameter models
- We can use the approximations previously shown to simply the model depending on transmission line length

Dr. Henry Louie 18

Short Line

- $X < 50$ mi
- Series impedance only $\mathbf{z} = \mathbf{z}X$

Dr. Henry Louie 19

Medium-Length Line

- $150 \text{ mi} > X > 50$ mi
- Capacitance becomes too large to ignore
- Also called the **nominal** Π -equivalent circuit

Dr. Henry Louie 20

Long Line

- $X > 150$ mi
- Use Π -equivalent circuit model (also transmission matrix or general solution)

Dr. Henry Louie 21

Summary

- Determined the transmission matrix using distributed parameters

$$\mathbf{T} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \mathbf{T} \begin{bmatrix} \mathbf{V}_2 \\ \mathbf{I}_2 \end{bmatrix}$$

- Discussed various line models
 - short line (series only; uses \mathbf{Z})
 - medium line (nominal Π -model; uses \mathbf{Z} and $\mathbf{Y}/2$)
 - long line (equivalent Π -model; uses \mathbf{Z}' and $\mathbf{Y}'/2$)

Dr. Henry Louie 22