

12-Power Transmission

Text: 4.6-4.10

ECEGR 451
Power Systems

Dr. Henry Louis 1

Overview

- Conservation of Complex Power
- Short Line Power Transmission
- Power Transmission Visualization
- Radial Line
- Medium and Long Line Power Transmission
- Voltage Collapse
- Surge Impedance Loading

Dr. Henry Louis 2

Introduction

- We want to determine the complex power (or P, Q) flowing out of generators and through transmission lines
- Most utility-scale power plants feature synchronous generators
 - $|V|$ controlled by exciter, which influences Q
 - δ (power angle) controlled by prime mover, which influences P

Dr. Henry Louis 3

Conservation of Complex Power

- Complex power (and P, Q) are conserved
- Single line example

$S_{12} + S_{21} = S_{Line}$
- System example

Complex power consumed by area B:
 $S_{AB} + S_{G1} + S_{G2} + S_{G3}$

Dr. Henry Louis 4

Power Transmission

Load 1 Load 2

Gen. 1 short line model Gen. 2

Dr. Henry Louis 5

Power Transmission-Short Line

$S_{12} = v_1 i_1 = v_1 \left(\frac{v_1 - v_2}{Z} \right)^*$

$S_{12} = \frac{|v_1|^2}{Z^*} - \frac{v_1 v_2^*}{Z}$

$S_{12} = \frac{|v_1|^2}{|Z|} e^{j\angle Z} - \frac{|v_1||v_2|}{|Z|} e^{j\angle Z} e^{-j\theta_{12}}$

$S_{21} = \frac{|v_2|^2}{|Z|} e^{j\angle Z} - \frac{|v_2||v_1|}{|Z|} e^{j\angle Z} e^{-j\theta_{12}}$ by symmetry

per-phase representation

Dr. Henry Louis 6

Power Transmission-Short Line

- Magnitudes of V_1 and V_2 are controlled by excitors of the generators and are fairly constant
- θ_{12} can be increased by increasing the mechanical power of Gen. 1 and/or by decreasing the mechanical power of Gen. 2 (recall power angle in ECEGR 450)

$$S_{12} = \frac{|V_1|^2}{|Z|} e^{j\angle Z} - \frac{|V_1||V_2|}{|Z|} e^{j\angle Z} e^{j\theta_{12}}$$

$$S_{21} = \frac{|V_2|^2}{|Z|} e^{j\angle Z} - \frac{|V_2||V_1|}{|Z|} e^{j\angle Z} e^{-j\theta_{12}}$$

Dr. Henry Louie 7

Example

Increasing the receiving end voltage (V_2) increases the complex power flowing from generator 1 (S_{12})

- True
- False

Dr. Henry Louie 8

Example

Increasing the receiving end voltage (V_2) increases the complex power flowing from generator 1 (S_{12})

- True
- False

$$S_{12} = \frac{|V_1|^2}{|Z|} e^{j\angle Z} - \frac{|V_1||V_2|}{|Z|} e^{j\angle Z} e^{j\theta_{12}}$$

Dr. Henry Louie 9

Power Transmission Visualization

$$S_{12} = \frac{|V_1|^2}{|Z|} e^{j\angle Z} - \frac{|V_1||V_2|}{|Z|} e^{j\angle Z} e^{j\theta_{12}}$$

$$S_{21} = \frac{|V_2|^2}{|Z|} e^{j\angle Z} - \frac{|V_2||V_1|}{|Z|} e^{j\angle Z} e^{-j\theta_{12}}$$

$$S_{12} = C_1 - Be^{j\theta_{12}}$$

$$-S_{21} = C_2 + Be^{-j\theta_{12}}$$

where

$$C_1 = \frac{|V_1|^2}{|Z|} e^{j\angle Z}$$

$$C_2 = -\frac{|V_2|^2}{|Z|} e^{j\angle Z}$$

$$B = \frac{|V_1||V_2|}{|Z|} e^{j\angle Z}$$

independent of θ_{12}

Dr. Henry Louie 10

Power Transmission-Short Line

- If θ_{12} is varied, S_{12} and S_{21} sweep out circles in complex plane

sending-end circle
 $S_{12} = C_1 - Be^{j\theta_{12}}$
 centered at C_1 radius = $|B|$

receiving-end circle
 $-S_{21} = C_2 + Be^{-j\theta_{12}}$
 centered at C_2 radius = $|B|$

Dr. Henry Louie 11

Power Transmission-Short Line

radius = $\frac{|V_1||V_2|}{|Z|}$

sending-end

$$C_1 = \frac{|V_1|^2}{|Z|} \angle Z$$

receiving-end

$$C_2 = \frac{|V_2|^2}{|Z|} \angle Z$$

Dr. Henry Louie 12

Power Transmission-Short Line

- Observations
 - circles do not intersect if voltage magnitudes are not equal
 - as θ_{12} increases from 0, active power sent and received increases
 - there is a maximum amount of real power sent

$$\theta_{12} = 180^\circ - \angle Z$$

- and received

$$\theta_{12} = \angle Z$$

- Most transmission lines have small resistance compared to inductance

Dr. Henry Louie 13

Power Transmission-Short Line

Lossless line ($R = 0$)

- $\angle Z = 0^\circ$
- $P_{12} = -P_{21}$
- circles lie on Q-axis

Dr. Henry Louie 14

Power Transmission-Short Line

- Assume lossless line ($R = 0$)

$$P_{12} = -P_{21} = \frac{|\mathbf{V}_1||\mathbf{V}_2|}{X_L} \sin \theta_{12} \quad \text{reactance of the line}$$

$$P_{12} = -P_{21} = \frac{|\mathbf{V}_1||\mathbf{V}_2|}{X_L} \sin \theta_{12} \quad \text{maximum power transfer: } \frac{|\mathbf{V}_1||\mathbf{V}_2|}{X_L}$$

$$Q_{12} = \frac{|\mathbf{V}_1|^2}{X_L} - \frac{|\mathbf{V}_1||\mathbf{V}_2|}{X_L} \cos \theta_{12}$$

$$Q_{21} = \frac{|\mathbf{V}_2|^2}{X_L} - \frac{|\mathbf{V}_1||\mathbf{V}_2|}{X_L} \cos \theta_{12}$$

We will derive these expressions later

Dr. Henry Louie 15

Power Transmission-Short Line

- Under normal operating conditions: $|\theta_{12}| < 10^\circ$
- Approximating
 - $\sin \theta_{12} \approx \theta_{12}$
 - $\cos \theta_{12} \approx 1$ in radians
- Results in
 - $P_{12} = \frac{|\mathbf{V}_1||\mathbf{V}_2|}{X_L} \sin \theta_{12} \approx \frac{|\mathbf{V}_1||\mathbf{V}_2|}{X_L} \theta_{12}$ P is sensitive to θ_{12}
 - $Q_{12} \approx \frac{|\mathbf{V}_1|^2}{X_L} - \frac{|\mathbf{V}_1||\mathbf{V}_2|}{X_L}$ Q is sensitive to voltage magnitude

Dr. Henry Louie 16

Example

- Lossless line
- Power consumed by the load is $(10 + j0)$ MVA
- Assume C is selected to make $|\mathbf{V}_2| = 100,000 = |\mathbf{V}_1|$
- Find the corresponding reactive power injected by the capacitor, Q_C

Dr. Henry Louie 17

Example

$P_{12} = -P_{21} = 1$ MW lossless line assumption

$$P_{12} = \frac{|\mathbf{V}_1||\mathbf{V}_2|}{X_L} \sin \theta_{12} = 10 \text{ MW}$$

$(20 \times 10^6) \sin \theta_{12} = 10 \text{ MW} \Rightarrow \theta_{12} = 30^\circ$


$$\theta_1 = 0^\circ \Rightarrow \theta_2 = -30^\circ$$

$$Q_{21} = \frac{|\mathbf{V}_2|^2}{X} - \frac{|\mathbf{V}_1||\mathbf{V}_2|}{X} \cos \theta_{12}$$

$$= (20 - 20 \cos 30^\circ) \times 10^6 = 2.68 \text{ MVAR}$$


$$Q_C = Q_{21} = 2.68 \text{ MVAR}$$

Dr. Henry Louie 18




Example


- Reactive power compensation is removed
- $|V_1| = 100,000 \text{ V}$
- Can the load of 10 MW be supplied?
- What is $|V_2|$ for this operating point?

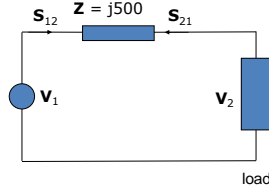

19



Example

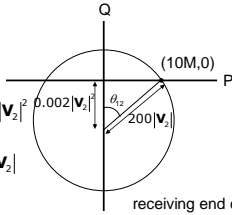


$$-S_{21} = C_2 + B e^{-j\theta_{12}}$$

$$C_2 = \frac{|V_2|^2}{Z} e^{j\theta_{12}} = 0.002 |V_2|^2 \angle \theta_{12}$$

$$B = \frac{|V_1| |V_2|}{Z} e^{j\theta_{12}} = 200 |V_2|$$

20



Example

By Pythagorean theorem:


$$(0.002 |V_2|^2)^2 + (10 \times 10^6)^2 = (200 |V_2|)^2$$

$$x = |V_2|^2$$

$$0.002^2 x^2 - 200^2 x + 10e12 = 0$$

$$x = 5e9$$

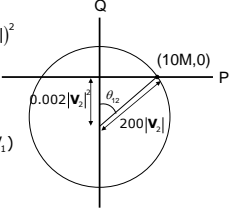
$$V_2 = 70,700 \text{ (very low compared to } V_1)$$



the capacitor bank greatly improved the voltage at bus 2

θ_{12} can be calculated as 45 degrees

21



Radial Line

- Lossless radial line
- We want to find the $|V_2|$ and S relationship
- Let $\phi = \theta_{V2} - \theta_1$


$$S_0 = \mathbf{V}_2 \mathbf{I}^*$$

$$= |V_2| |\mathbf{I}| (\cos \phi + j \sin \phi)$$


$$= P_0 + j |V_2| |\mathbf{I}| \sin \phi$$

$$= P_0 + j |V_2| |\mathbf{I}| \cos \phi \frac{\sin \phi}{\cos \phi}$$
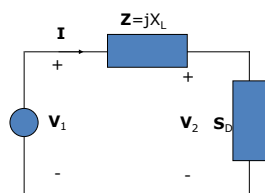
$$= P_0 (1 + j \beta) \quad \beta = \tan \phi$$



22



Radial Line

$$P_D = P_{12} = \frac{|V_1| |V_2|}{X_L} \sin \theta_{12}$$

$$Q_0 = -Q_{21} = \frac{|V_2|^2}{X_L} + \frac{|V_1| |V_2|}{X_L} \cos \theta_{12}$$


} previous result

$$P_D^2 = \left(\frac{|V_1| |V_2|}{X_L} \right)^2 \sin^2 \theta_{12}$$

$$P_D^2 = \left(\frac{|V_1| |V_2|}{X_L} \right)^2 (-\cos^2 \theta_{12} + 1) \quad \text{using } \cos^2 \theta_{12} + \sin^2 \theta_{12} = 1$$

$$\left(Q_0 + \frac{|V_2|^2}{X_L} \right)^2 = \left(\frac{|V_1| |V_2|}{X_L} \right)^2 \cos^2 \theta_{12}$$

23



Radial Line

$$P_D^2 = \left(\frac{|V_1| |V_2|}{X_L} \right)^2 (-\cos^2 \theta_{12} + 1)$$

$$\left(Q_0 + \frac{|V_2|^2}{X_L} \right)^2 = \left(\frac{|V_1| |V_2|}{X_L} \right)^2 \cos^2 \theta_{12}$$

$$P_D^2 = - \left(Q_0 + \frac{|V_2|^2}{X_L} \right)^2 + \left(\frac{|V_1| |V_2|}{X_L} \right)^2 \quad \text{substituting for the cosine term}$$

$$P_D^2 = - \left(\beta P_D + \frac{|V_2|^2}{X_L} \right)^2 + \left(\frac{|V_1| |V_2|}{X_L} \right)^2 \quad \text{using } \beta = \tan \phi = \frac{Q_0}{P_D}$$

$$|V_2|^4 + (2\beta P_D X_L - |V_1|^2) |V_2|^2 + (1 + \beta) P_D^2 X_L^2 = 0 \quad \text{arranging for the quadratic equation}$$

24

Radial Line


$$|V_2|^4 + (2/\beta P_D X_L - |V_1|^2) |V_2|^2 + (1 + \eta) P_D^2 X_L^2 = 0$$

$$|V_2|^2 = \frac{|V_1|^2}{2} - 2/\beta P_D X_L \pm \left[\frac{|V_1|^4}{4} - |V_2|^2 P_D X_L (P_D X_L + \beta |V_1|^2) \right]^{1/2}$$




solutions to quad. eqn

Two solutions! Two receiving-end voltages that supply S_D . Power system is operated at the higher voltage solution.
Is there a limit to the power that can be delivered?

Dr. Henry Louie 25

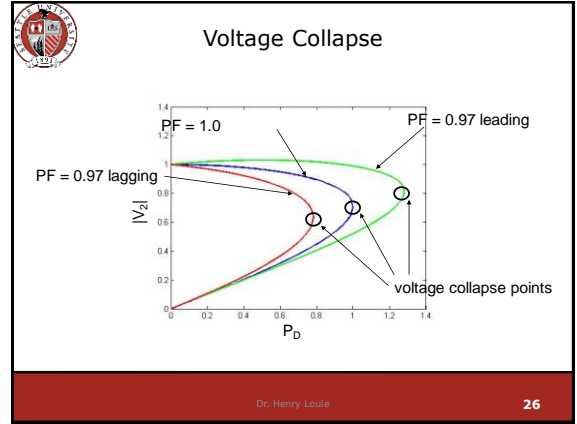

- Voltage Collapse**
- Voltage collapse is characterized by a precipitous decline in voltage at the receiving end bus as more power is demanded
 - Power systems should be designed and operated to avoid this condition
 - Voltage collapse is a function of several parameters, including:
 - sending and receiving end voltage magnitudes
 - power factor angle of the load
 - line impedance
 - A dc example can be used explain the mechanism of collapse
- Dr. Henry Louie 27

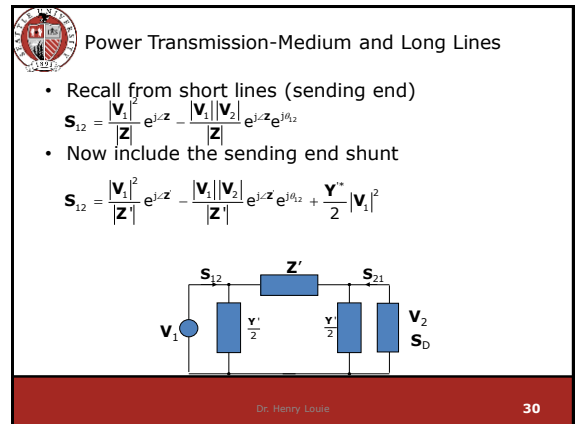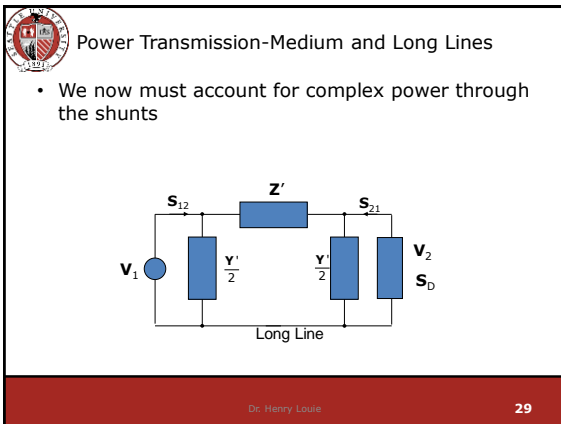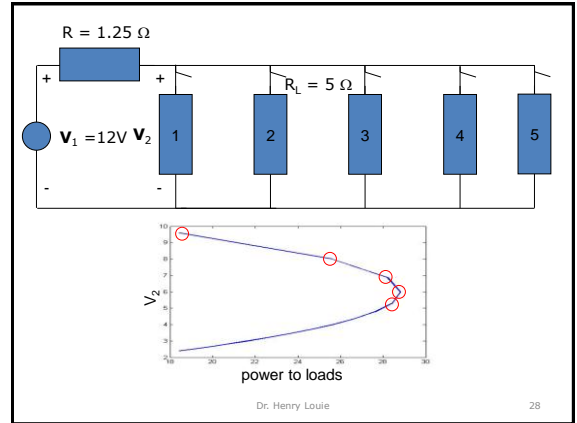


Power Transmission-Medium and Long Lines

- Receiving end short line

$$S_{21} = \frac{|V_2|^2}{|Z|} e^{j\alpha Z} - \frac{|V_2||V_1|}{|Z|} e^{j\alpha Z} e^{-j\theta_{12}}$$
- Now include the shunts

$$S_{21} = \frac{|V_1|^2}{|Z|} e^{j\alpha Z'} - \frac{|V_2||V_1|}{|Z|} e^{j\alpha Z'} e^{-j\theta_{12}} + \frac{Y^*}{2} |V_2|^2$$

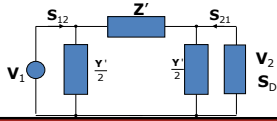

Dr. Henry Louie 31

Power Transmission-Medium and Long Lines

- Note that for long lines, use Z' and Y'
- For medium lines, use Z and Y
- Influence of $\frac{Y}{2}|V_1|^2$ and $\frac{Y}{2}|V_2|^2$ is usually limited
- How does this affect the sending and receiving end circles?

Dr. Henry Louie 32


Surge Impedance Loading (SIL)

- A lossless line terminated in its characteristic impedance (Z_c) is said to be Surge Impedance Loaded (SIL)
- Under these conditions:
 - $|V_1| = |V_2|$
 - $|I_1| = |I_2|$
- The transmitted power is $P_{SIL} = |V_1|^2/Z_c$

Dr. Henry Louie 33

Surge Impedance Loading (SIL)

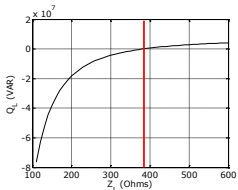- For lossless lines, Z_c is real
 - $Z_L < Z_c$
 - $Q_{12} < 0$
 - Transmission line absorbs reactive power (inductive)
 - $Z_L = Z_c$
 - $Q_{12} = 0$
 - $Z_L > Z_c$
 - $Q_{12} > 0$
 - Transmission line supplies reactive power (capacitive)




$y = j5.38e-3$
 $z = j0.789$
 $Z_c = 383 \Omega$
 Length = 1000 km
 $V_{21-L} = 138\text{kv}$

Dr. Henry Louie 34

Surge Impedance Loading (SIL)

- $Z_L < Z_c$
 - $|V_1| > |V_2|$
 - Sending end voltage higher than receiving
- $Z_L = Z_c$
 - $|V_1| = |V_2|$
- $Z_L > Z_c$
 - $|V_1| < |V_2|$
 - Sending end voltage less than receiving!
 - Ferranti effect

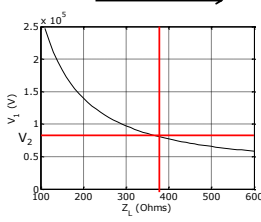

↓ decreasing load →

Dr. Henry Louie 35

Example

What time of day do you expect the voltage at the end of long transmission lines to be the highest?

Dr. Henry Louie 36

Surge Impedance Loading

- See
 - SIL_Movie.mat ($Z_L = Z_C$)
 - SIL_Movie_2.mat ($Z_L = 0.5Z_C$)
 - SIL_Movie_3.mat ($Z_L = 100Z_C$)

37

Surge Impedance Loading (SIL)

- See example 4.2, 4.3 for more details

38

Stability Limits

- Increasing θ_{12} increases the power flow across the line
- For lossless lines, maximum power transmission occurs when $\theta_{12} = 90^\circ$

$P_{12} = \frac{|V_1||V_2|}{X_L} \sin \theta_{12}$

39

Stability Limits

- It is desired to limit $|\theta_{12}|$ for stability reasons
- Consider a lossless long transmission line
- Transmitted power is

$$S_{12} = \frac{Y''}{2} |V_1|^2 + \frac{|V_1|^2}{Z^*} - \frac{|V_1||V_2|}{Z} e^{j\theta_{12}}$$
- With lossless assumptions

$$Z' = Z_c \sinh(\beta X) = jZ_c \sin(\beta X) \quad Y'' = Y \frac{\tanh(\gamma X/2)}{\gamma X/2} = j\omega C \frac{\tanh(\beta X/2)}{\beta X/2}$$
- Real power transmitted:

$$\text{Re}\{S_{12}\} = \text{Re}\left\{ \frac{Y}{2} |V_1|^2 + \frac{|V_1|^2}{Z^*} - \frac{|V_1||V_2|}{Z} e^{j\theta_{12}} \right\}$$

40

Stability Limits

- Via Euler's Identity and assuming voltage magnitude at each end of the line are equal:

$$\text{Re}\{S_{12}\} = \text{Re}\left\{ \frac{|V_1||V_2|}{Z} e^{j\theta_{12}} \right\} = P_{12} = \frac{|V_1|^2}{Z_c} \frac{\sin(\theta_{12})}{\sin(\beta X)}$$
- From the SIL definition:

$$P_{12} = P_{\text{SIL}} \frac{\sin(\theta_{12})}{\sin(\beta X)}$$
- Limiting θ_{12} , limits maximum power transferred
- For a fixed θ_{12} , as length increases, maximum power transfer decreases
- For very long lines with $\beta X = \pi/2$, P_{SIL} cannot be exceeded

41

Limits

42

Summary (Short Line)

$$S_{12} = \frac{|V_1|^2}{|Z|} e^{j\alpha Z} - \frac{|V_1||V_2|}{|Z|} e^{j\alpha Z} e^{j\theta_{12}} \quad S_{21} = \frac{|V_2|^2}{|Z|} e^{j\alpha Z} - \frac{|V_2||V_1|}{|Z|} e^{j\alpha Z} e^{-j\theta_{12}}$$

per-phase representation

43

Summary (Short Lossless Line)

$$P_{12} = -P_{21} = \frac{|V_1||V_2|}{X_L} \sin \theta_{12} \quad Q_{12} = \frac{|V_1|^2}{X_L} - \frac{|V_1||V_2|}{X_L} \cos \theta_{12}$$

per-phase representation

44

Summary (Short Line)

- Discussed power circles for power transmission analysis

$$S_{12} = \frac{|V_1|^2}{|Z|} e^{j\alpha Z} - \frac{|V_1||V_2|}{|Z|} e^{j\alpha Z} e^{j\theta_{12}} \quad S_{21} = \frac{|V_2|^2}{|Z|} e^{j\alpha Z} - \frac{|V_2||V_1|}{|Z|} e^{j\alpha Z} e^{-j\theta_{12}}$$

- Lossless lines:

$$P_{12} = -P_{21} = \frac{|V_1||V_2|}{X_L} \sin \theta_{12} \quad Q_{12} = \frac{|V_1|^2}{X_L} - \frac{|V_1||V_2|}{X_L} \cos \theta_{12}$$

(if a short line model is used)

45

Summary (Medium Line)

$$S_{12} = \frac{|V_1|^2}{|Z|} e^{j\alpha Z} - \frac{|V_1||V_2|}{|Z|} e^{j\alpha Z} e^{j\theta_{12}} + \frac{Y^*}{2} |V_1|^2$$

$$S_{21} = \frac{|V_2|^2}{|Z|} e^{j\alpha Z} - \frac{|V_2||V_1|}{|Z|} e^{j\alpha Z} e^{-j\theta_{12}} + \frac{Y^*}{2} |V_2|^2$$

46

Summary (Long Line)

$$S_{12} = \frac{|V_1|^2}{|Z|} e^{j\alpha Z} - \frac{|V_1||V_2|}{|Z|} e^{j\alpha Z} e^{j\theta_{12}} + \frac{Y^*}{2} |V_1|^2$$

$$S_{21} = \frac{|V_2|^2}{|Z|} e^{j\alpha Z} - \frac{|V_2||V_1|}{|Z|} e^{j\alpha Z} e^{-j\theta_{12}} + \frac{Y^*}{2} |V_2|^2$$

47

Summary

- Discussed radial lines
 - two operating points: one is stable, one unstable
 - voltage collapse: limits the amount of power that can be supplied to a load
- Stability limits tend to limit power transfer for long lines

48