

14-Ideal Single Phase Transformers

ECEGR 450
Electromechanical Energy Conversion



Overview

- Transformers
- Ideal Single-Phase Transformer
- Transformer Polarity
- Circuit Model

Dr. Louie

2



Questions

- Why are transformers used in power systems?
- Is it possible to use a "dc" transformer?
- Are transformers efficient?
- How is the power into a transformer related to the power out of a transformer?

Dr. Louie

3



Introduction



Dr. Louie

4



Introduction



Dr. Louie

5



Introduction



"homemade" zambian transformer

Dr. Louie

6

Introduction

- Review Chapter 2
- Transformers are important electrical-electrical energy conversion components
- One important reason we use AC is because we can easily change the voltage levels, which reduces losses
- Transformers enable this conversion of voltage level
 - High efficiency (up to 99%)
 - No or few moving parts (low maintenance)

7


Transformers

- Shift between voltage levels
 - generation 11 kV to 30 kV
 - transmission up to 765 kV
 - distribution around 69 kV
 - residential 240/120 V
- Controlling voltages, power flows
 - regulating transformers
- Isolation (dc current)
- Instrument
 - PTs, CTs

8

Ideal Single-Phase Transformer

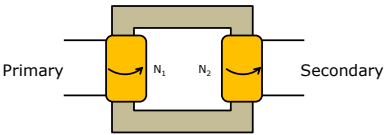- Two magnetically coupled coils
 - Primary: N_1 turns
 - Secondary: N_2 turns
- Primary and secondary can be arbitrarily assigned
- Note direction of windings



Primary Secondary


9

Ideal Single-Phase Transformer

Ideal assumptions

- No flux leakage
- No eddy currents
- No winding resistance
- Near infinite core permeability

} Recall from magnetic circuits lecture

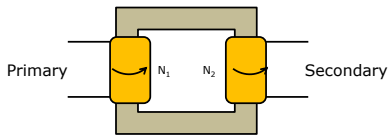


Primary Secondary

10

Single-Phase Transformer

- Primary directly connected to AC voltage source
- Voltage across coil has sinusoidal flux associated with it
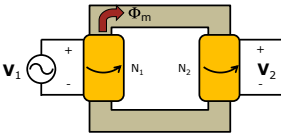
$$e = -\frac{d\phi}{dt} \text{ (Faraday's Law)}$$


11


Single-Phase Transformer

- Same flux passes through each coil
 - Φ_m : mutual flux (phasor)
- Therefore:

$$V_1 = \frac{d\lambda_1}{dt} = N_1 \frac{d\Phi_m}{dt}$$

$$V_2 = \frac{d\lambda_2}{dt} = N_2 \frac{d\Phi_m}{dt}$$
- Rewritten:
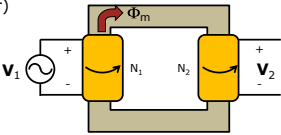
$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \triangleq a \triangleq \frac{1}{n}$$



12

Single-Phase Transformer

- Ratio of voltages is the same as the ratio of turns
- Possible to transform voltage level from primary V_1 to secondary (and vice versa)
- Note: no current flows (near infinite permeability)
 - $\phi = BA = \frac{\mu NiA}{\ell}$

Dr. Louie 13

Question

If $|V_1| = 120V$, is $|V_2|$ greater than 120V?

Dr. Louie 14

Question

If $|V_1| = 120V$, is $|V_2|$ greater than 120V?

Less than 120V.

The winding with more turns has greater voltage

Dr. Louie 15

Single-Phase Transformer

Phasor Diagram (ideal, no load)

V_1, V_2 in phase.
 Φ_m lags voltage by 90°
 No current flows

Dr. Louie 16

Single-Phase Transformer

- Now a resistive load is connected to the secondary
- V_2 causes I_2 to flow
- Examining mmf $\sum = N_1 I_1 - N_2 I_2 = \mathcal{H} \ell = \Phi_m \mu A$
- Infinite permeability $\sum = N_1 I_1 - N_2 I_2 = 0$
- Current gain $\frac{I_2}{I_1} = \frac{N_1}{N_2} = a$

Compare to: $\frac{V_1}{V_2} = \frac{N_1}{N_2}$

Dr. Louie 17

Single-Phase Transformer

Phasor Diagram (ideal, resistive load)

V_1, V_2 in phase.
 I_1, I_2 in phase.
 I_1, I_2 in phase with Φ_m
 Φ_m lags voltage by 90°

Note: $|\Phi|$ arbitrarily drawn

Dr. Louie 18

Question

In an ideal transformer serving a load, if $|\mathbf{V}_1| > |\mathbf{V}_2|$, is $|\mathbf{I}_1| > |\mathbf{I}_2|$?

Dr. Louie 19

Question

In an ideal transformer serving a load, if $|\mathbf{V}_1| > |\mathbf{V}_2|$, is $|\mathbf{I}_1| > |\mathbf{I}_2|$?

No. The transformer would be creating energy.

Dr. Louie 20

Question

How are the transformer input and output power related? Find α in $P_1 = \alpha P_2$

Dr. Louie 21


Single-Phase Transformer

- Power into the transformer
 $P_1 = \text{Re}\{\mathbf{V}_1 \mathbf{I}_1^*\}$
- Power out of the transformer
 $P_2 = \text{Re}\{\mathbf{V}_2 \mathbf{I}_2\} = \text{Re}\{\frac{1}{a} \mathbf{V}_1 \mathbf{I}_2\} = \text{Re}\{\frac{1}{a} \mathbf{V}_1 a \mathbf{I}_1\} = P_1$
- Power is conserved

Dr. Louie 22

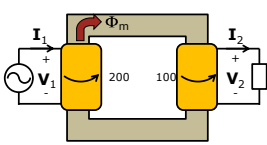Question

- Now a load with PF = 0.707 lagging is connected to the secondary
- Draw the phasor diagram of $\mathbf{V}_1, \mathbf{V}_2, \mathbf{I}_1, \mathbf{I}_2, \Phi_m$




Dr. Louie 23

Question

- Now a load with PF = 0.707 lagging is connected to the secondary
- Draw the phasor diagram of $\mathbf{V}_1, \mathbf{V}_2, \mathbf{I}_1, \mathbf{I}_2, \Phi_m$

$|\Phi_m|, |\mathbf{I}|$ can be arbitrarily drawn with respect to each other

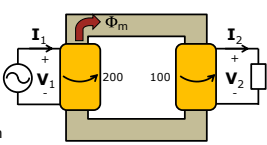

Dr. Louie 24

Question

- V_1, V_2 in phase: $V_1 = V_2 \frac{N_1}{N_2}$
- Φ_m lags voltage by 90° : $e = -\frac{d\phi}{dt}$
- I_2 lags V_2 by 45° : $\phi = \cos^{-1}(0.707) = 45^\circ$
- I_1, I_2 in phase: $I_1 = I_2 \frac{N_2}{N_1}$

I_1, I_2 not in phase with Φ_m .

Dr. Louie 25

Transformer Polarity

What if the secondary coil was wound the opposite direction?

Examining the mmf:
 $\sum = N_1 I_1 + N_2 I_2 = 0$
 $N_1 I_1 = -N_2 I_2$

Current and voltage polarity reverses

Dr. Louie 26

Transformer Polarity

- Dot polarity:
 - Current entering polarity-marked terminals create flux in the same direction
 - When current enters one polarity-marked terminal, it leaves the other
 - Voltage of polarity-marked terminals are in phase (e.g. they are positive at the same time)

Transformer polarity is dictated by the direction of windings

Dr. Louie 27

Circuit Model

- New circuit element: Ideal Transformer
- Voltage relationship
 $e_1 = a e_2$
- Current relationship
 $I_1 = \frac{1}{a} I_2$

Recall: $a = \frac{N_1}{N_2}$

Dr. Louie 28

Circuit Model

- Now a load is connected to the secondary
- Solving for I_1

$$I_1 = \frac{1}{a} I_2$$

$$I_1 = \frac{1}{a} \frac{V_2}{Z} \text{ using } I_2 = \frac{V_2}{Z}$$

$$I_1 = \frac{V_1}{a^2 Z} \text{ using } V_1 = a V_2$$

Dr. Louie 29

Circuit Model

From this result, it is possible to analyze the circuit only using primary-side voltage and current (V_1, I_1)

$I_1 = \frac{V_1}{a^2 Z}$ [Secondary impedance referred to the primary side]

Dr. Louie 30

Example

Consider an ideal transformer with $N_1 = 100$ and $N_2 = 500$. The primary is connected to a 100 V source. A load of 100 Ohms is connected to the secondary. Find the power delivered to the load.

Dr. Louie 31

Example

Consider an ideal transformer with $N_1 = 100$ and $N_2 = 500$. The primary is connected to a 100 V source. A load of 100 Ohms is connected to the secondary. Find the power delivered to the load.

$a = \frac{N_1}{N_2} = \frac{100}{500} = 0.2$

Dr. Louie 32

Example

Consider an ideal transformer with $N_1 = 100$ and $N_2 = 500$. The primary is connected to a 100 V source. A load of 100 Ohms is connected to the secondary. Find the power delivered to the load.

$P = \frac{|V_1|^2}{R} = \frac{10,000}{4} = 2,500 \text{ W}$

Dr. Louie 33

Summary

- Transformers are magnetically coupled coils
- Ratio of turns from primary to secondary is the "turns ratio". Side with greater number of turns has higher voltage, but lower current
- Ideal transformers: Power in = Power out
- Equivalent circuit is used to analyze transformers. Impedances can be transferred from secondary to primary by scaling by a^2

Dr. Louie 34