

14-Per Unit

Text: 5.5 – 5.7

ECEGR 451
Power Systems

Dr. Henry Louie

1

Topics

- Definitions
- Per Unit Analysis
- Per Unit & Transformers
- Three-Phase Per Unit

Dr. Henry Louie

2

Per Unit

- Per unit (p.u.) simplifies system calculations
 - eliminates partitions introduced by transformers
 - erroneous values are easily spotted
- Normalizes values in the system

$$\text{per unit quantity} = \frac{\text{actual quantity}}{\text{base value of quantity}}$$

Dr. Henry Louie

3

Per Unit

- Voltage
 $V_{p.u.} = \frac{V}{V_{Base}}$
- Current
 $I_{p.u.} = \frac{I}{I_{Base}}$
- Power
 $S_{p.u.} = \frac{S}{S_{Base}}$
- Impedance
 $Z_{p.u.} = \frac{Z}{Z_{Base}}$

Note: base values are scalars

Dr. Henry Louie

4

Per Unit

- Example
if V_B is selected to be 125,000 volts and $V = 137,500$ at zero degrees, then
$$V_{p.u.} = \frac{137,500 \angle 0^\circ \text{ V}}{125,000 \text{ V}} = 1.1 \angle 0^\circ$$
- Note: units cancel, so $V_{p.u.}$ is technically unitless, but it is common to add a "per unit" at the end

Dr. Henry Louie

5

Base Selection

- Proper selection of base quantities is essential to simplify the problem
base must be a **real scalar**
select base quantities to obey Ohm's Law

$$V_B = I_B Z_B$$


therefore:

$$\frac{V}{V_B} = \frac{I Z}{I_B Z_B}$$

$$\Rightarrow V_{p.u.} = I_{p.u.} Z_{p.u.}$$

Dr. Henry Louie

6

 Per Unit

- We follow the same procedure to define the power base

$$\mathbf{S} = \mathbf{VI}^*$$

$$\frac{\mathbf{S}}{S_B} = \frac{\mathbf{VI}^*}{V_B I_B}$$


$$\Rightarrow \mathbf{S}_{p.u.} = \mathbf{V}_{p.u.} \mathbf{I}_{p.u.}^*$$

$$\mathbf{S}_{p.u.} = P_{p.u.} + jQ_{p.u.} \quad \text{note error in the book}$$

$$P_{p.u.} = \frac{P}{S_B}$$

$$Q_{p.u.} = \frac{Q}{S_B}$$

Dr. Henry Louie 7

 Per Unit

- For impedance:


$$\mathbf{Z}_{p.u.} = R_{p.u.} + jX_{p.u.}$$

$$R_{p.u.} = \frac{R}{Z_B}$$

$$X_{p.u.} = \frac{X}{Z_B}$$


$$Y_B \triangleq \frac{I_B}{V_B} = \frac{1}{Z_B}$$

Dr. Henry Louie 8

 Example

Let $V_B = 100\text{kV}$ and $I_B = 50\text{A}$, compute Z_B and S_B .

Dr. Henry Louie 9

 Example


Let $V_B = 100\text{kV}$ and $I_B = 50\text{A}$, compute Z_B and S_B .

$$V_B = I_B Z_B$$

$$Z_B = \frac{V_B}{I_B} = 2000\Omega$$

$$S_B = V_B I_B = 5\text{MVA}$$

Dr. Henry Louie 10


 Per Unit Base Selection

- There are two equations that govern the relationship between base values

$$V_B = I_B Z_B \quad S_B = V_B I_B$$

- There are four base values that can be assigned
 - V_B, I_B, Z_B, S_B
- Convention is to select V_B and S_B and compute Z_B and I_B
 - V_B is typically selected such that the voltage levels are between 0.95 to 1.05 p.u.

Dr. Henry Louie 11


 Example

- Let

$$V_B = 277\text{ V}$$

$$S_B = 69.25\text{ VA}$$

- Compute Z_B and I_B

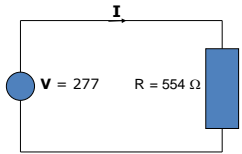

Dr. Henry Louie 12

Example

- Let
 - $V_B = 277 \text{ V}$
 - $S_B = 69.25 \text{ VA}$
- Compute Z_B and I_B
 - $Z_B = \frac{V_B^2}{S_B} = 1108 \Omega$
 - $I_B = \frac{V_B}{Z_B} = 0.25 \text{ A}$

equivalent circuit

13

Per Unit Example

- We can easily solve the circuit
 - $I_{p.u.} = \frac{V_{p.u.}}{Z_{p.u.}} = \frac{1 \angle 0^\circ}{0.5} = 2 \angle 0^\circ$
 - $S_{p.u.} = V_{p.u.} I_{p.u.}^* = 1 \angle 0^\circ \times 2 \angle 0^\circ = 2 + j0$
- We may wish to convert back to current and power:
 - $I = 2/0.25 = 0.5 \text{ A}$
 - $S = 2/69.25 = 138.5 \text{ VA}$

equivalent circuit

14

Per Unit & Transformers

- One of the most important advantages of using per unit is realized when transformers are involved

$\left. \begin{matrix} V_{1B} \\ S_B \\ I_{1B} \\ Z_{1B} \end{matrix} \right\} \text{side 1 bases}$	side 2 bases	$\left\{ \begin{matrix} V_{2B} = nV_{1B} \\ S_B \\ I_{2B} = aI_{1B} \\ Z_{2B} = n^2Z_{1B} \end{matrix} \right.$
---	--------------	---

15

Per Unit & Transformers

- We then get
 - $V_{2,a'n',p.u.} = \frac{V_{2,a'n'}}{V_{2B}} = \frac{nV_{1,a'n}}{nV_{1B}} = V_{1,a'n,p.u.}$
 - $I_{2,p.u.} = \frac{I_2}{I_{2B}} = \frac{aI_1}{aI_{1B}} = I_{1,p.u.}$

And can remove the ideal transformer

16

Example


- Transformer nameplate:
 - 22 kV Y/13.8 kV Y
 - $S_{rated} = 60 \text{ MVA}$ (3 phase)
 - $jX_L = j0.0807 \text{ Ohms}$
- Load:
 - $R = 5 \text{ Ohms}$
- Generator:
 - $V_{rated} = 22 \text{ kV}$
 - $S_{rated} = 60 \text{ MVA}$
- Find the power out of the generator

17

Example


- Transformer nameplate:
 - 22 kV Y/13.8 kV Y
 - $S_{rated} = 60 \text{ MVA}$ (3 phase)
 - $jX_L = j0.0807 \text{ Ohms}$
- Load:
 - $R = 5 \text{ Ohms}$
- Generator:
 - $V_{rated} = 22 \text{ kV}$
 - $S_{rated} = 60 \text{ MVA}$
- Assign bases
 - generator side
 - $V_{1B} = 22 \text{ kV}/(1.73) = 12.7 \text{ kV}$
 - $S_B = 20 \text{ MVA}$
 - load side
 - $V_{2B} = 13.8 \text{ kV}/(1.73) = 7.9 \text{ kV}$
 - $S_B = 20 \text{ MVA}$

18

 Example


- Assigned bases
 - generator side
 - $V_{1B} = 22\text{kV}/(1.73) = 12.7\text{ kV}$
 - $S_B = 20\text{ MVA}$
 - load side
 - $V_{2B} = 13.8\text{kV}/(1.73) = 7.9\text{ kV}$
 - $S_B = 20\text{ MVA}$
- Computed bases
 - $Z_{1B} = (V_{1B})^2/S_B = 8.07\ \Omega$
 - $Z_{2B} = (V_{2B})^2/S_B = 3.174\ \Omega$
 - $I_{1B} = V_{1B}/Z_{1B} = 1574.6\text{ A}$
 - $I_{2B} = 2510.2\text{ A}$

Dr. Henry Louie 19

 Example


- Transformer impedance (p.u.)
 - $X_{1p.u.} = 0.0807/8.07 = 0.01\text{ p.u.}$
- Load (p.u.):
 - $R_{p.u.} = (5/3.174) = 1.576\text{ p.u.}$
- Generator (p.u.):
 - $V_{p.u.} = 12.7\text{kV}/12.7\text{kV} = 1\text{ p.u.}$

Dr. Henry Louie 20


 Example

- Transformer
 - $X_{1p.u.} = 0.01\text{ p.u.}$
- Load:
 - $R_{p.u.} = 1.575\text{ p.u.}$
- Generator:
 - $V_{p.u.} = 1\text{ p.u.}$

equivalent circuit

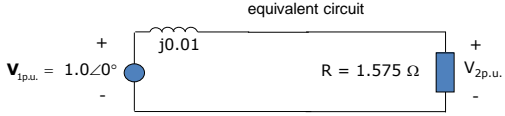


Dr. Henry Louie 21


 Example

- Solving
 - $I_{p.u.} = \frac{1}{1.575 + j0.01} = 0.634 \angle -0.36^\circ$
 - $S_{p.u.} = (1 \angle 0^\circ)(0.634 \angle -0.36^\circ) = 0.634 \angle -0.36^\circ$
 - $S = (S_B S_{p.u.}) = 12.7 \angle -0.36^\circ\text{ MVA}$
 - $S_{3\phi} = 38.1 \angle -0.36^\circ\text{ MVA}$

equivalent circuit




Dr. Henry Louie 22

 Example

- To find current:
 - $I_1 = I_{1B} I_{p.u.} = 1574.6(0.634 \angle -0.36^\circ) = 999.73 \angle -0.36^\circ\text{ A}$
 - $I_2 = I_{2B} I_{p.u.} = 2510.2(0.634 \angle -0.36^\circ) = 1593.7 \angle -0.36^\circ\text{ A}$

Dr. Henry Louie 23

 Notes on the Example

- Transformer impedances are usually given in p.u. (expressed as %) based on three-phase power and line-line voltage
 - i.e. $X_1 = 1\% = 0.01$
- A per-phase diagram using per unit values is called an **impedance diagram**
- We considered a Y-Y case. For normal systems, phase shifts are ignored. See text page 160 for other xfmr connection notes

Dr. Henry Louie 24

Three-Phase Per Unit

- So far we have dealt with per unit as defined by single phase expressions
- Interested in extension to three-phase
 - line-line voltages are used for V_B
 - three-phase power used for S_B

25

Three-Phase Per Unit

- As with three phase circuits, convention is to always give power base as three-phase, and voltage base as line-line
- Extra notation is given in this lecture and is omitted later

$$S_B^{3\phi} \triangleq 3S_B$$

$$V_B^{ll} \triangleq \sqrt{3}V_B$$

$$I_B = \frac{S_B^{3\phi}}{\sqrt{3}V_B^{ll}} = \frac{S_B}{V_B}$$

$$Z_B = \frac{(V_B)^2}{S_B} = \frac{(V_B^{ll}/\sqrt{3})^2}{S_B^{3\phi}/3} = \frac{V_B^{ll}}{S_B^{3\phi}}$$

$$S_B^{3\phi} \neq V_B^{ll} I_B$$

26

Change of Base

- Impedance of machines may not be given in the same base as used in the system
- Base conversion of impedance can save time

$$Z_{actual} = Z_{p.u.}^{old} Z_B^{old} = Z_{p.u.}^{new} Z_B^{new}$$

$$Z_{p.u.}^{new} = Z_{p.u.}^{old} \frac{Z_B^{old}}{Z_B^{new}}$$

$$Z_{p.u.}^{new} = Z_{p.u.}^{old} \left(\frac{V_B^{old}}{V_B^{new}} \right)^2 \frac{S_B^{new}}{S_B^{old}}$$

27

Per Unit (single vs three-phase)

- Given: $Z_{line} = j100 \Omega$, $Z_{load} = 75 \Omega$ (per phase) and $V_1 = 13.8 \text{ kV}$ (line-line)
- First without using per unit

$$I = \frac{7.967 \text{ kV}}{j100 + 75} = 63.73 \angle -53.13^\circ$$

$$S = V_{1,an} I^* = 0.304 + j0.406 \text{ MVA}$$

$$S_{3\phi} = 3S = 0.912 + j1.219 \text{ MVA}$$

28

Per Unit (single vs three-phase)

- Now using per unit with $V_B = 13.8/\sqrt{3}$, $S_B = 1 \text{ MVA}$

$$Z_B = \frac{(7.967)^2}{1} = 63.47 \Omega$$

$$Z_{load} = \frac{75}{63.47} = 1.18$$

$$Z_{line} = \frac{j100}{63.47} = j1.575$$

29

Per Unit (single vs three-phase)

- Now find the single-phase and three-phase power from the generator:

$$I_{pu} = \frac{1}{j1.575 + 1.18} = 0.508 \angle -53.13^\circ$$

$$S_{pu} = V_{1,pu} I_{pu}^* = 0.304 + j0.406 \text{ p.u.}$$

$$S = S_B S_{pu} = 0.304 + j0.406 \text{ MVA}$$

$$S_{3\phi,pu} = 3S_{pu} = 0.912 + j1.219 \text{ p.u.}$$

$$S_{3\phi} = S_B (S_{pu}) = 0.912 + j1.219 \text{ MVA}$$

30



Per Unit (single vs three-phase)

- We found the single-phase power to be:
 $S_{pu} = 0.304 + j0.406$ p.u.
 $S = 0.304 + j0.406$ MVA
- and the three-phase power to be:
 $S_{3\phi, pu} = 0.912 + j1.219$ p.u.
 $S_{3\phi} = 0.912 + j1.219$ MVA
- We define the three-phase base power as:
 $S_B^{3\phi} = 3S_B = 3$ MVA
 $S_{3\phi, pu} = \frac{0.912 + j1.219 \text{ MVA}}{3 \text{ MVA}} = 0.304 + j0.406$ p.u.

Dr. Henry Louie

31



Per Unit (single vs three-phase)

- If the single phase power is $0.304 + j0.406$ p.u., the three phase power is also $0.304 + j0.406$ p.u.
- A voltage of 1.0 p.u. in the single phase circuit implies that the line-line voltage is 1.0 p.u.
- When we do a per-phase analysis, the results can be applied the three-phase quantities; just remember to use the correct base when converting back to the actual values
- If we dealing with per unit values only, you need not distinguish between per phase and three phase power, nor line-line voltage and line-neutral voltage

Dr. Henry Louie

32



Per Unit (single vs three-phase)

- For example: you are doing a problem with $V_B = 22$ kV (line-line), and $S_B = 100$ MVA (three-phase). You do a **per-phase analysis** and find:
- $V_{1, an, pu} = 0.90$ p.u.
- $S_{pu} = 1.5$ p.u. (per phase power)
- What is the line-line voltage at V_1 ?
 $V_1 = 0.9(22\text{kV}) = 19.8\text{kV}$
- What about the three phase power?
 $S_{3\phi} = 1.5(100 \text{ MVA}) = 150 \text{ MVA}$

Dr. Henry Louie

33



Per Unit (transformer connections)

- If we use the bases corresponding to the nameplate ratings, the per unit reactances have the **same numerical values** in the Y-Y, Δ -Y, Δ - Δ and Y- Δ connections as in the single phase case
- See example 5.11 for details

Dr. Henry Louie

34



Per Unit Analysis Procedure (normal systems)

- Pick a VA base for the entire system (usually largest generator rating)
- Arbitrarily select one voltage base. Relate all others by the ratio of the magnitudes of the open-circuit line voltages of each transformer bank
- Find the impedance bases in the different sections and express all impedances in consistent per unit terms.
- Draw the impedance diagram for the entire system, and solve for the desired per unit quantities.
- Convert back to actual quantities, if needed.

Dr. Henry Louie

35