

14-Registers and Counters Part 2

Text: Unit 12

ECEGR/ISSC 201
Digital Operations and Computations
Winter 2011

Overview

- Binary Counter Design
- Counters for other Sequences
- Counter Design using S-R and J-K Flip-Flops

Dr. Louie 2

Counters

- Output changes state in a prescribed sequence when input pulses are received
 - Made from two or more flip-flops
- Consider synchronous counters
 - Common clock signal

Dr. Louie 3

Design of Binary Counters

- Consider three T flip-flops
- The output is read: CBA
 - Example: 001 if C = 0, B = 0 and A = 1
- Assume initially:
 - A = B = C = 0

Dr. Louie 4

Design of Binary Counters

- Recall that for T flip-flop
 - $Q^+ = T'Q + TQ' = T \oplus Q$

| T | Q | Q ⁺ |
|---|---|----------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Dr. Louie 5

Design of Binary Counters

- Output: 000
- After the first active edge
 - Output: 001

Dr. Louie 6

Design of Binary Counters

- Output: 001
- After the second active edge
 - Output: 010

Dr. Louie 7

Design of Binary Counters

- Output: 010
- After the third active edge
 - Output: 011

Dr. Louie 8

Design of Binary Counters

- Output: 011
- After the fourth active edge
 - Output: 100

Dr. Louie 9

Design of Binary Counters

- Counting continues in binary until output is 111
- What happens next?

Dr. Louie 10

Design of Binary Counters

- Output: 111
- After the eighth active edge

Dr. Louie 11

Design of Binary Counters

- Output: 111
- After the eighth active edge
 - Output: 000
- Sequence repeats

Dr. Louie 12

Design of Binary Counters

- Any time Q does not equal Q⁺, a 1 is applied to T

| C | B | A | C ⁺ | B ⁺ | A ⁺ | Flip-flop inputs | | |
|---|---|---|----------------|----------------|----------------|------------------|----------------|----------------|
| | | | | | | T _C | T _B | T _A |
| 0 | 0 | 0 | 0 | 0 | 1 | | | |
| 0 | 0 | 1 | 0 | 1 | 0 | | | |
| 0 | 1 | 0 | 0 | 1 | 1 | | | |
| 0 | 1 | 1 | 1 | 0 | 0 | | | |
| 1 | 0 | 0 | 1 | 0 | 1 | | | |
| 1 | 0 | 1 | 1 | 1 | 0 | | | |
| 1 | 1 | 0 | 1 | 1 | 1 | | | |
| 1 | 1 | 1 | 0 | 0 | 0 | | | |

Dr. Louie 13

Design of Binary Counters

- Any time Q does not equal Q⁺, a 1 is applied to T

| C | B | A | C ⁺ | B ⁺ | A ⁺ | Flip-flop inputs | | |
|---|---|---|----------------|----------------|----------------|------------------|----------------|----------------|
| | | | | | | T _C | T _B | T _A |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |

Dr. Louie 14

Design of Binary Counters

- Derivation of T_C, T_B, T_A from the K-map

T_C

T_B

T_A

Dr. Louie 15

Design of Binary Counters

- T_C = AB
- T_B = A
- T_A = 1

T_C

T_B

T_A

Dr. Louie 16

Design of Binary Counters

- These equations match our circuit
- T_C = AB
- T_B = A
- T_A = 1

Dr. Louie 17

Design of Binary Counters

- How else could we design this counter?
- Try using D flip-flops

| C | B | A | C ⁺ | B ⁺ | A ⁺ | Flip-flop inputs | | |
|---|---|---|----------------|----------------|----------------|------------------|----------------|----------------|
| | | | | | | D _C | D _B | D _A |
| 0 | 0 | 0 | 0 | 0 | 1 | | | |
| 0 | 0 | 1 | 0 | 1 | 0 | | | |
| 0 | 1 | 0 | 0 | 1 | 1 | | | |
| 0 | 1 | 1 | 1 | 0 | 0 | | | |
| 1 | 0 | 0 | 1 | 0 | 1 | | | |
| 1 | 0 | 1 | 1 | 1 | 0 | | | |
| 1 | 1 | 0 | 1 | 1 | 1 | | | |
| 1 | 1 | 1 | 0 | 0 | 0 | | | |

Dr. Louie 18

Design of Binary Counters

- Construct the K-maps for the flip-flop inputs

| Flip-flop inputs | | | | | | | | |
|------------------|---|---|----------------|----------------|----------------|----------------|----------------|----------------|
| C | B | A | C ⁺ | B ⁺ | A ⁺ | D _C | D _B | D _A |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |

Dr. Louie 19

Design of Binary Counters

- $D_C = C^+ = C'BA + CB' + CA'$
 $D_B = B^+ = B'A + BA'$
 $D_A = A^+ = A'$

Dr. Louie 20

Design of Binary Counters

- We could build the circuit directly from these equations, but there is a more elegant solution
- $D_C = C^+ = C'BA + CB' + CA'$
 $D_B = B^+ = B'A + BA'$
 $D_A = A^+ = A'$

Dr. Louie 21

Design of Binary Counters

- We could build the circuit directly from these equations, but there is a more elegant solution
- $D_C = C^+ = C'BA + CB' + CA' = AB \text{ XOR } C$
 $D_B = B^+ = B'A + BA' = A \text{ XOR } B$
 $D_A = A^+ = A' = 1 \text{ XOR } A$
- We can simply place XOR in front of the D Flip-flops and use the circuit from the T flip-flop

Dr. Louie 22

Design of Binary Counters

- Using D flip-flops

Dr. Louie 23

Up-Down Counter

- Binary Up-Down Counter
 - Inputs U, D
 - If U = 1, D = 0
 - Sequence is 000, 001, 010, 011, 100 and so on (repeats after 111)
 - If D = 1, U = 0
 - Sequence is 111, 110, 101, 100 and so on (repeats after 000)
 - If D = 0, U = 0
 - Output does not change
 - D = 1, U = 1 is not allowed

Dr. Louie 24

Up-Down Counter

- State graph
 - U = (1 outer loop)
 - D = (1 inner loop)

Dr. Louie 25

Up-Down Counter

- Let's implement using D flip-flops

| C | B | A | Up | | | Down | | |
|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|
| | | | C ⁺ | B ⁺ | A ⁺ | C ⁻ | B ⁻ | A ⁻ |
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |

Dr. Louie 26

Up-Down Counter

- When U = 1 and D = 0
 - $D_A = A^+ = A'$
 - $D_B = B^+ = BA' + B'A = B \oplus A$
 - $D_C = C^+ = C'AB + CB'A' + CB'A + CBA' = C'AB + CB' + CA' = C'BA + C(BA)' = C \oplus (BA)$

Dr. Louie 27

Up-Down Counter

- When U = 0 and D = 1
 - $D_A = A^+ = A'$
 - $D_B = B^+ = B \oplus A'$
 - $D_C = C^+ = C \oplus B'A'$
- In general:
 - $D_A = A^+ = A \oplus (U+D)$
 - $D_B = B^+ = B \oplus (UA+DA')$
 - $D_C = C^+ = C \oplus (UBA+DB'A')$

Dr. Louie 28

Up-Down Counter

Dr. Louie 29

Counters for Other Sequences

- Some applications call for counters that are not in ascending or descending binary order
- Consider the following state graph
- Construct a counter using T flip-flops

Dr. Louie 30

Counters for Other Sequences

| C | B | A | C ⁺ | B ⁺ | A ⁺ |
|---|---|---|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | - | - | - |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | - | - | - |
| 1 | 1 | 0 | - | - | - |
| 1 | 1 | 1 | 0 | 1 | 0 |

31

Counters for Other Sequences

- We could design a circuit using T flip-flops directly from the next state table as we have done previously
- Better approach is to examine the next-state K-maps

32

Counters for Other Sequences

- Resulting next-state K-maps

| | | |
|----|----|-----|
| C | 0 | 1 |
| BA | 00 | 01 |
| | 00 | 1 1 |
| | 01 | X X |
| | 11 | 0 0 |
| | 10 | 0 X |

C⁺

| | | |
|----|----|-----|
| C | 0 | 1 |
| BA | 00 | 01 |
| | 00 | 0 1 |
| | 01 | X X |
| | 11 | 0 1 |
| | 10 | 1 X |

B⁺

| | | |
|----|----|-----|
| C | 0 | 1 |
| BA | 00 | 01 |
| | 00 | 0 1 |
| | 01 | X X |
| | 11 | 0 0 |
| | 10 | 1 X |

A⁺

33

Counters for Other Sequences

- What must the T_C K-map look like to realize this?
- Begin by examining the C and C⁺ relationship
- Whenever C changes state, a 1 to the T_C must be applied

| | | |
|----|----|-----|
| C | 0 | 1 |
| BA | 00 | 01 |
| | 00 | 1 1 |
| | 01 | X X |
| | 11 | 0 0 |
| | 10 | 0 X |

C⁺

| | | |
|----|----|----|
| C | 0 | 1 |
| BA | 00 | 01 |
| | 00 | |
| | 01 | |
| | 11 | |
| | 10 | |

T_C

34

Counters for Other Sequences

- Consider C=B=A=0; the next state C⁺ is 1
 - This is a change in state, so a 1 must be applied to T_C for the state to change

| | | |
|----|----|-----|
| C | 0 | 1 |
| BA | 00 | 01 |
| | 00 | 1 1 |
| | 01 | X X |
| | 11 | 0 0 |
| | 10 | 0 X |

C⁺

| | | |
|----|----|----|
| C | 0 | 1 |
| BA | 00 | 01 |
| | 00 | 1 |
| | 01 | |
| | 11 | |
| | 10 | |

T_C

35

Counters for Other Sequences

- Consider C= 1, B=A=0; the next state C⁺ is 1
 - No change in state so the input to T_C must be 0

| | | |
|----|----|-----|
| C | 0 | 1 |
| BA | 00 | 01 |
| | 00 | 1 1 |
| | 01 | X X |
| | 11 | 0 0 |
| | 10 | 0 X |

C⁺

| | | |
|----|----|-----|
| C | 0 | 1 |
| BA | 00 | 01 |
| | 00 | 1 0 |
| | 01 | |
| | 11 | |
| | 10 | |

T_C

36

Counters for Other Sequences

- Consider $C = 0, B=A=1$; what should the input to T_C be?

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 1 | |
| 01 | X | X | |
| 11 | 0 | 0 | |
| 10 | 0 | X | |

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 0 | |
| 01 | | | |
| 11 | | | |
| 10 | | | |

C^+ T_C

Dr. Louie 37

Counters for Other Sequences

- Consider $C = 0, B=A=1$; what should the input to T_C be?
 - No change, so T_C should be 0

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 1 | |
| 01 | X | X | |
| 11 | 0 | 0 | |
| 10 | 0 | X | |

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 0 | |
| 01 | | | |
| 11 | 0 | | |
| 10 | | | |

C^+ T_C

Dr. Louie 38

Counters for Other Sequences

- Consider $C = B=A=1$; what should the input to T_C be?

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 1 | |
| 01 | X | X | |
| 11 | 0 | 0 | |
| 10 | 0 | X | |

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 0 | |
| 01 | | | |
| 11 | 0 | | |
| 10 | | | |

C^+ T_C

Dr. Louie 39

Counters for Other Sequences

- Consider $C = B=A=1$; what should the input to T_C be?
 - $C^+ = 0$, so a change occurs,

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 1 | |
| 01 | X | X | |
| 11 | 0 | 0 | |
| 10 | 0 | X | |

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 0 | |
| 01 | | | |
| 11 | 0 | 1 | |
| 10 | | | |

C^+ T_C

Dr. Louie 40

Counters for Other Sequences

- Completing the map

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 1 | |
| 01 | X | X | |
| 11 | 0 | 0 | |
| 10 | 0 | X | |

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 0 | |
| 01 | X | X | |
| 11 | 0 | 1 | |
| 10 | 0 | X | |

C^+ T_C

Dr. Louie 41

Counters for Other Sequences

- Finding the characteristic equation
 - $T_C = C'B' + CB$

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 1 | |
| 01 | X | X | |
| 11 | 0 | 0 | |
| 10 | 0 | X | |

| | | | |
|----|---|---|---|
| | C | 0 | 1 |
| BA | 0 | 1 | 1 |
| 00 | 1 | 0 | |
| 01 | X | X | |
| 11 | 0 | 1 | |
| 10 | 0 | X | |

C^+ T_C

Dr. Louie 42

Counters for Other Sequences

- Find the simplified SoP equations for T_B and T_A

| | | | |
|----|---|----|-----|
| | | C | |
| | | BA | 0 1 |
| 00 | 0 | 1 | |
| 01 | X | X | |
| 11 | 0 | 1 | |
| 10 | 1 | X | |

| | | | |
|----|--|----|-----|
| | | C | |
| | | BA | 0 1 |
| 00 | | | |
| 01 | | | |
| 11 | | | |
| 10 | | | |

| | | | |
|----|---|----|-----|
| | | C | |
| | | BA | 0 1 |
| 00 | 0 | 1 | |
| 01 | X | X | |
| 11 | 0 | 0 | |
| 10 | 1 | X | |

| | | | |
|----|--|----|-----|
| | | C | |
| | | BA | 0 1 |
| 00 | | | |
| 01 | | | |
| 11 | | | |
| 10 | | | |

B^+
 T_B
 A^+
 T_A

Dr. Louie 43

Counters for Other Sequences

- Find the simplified SoP equations for T_B and T_A
 - $T_B = C'A + CB'$

| | | | |
|----|---|----|-----|
| | | C | |
| | | BA | 0 1 |
| 00 | 0 | 1 | |
| 01 | X | X | |
| 11 | 0 | 1 | |
| 10 | 1 | X | |

| | | | |
|----|---|----|-----|
| | | C | |
| | | BA | 0 1 |
| 00 | 0 | 1 | |
| 01 | X | X | |
| 11 | 1 | 0 | |
| 10 | 0 | X | |

B^+
 T_B

Dr. Louie 44

Counters for Other Sequences

- Find the simplified SoP equations for T_B and T_A
 - $T_C = C'B' + CB$
 - $T_B = C'A + CB'$
 - $T_A = C + B$

| | | | |
|----|---|----|-----|
| | | C | |
| | | BA | 0 1 |
| 00 | 0 | 1 | |
| 01 | X | X | |
| 11 | 0 | 0 | |
| 10 | 1 | X | |

| | | | |
|----|---|----|-----|
| | | C | |
| | | BA | 0 1 |
| 00 | 0 | 1 | |
| 01 | X | X | |
| 11 | 1 | 1 | |
| 10 | 1 | X | |

A^+
 T_A

Dr. Louie 45

Counters for Other Sequences

- Circuit realization (feedback loops not shown)
 - $T_C = C'B' + CB$ (XOR can also be used)
 - $T_B = C'A + CB'$
 - $T_A = C + B$

Dr. Louie 46

Counters for Other Sequences

- Some pitfalls
 - The state graph does not describe what happens for three states
 - When the circuit is turned on, the states are random
 - It should be checked that these states transition into the sequence, once there it should never leave

Dr. Louie 47

Counters for Other Sequences

- For example: 001
 - $T_C = C'B' + CB = 1 \Rightarrow$ change $C^+ = 1$
 - $T_B = C'A + CB' = 1 \Rightarrow$ change $B^+ = 1$
 - $T_A = C + B = 0 \Rightarrow$ no change $A^+ = 1$

Dr. Louie 48

Counter Design Using D Flip-Flops

- Design using D flip-flops is simple
- Consider the same state graph previously considered
 - $D_C = C^+$

Dr. Louie 49

Counter Design Using D Flip-Flops

- Design using D flip-flops is simple
- Consider the same state graph previously considered
 - $D_C = C^+$

Dr. Louie 50

Counter Design Using D Flip-Flops

- For the other D flip-flops
 - $D_B = B^+ = C + BA'$
 - $D_A = A^+ = CA' + BA' = A'(C+B)$

Dr. Louie 51

Counter Design Using D Flip-Flops

- Draw the resulting circuit
 - $D_C = C^+ = B'$
 - $D_B = B^+ = C + BA'$
 - $D_A = A^+ = CA' + BA' = A'(C+B)$

Dr. Louie 52

Counter Design Using D Flip-Flops

Dr. Louie 53

Counter Design Using S-R and J-K Flip-Flops

- We next examine counter design using S-R and J-K flip-flops
- Recall for an S-R flip-flop

| S | R | Q | Q ⁺ |
|---|---|---|----------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | - |
| 1 | 1 | 1 | - |

Dr. Louie 54

Counter Design Using S-R and J-K Flip-Flops

- Design approach is similar to T and D flip-flops but now there are two inputs S and R

| Q | Q ⁺ | S | R |
|---|----------------|---|---|
| 0 | 0 | 0 | 0 |
| | | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 |
| | | 1 | 0 |

=>

| Q | Q ⁺ | S | R |
|---|----------------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | X | 0 |

Dr. Louie 55

Counter Design Using S-R and J-K Flip-Flops

- Consider C⁺

| C | B | A | C ⁺ | B ⁺ | A ⁺ | S _C | R _C |
|---|---|---|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | | |
| 0 | 0 | 1 | - | - | - | | |
| 0 | 1 | 0 | 0 | 1 | 1 | | |
| 0 | 1 | 1 | 0 | 0 | 0 | | |
| 1 | 0 | 0 | 1 | 1 | 1 | | |
| 1 | 0 | 1 | - | - | - | | |
| 1 | 1 | 0 | - | - | - | | |
| 1 | 1 | 1 | 0 | 1 | 0 | | |

Dr. Louie 56

Counter Design Using S-R and J-K Flip-Flops

- Consider C⁺

| C | B | A | C ⁺ | B ⁺ | A ⁺ | S _C | R _C |
|---|---|---|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | - | - | - | X | X |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | X |
| 1 | 0 | 0 | 1 | 1 | 1 | X | 0 |
| 1 | 0 | 1 | - | - | - | X | X |
| 1 | 1 | 0 | - | - | - | X | X |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |

Dr. Louie 57

Counter Design Using S-R and J-K Flip-Flops

- Next consider B⁺

| C | B | A | C ⁺ | B ⁺ | A ⁺ | S _C | R _C | S _B | R _B |
|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | X |
| 0 | 0 | 1 | - | - | - | X | X | X | X |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X | X | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | X | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 | X | 0 | 1 | 0 |
| 1 | 0 | 1 | - | - | - | X | X | X | X |
| 1 | 1 | 0 | - | - | - | X | X | X | X |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | X | 0 |

Dr. Louie 58

Counter Design Using S-R and J-K Flip-Flops

- Finally, consider A⁺

| C | B | A | C ⁺ | B ⁺ | A ⁺ | S _C | R _C | S _B | R _B | S _A | R _A |
|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | X | 0 | X |
| 0 | 0 | 1 | - | - | - | X | X | X | X | X | X |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X | X | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | X | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | X | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | - | - | - | X | X | X | X | X | X |
| 1 | 1 | 0 | - | - | - | X | X | X | X | X | X |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | X | 0 | 0 | 1 |

Dr. Louie 59

Counter Design Using S-R and J-K Flip-Flops

- We could build directly from the next state table, but it is easier to use next state K-maps

Dr. Louie 60

Counter Design Using S-R and J-K Flip-Flops

- Need an S and R for each next state
- Do not let 1s (or Don't Cares taken as 1s) to overlap between S and R
- $S = B'$; $R = A$

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 1 | 1 |
| 01 | | X | X |
| 11 | | 0 | 0 |
| 10 | | 0 | X |
| | | C ⁺ | |

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 1 | X |
| 01 | | X | X |
| 11 | | 0 | 0 |
| 10 | | 0 | X |
| | | S _C | |

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 0 |
| 01 | | X | X |
| 11 | | X | 1 |
| 10 | | X | X |
| | | R _C | |

Dr. Louie 61

Counter Design Using S-R and J-K Flip-Flops

- Complete for B⁺ and A⁺

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 1 |
| 01 | | X | X |
| 11 | | 0 | 1 |
| 10 | | 1 | X |
| | | B ⁺ | |

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 1 |
| 01 | | X | X |
| 11 | | 0 | 0 |
| 10 | | 1 | X |
| | | A ⁺ | |

Dr. Louie 62

Counter Design Using S-R and J-K Flip-Flops

- Complete for B⁺ and A⁺
- $S_B = C$
- $R_B = C'A$

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 1 |
| 01 | | X | X |
| 11 | | 0 | 1 |
| 10 | | 1 | X |
| | | B ⁺ | |

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 1 |
| 01 | | X | X |
| 11 | | 0 | X |
| 10 | | X | X |
| | | S _B | |

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | X | 0 |
| 01 | | X | X |
| 11 | | 1 | 0 |
| 10 | | 0 | X |
| | | R _B | |

Dr. Louie 63

Counter Design Using S-R and J-K Flip-Flops

- Complete for B⁺ and A⁺
- $S_B = CA' + BA' = A'(C+B)$
- $R_B = A$

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 1 |
| 01 | | X | X |
| 11 | | 0 | 0 |
| 10 | | 1 | X |
| | | A ⁺ | |

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 1 |
| 01 | | X | X |
| 11 | | 0 | 0 |
| 10 | | 1 | X |
| | | S _A | |

| | | | |
|----|--|----------------|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | X | 0 |
| 01 | | X | X |
| 11 | | 1 | 1 |
| 10 | | 0 | X |
| | | R _A | |

Dr. Louie 64

Counter Design Using S-R and J-K Flip-Flops

- Circuit realization

Dr. Louie 65

Counter Design Using S-R and J-K Flip-Flops

- Now using J-K flip-flops

| J | K | Q | Q ⁺ |
|---|---|---|----------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

=>

| Q | Q ⁺ | J | K |
|---|----------------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

Dr. Louie 66

Counter Design Using S-R and J-K Flip-Flops

- Consider C⁺

| C | B | A | C ⁺ | B ⁺ | A ⁺ | J _C | K _C |
|---|---|---|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | | |
| 0 | 0 | 1 | - | - | - | | |
| 0 | 1 | 0 | 0 | 1 | 1 | | |
| 0 | 1 | 1 | 0 | 0 | 0 | | |
| 1 | 0 | 0 | 1 | 1 | 1 | | |
| 1 | 0 | 1 | - | - | - | | |
| 1 | 1 | 0 | - | - | - | | |
| 1 | 1 | 1 | 0 | 1 | 0 | | |

Dr. Louie 67

Counter Design Using S-R and J-K Flip-Flops

- Consider C⁺

| C | B | A | C ⁺ | B ⁺ | A ⁺ | J _C | K _C |
|---|---|---|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | X |
| 0 | 0 | 1 | - | - | - | X | X |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | X |
| 1 | 0 | 0 | 1 | 1 | 1 | X | 0 |
| 1 | 0 | 1 | - | - | - | X | X |
| 1 | 1 | 0 | - | - | - | X | X |
| 1 | 1 | 1 | 0 | 1 | 0 | X | 1 |

Dr. Louie 68

Counter Design Using S-R and J-K Flip-Flops

- Next consider B⁺

| C | B | A | C ⁺ | B ⁺ | A ⁺ | J _C | K _C | J _B | K _B |
|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | X | 0 | X |
| 0 | 0 | 1 | - | - | - | X | X | X | X |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X | X | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | X | X | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | X | X | 1 | X |
| 1 | 0 | 1 | - | - | - | X | X | X | X |
| 1 | 1 | 0 | - | - | - | X | X | X | X |
| 1 | 1 | 1 | 0 | 1 | 0 | X | 1 | X | 0 |

Dr. Louie 69

Counter Design Using S-R and J-K Flip-Flops

- Finally, consider A⁺

| C | B | A | C ⁺ | B ⁺ | A ⁺ | J _C | K _C | J _B | K _B | J _A | K _A |
|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | X | 0 | X | 0 | X |
| 0 | 0 | 1 | - | - | - | X | X | X | X | X | X |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X | X | 0 | 1 | X |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | X | X | 1 | X | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | X | 0 | 1 | X | 1 | X |
| 1 | 0 | 1 | - | - | - | X | X | X | X | X | X |
| 1 | 1 | 0 | - | - | - | X | X | X | X | X | X |
| 1 | 1 | 1 | 0 | 1 | 0 | X | 1 | X | 0 | X | 1 |

Dr. Louie 70

Counter Design Using S-R and J-K Flip-Flops

- Need a J and K for each next state
 - J_C = B⁺
 - K_C = A

| C | 0 | 1 |
|----|---|---|
| BA | | |
| 00 | 1 | 1 |
| 01 | X | X |
| 11 | 0 | 0 |
| 10 | 0 | X |

| C | 0 | 1 |
|----|---|---|
| BA | | |
| 00 | 1 | X |
| 01 | X | X |
| 11 | 0 | X |
| 10 | 0 | X |

| C | 0 | 1 |
|----|---|---|
| BA | | |
| 00 | X | 0 |
| 01 | X | X |
| 11 | X | 1 |
| 10 | X | X |

C⁺ J_C K_C

Dr. Louie 71

Counter Design Using S-R and J-K Flip-Flops

- Complete for B⁺ and A⁺

| C | 0 | 1 |
|----|---|---|
| BA | | |
| 00 | 0 | 1 |
| 01 | X | X |
| 11 | 0 | 1 |
| 10 | 1 | X |

| C | 0 | 1 |
|----|---|---|
| BA | | |
| 00 | 0 | 1 |
| 01 | X | X |
| 11 | 0 | 0 |
| 10 | 1 | X |

B⁺ A⁺

Dr. Louie 72

Counter Design Using S-R and J-K Flip-Flops

- Complete for B⁺ and A⁺
 - J_B = C
 - K_B = C'A

| | | | |
|----|--|---|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 1 |
| 01 | | X | X |
| 11 | | 0 | 1 |
| 10 | | 1 | X |

B⁺

| | | | |
|----|--|---|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 1 |
| 01 | | X | X |
| 11 | | X | X |
| 10 | | X | X |

J_B

| | | | |
|----|--|---|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | X | 0 |
| 01 | | X | X |
| 11 | | 1 | 0 |
| 10 | | 0 | X |

K_B

Dr. Louie 73

Counter Design Using S-R and J-K Flip-Flops

- Complete for B⁺ and A⁺
 - J_A = C
 - K_A = 1

| | | | |
|----|--|---|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 1 |
| 01 | | X | X |
| 11 | | 0 | 0 |
| 10 | | 1 | X |

A⁺

| | | | |
|----|--|---|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | 0 | 1 |
| 01 | | X | X |
| 11 | | X | X |
| 10 | | 1 | X |

J_A

| | | | |
|----|--|---|---|
| | | C | |
| BA | | 0 | 1 |
| 00 | | X | X |
| 01 | | X | X |
| 11 | | 1 | 1 |
| 10 | | X | X |

K_A

Dr. Louie 74

Counter Design Using S-R and J-K Flip-Flops

- Circuit realization

Dr. Louie 75