



15-System Model
Text: 5.8 – 5.11

ECEGR 451
Power Systems

Dr. Henry Louie

1

Topics

- One-line Diagram
- System Modeling
- Example
- Regulating Transformers


Dr. Henry Louie

2



One-Line Diagram

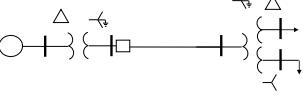- Generator
- Bus
- Transformer
- Transmission line
- Circuit breaker
- Load




3



One-Line Diagram

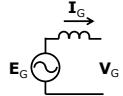- Simple generator model:
 \mathbf{V}_G : terminal voltage
 \mathbf{E}_G : open circuit voltage
 \mathbf{I}_G : generator current



4



System Model

- We've discussed transmission lines, transformers, per unit, one line diagrams
- Now we put them all together to model the system


Dr. Henry Louie

5



System Model

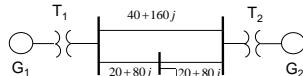- G_1 : 50 MVA, 12.2 kV, $X = 0.15$ p.u.
- G_2 : 20 MVA, 13.8 kV, $X = 0.15$ p.u.
- T_1 : 80 MVA 12.2/161 kV, $X = 0.10$ p.u.
- T_2 : 40 MVA 13.8/161 kV, $X = 0.10$ p.u.
- Load: 50 MVA, 0.80 PF (lagging), operating at 154 kV




Dr. Henry Louie

6



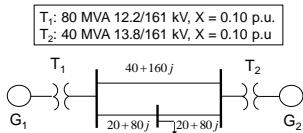1. Pick a power base for the system

- Common to select power base equal to or near the largest generator in the system
- Let $S_B = 100 \text{ MVA}$ (three phase)




Dr. Henry Louie

7

2a. Select voltage base

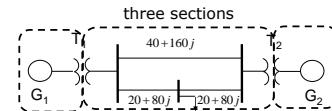- Common to select voltage base equal to or near the line-line voltage at any section
- Must keep track of voltage base and section
- Sections are separated by transformers
- Let $V_B = 132 \text{ kV}$ (line-line) at the transmission line section




Dr. Henry Louie

8



2b. Compute voltage bases for all sections

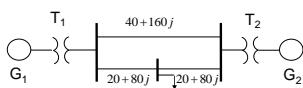- Use transformer ratios (line-line) to relate base voltages between sections
- G1 section: $V_{1B} = 132 \times (12.2/161) = 10.002 \text{ kV}$
- G2 section: $V_{2B} = 132 \times (13.8/161) = 11.31 \text{ kV}$




Dr. Henry Louie

9



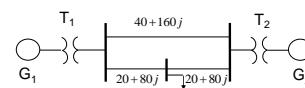3. Express all impedances in consistent p.u. terms

- All sections have same power bases, but different voltage bases
- Impedances are given with different power and voltage bases
- Convert using: $\mathbf{Z}_{\text{p.u.}}^{\text{new}} = \mathbf{Z}_{\text{p.u.}}^{\text{old}} \left(\frac{V_B^{\text{old}}}{V_B^{\text{new}}} \right)^2 \frac{S_B^{\text{new}}}{S_B^{\text{old}}}$



Dr. Henry Louie


10



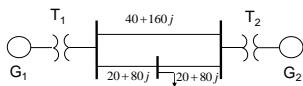3. Express all impedances in consistent p.u. terms

- $G_1: X = 0.15 \times (100/50) \times (12.2/10.002)^2 = 0.4463 \text{ p.u.}$
- $G_2: X = 0.15 \times (100/20) \times (13.8/11.31)^2 = 1.1166 \text{ p.u.}$
- $T_1: X = 0.1 \times (100/80) \times (12.2/10.002)^2 = 0.1 \times (100/80) \times (161/132)^2 = 0.18596 \text{ p.u.}$
- $T_2 = 0.1 \times (100/40) \times (13.8/11.31)^2 = 0.3719 \text{ p.u.}$

$$\mathbf{Z}_{\text{p.u.}}^{\text{new}} = \mathbf{Z}_{\text{p.u.}}^{\text{old}} \left(\frac{S_B^{\text{new}}}{S_B^{\text{old}}} \right) \left(\frac{V_B^{\text{old}}}{V_B^{\text{new}}} \right)^2$$




Dr. Henry Louie

11



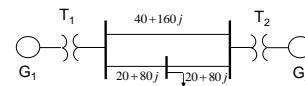3. Express all impedances in consistent p.u. terms

- The transmission line and load:
 - $Z_{3B} = (132)^2/100 = 174.24 \text{ p.u.}$
 - $\mathbf{Z}_{\text{line,a}} = (40 + j160)/174.24 = 0.2296 + j0.9183$
 - $\mathbf{Z}_{\text{line,b}} = (20 + j80)/174.24 = 0.1148 + j0.4591 \text{ p.u.}$
- and for the load:
 - $\mathbf{S} = 50(.8 + j.6) = 40 + 30j \text{ MVA}$
 - $\mathbf{Z}_{\text{load}} = \{(154)^2/(40 + 30j)\}^* = 379.456 + j284.529 = 2.18 + j1.63 \text{ p.u.}$




Dr. Henry Louie

12



4a. Draw the impedance diagram

- Redrawing the system

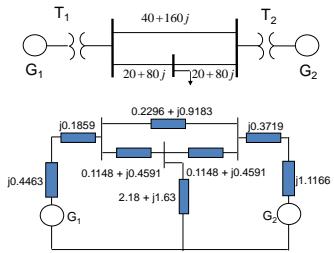


Dr. Henry Louie

13



4b. Solve for desired quantities

- Use per-phase analysis

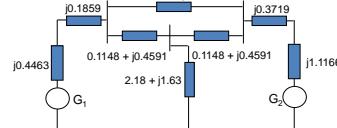


impedance diagram

Dr. Henry Louie

14



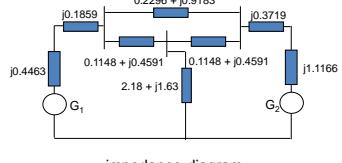5. Convert back to actual quantities, if needed



impedance diagram

Dr. Henry Louie

15




Example

- Specifications

- G_1 : 75 MVA, 10 kV, $X = 0.10$ p.u.
- G_2 : 75 MVA, 22 kV, $X = 0.08$ p.u.
- T_1 : 75 MVA 10/365 kV, $X = 0.12$ p.u.
- T_2 : 80 MVA 24/380 kV, $X = 0.14$ p.u.
- Load: $I_{\text{load}} = 118.6 \angle -10^\circ$ A
- $E_{G2} = 25 \angle 0^\circ$ kV

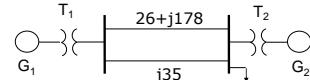- Choose $V_B = 365$ kV at the transmission line and $S_B = 75$ MVA



Dr. Henry Louie

16




Example

- Section base voltages:

$$V_{B3} = 365\text{kV}$$

$$V_{B1} = 10\text{kV}$$

$$V_{B2} = 23.05\text{kV}$$

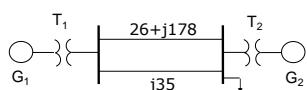

Dr. Henry Louie

17



Example

- New generator impedances

$$Z_{\text{p.u.}}^{\text{new}} = Z_{\text{p.u.}}^{\text{old}} \left(\frac{V_B^{\text{old}}}{V_B^{\text{new}}} \right)^2 S_B^{\text{new}} / S_B^{\text{old}}$$

$$X_{G1} = 0.1 \left(\frac{10}{365} \right)^2 \frac{75}{75} = 0.1$$

$$X_{G2} = 0.08 \left(\frac{22}{23.05} \right)^2 \frac{75}{75} = 0.073$$

Dr. Henry Louie

18



Example

- New transformer impedances

$$\mathbf{Z}_{\text{p.u.}}^{\text{new}} = \mathbf{Z}_{\text{p.u.}}^{\text{old}} \left(\frac{V_B^{\text{old}}}{V_B^{\text{new}}} \right)^2 \frac{S_B^{\text{new}}}{S_B^{\text{old}}}$$

$$X_{T_1} = 0.12 \left(\frac{10}{10} \right)^2 \frac{75}{75} = 0.12$$

$$X_{T_2} = 0.14 \left(\frac{24}{23.05} \right)^2 \frac{80}{75} = 0.1423$$

Dr. Henry Louie

19

Example

- Transmission line impedance in p.u.

$$Z_B = \frac{V_B^2}{S_B} = \frac{365k^2}{75M} = 1776.3\Omega$$

$$\mathbf{Z}_{L1} = \frac{26 + j178}{1776.3} = 0.015 + j0.1$$

$$\mathbf{Z}_{L2} = \frac{j35}{1776.3} = j0.02$$

Dr. Henry Louie

20



Example

- Load current and generator 2 voltage

$$I_B = \frac{S_B}{\sqrt{3}V_B} = 118.6A$$

$$I_{\text{Load}} = \frac{118.6 \angle -10^\circ}{I_B} = 1 \angle -10^\circ$$

$$E_{G2} = \frac{25 \angle 0^\circ}{23.05} = 1.08 \angle 0^\circ$$


Dr. Henry Louie

21



Example

- Impedance diagram with sources

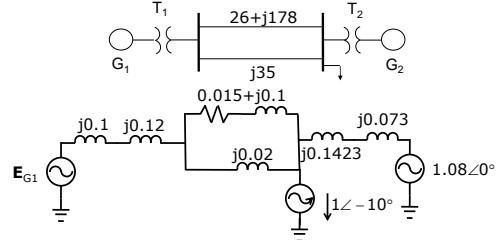

Dr. Henry Louie

22



Regulating Transformers

- We can now describe the system model in per unit with the impedance diagram
- We have seen that using per unit on normal systems, we have eliminated the transformers
- However, this is not a general result as there are some transformers that do not "disappear" when per unit normalization is used
 - regulating and off-nominal transformers

Dr. Henry Louie

23




Regulating Transformers

- Transformers used to adjust voltage magnitude or phase are called "regulating transformers"
- They do this by adding a small amount (+ or - 10 %) of voltage to the line or phase voltages
- Voltage can also be changed by adjusting the turns ratio of the transformer (called tap changing)
- Tap changing may be automatic and may occur while the transformer is energized (load-tap-changing)

Dr. Henry Louie

24

Regulating Transformers

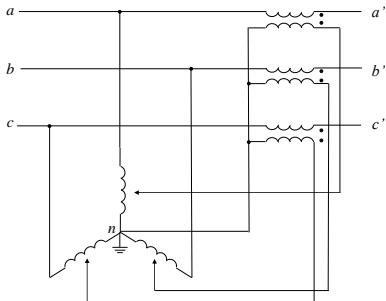


Dr. Henry Louie

25

Regulating Transformer
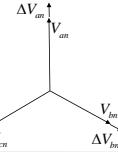
$$\begin{aligned}\mathbf{V}_{a'n} &= \mathbf{V}_{an} + \Delta\mathbf{V}_{an} \\ \mathbf{V}_{b'n} &= \mathbf{V}_{bn} + \Delta\mathbf{V}_{bn} \\ \mathbf{V}_{c'n} &= \mathbf{V}_{cn} + \Delta\mathbf{V}_{cn}\end{aligned}$$




voltage magnitude increase

Dr. Henry Louie

26

Phase-Shifting Transformer

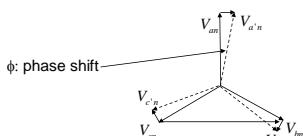- Basic idea: add a voltage that is 90 degrees out of phase
 $\mathbf{V}_{bc} = \sqrt{3}\mathbf{V}_{an} e^{\frac{-j\pi}{2}}$ $\mathbf{V}_{a'n} = \mathbf{V}_{an} \left(1 + p\sqrt{3}e^{\frac{-j\pi}{2}}\right) = \mathbf{V}_{an} \left(1 - jp\sqrt{3}\right)$
- Phase shift, and small voltage magnitude change occur




Dr. Henry Louie

27

Off-Nominal Turns Ratio

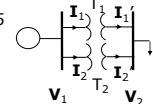- Consider two transformers in parallel with different ratios
- Assume system is per unit normalized to T_1 ratio, n
 - T_1 disappears from the impedance circuit
 - assume T_2 has the ratio n' (off-nominal)
 - define: $\bar{n} = n'/n$
- T_1 : $X = 0.2$
- T_2 : $X = 0.4$, n' is such that $\bar{n} = 1.05$
- Load:
 $\mathbf{V}_2 = 1\angle 0^\circ$
 $\mathbf{I}_{load} = 1.05\angle -45^\circ$




Dr. Henry Louie

28

Off-Nominal Turns Ratio

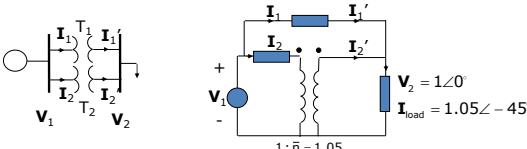- T_2 does not disappear from the circuit, we must include it using a transformer model
- How does arrangement affect power flows through each transformer?




Dr. Henry Louie

29

Off-Nominal Turns Ratio

- Using KVL and KCL:
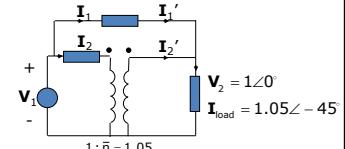
$$\begin{aligned}\mathbf{I}_1 + \mathbf{I}_2 &= 1.05\angle -45^\circ \\ \mathbf{V}_1 &= 1\angle 0^\circ + j0.2\mathbf{I}_1 = \frac{1}{1.05} \angle 0^\circ + j0.4(1.05\mathbf{I}_2) \\ &= -j0.2\mathbf{I}_1 + j0.42\mathbf{I}_2 = 0.0476 \\ \mathbf{I}_1 &= 0.5030 - j0.4262 \\ \mathbf{I}_2 &= 0.2395 - j0.3163\end{aligned}$$




Dr. Henry Louie

30



Off-Nominal Turns Ratio

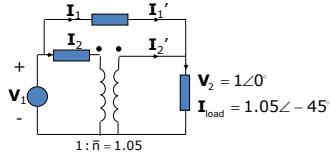- Finding the power:
 $\mathbf{S}_{t_1} = \mathbf{V}_1 \mathbf{I}_1^* = 0.5030 + j0.4262$
 $\mathbf{S}_{t_2} = \mathbf{V}_2 \mathbf{I}_2^* = 0.2395 + j0.3163$
- If the turns ratios were the same:
 $\mathbf{S}_{t_1} = 0.4950 + j0.4950$ note the large
 $\mathbf{S}_{t_2} = 0.2475 + j0.2475$ affect on VARS



Dr. Henry Louie

31



Summary

- The system model procedure discussed takes a one line diagram of a power system and produces an impedance diagram
 - per unit is convenient and lends itself to three phase or single phase quantities
 - most transformers disappear from the system
- Regulating transformers can be used to adjust real and reactive power flows through the system
- Next lecture we begin to focus on two other representations of the system using network matrices

Dr. Henry Louie

32