

## 17-Network Matrices

Text: 9

ECEGR 451  
Power Systems

Dr. Henry Louie

1

## Topics

- Component Modeling
  - Short Transmission Line
  - Medium/Long Transmission Line
  - Off-Nominal Transformer
- Ybus
  - Network Solution
  - Generator Modeling
  - Matlab
  - Network Reduction

Dr. Henry Louie

## Network Matrices

- We use matrices because power systems are large
- Convenient to express voltage and current relationships in matrices
  - computationally efficient
  - lends itself to computer implementation
  - will be used later in power flow analysis

Dr. Henry Louie

## Bus Admittance Matrix

- Goal: express network voltage and current relationships as  $\mathbf{I} = \mathbf{Y}_{\text{bus}} \mathbf{V}$  where:
  - $\mathbf{I}$  is a column matrix of node current injections (not identity matrix)
  - $\mathbf{Y}_{\text{bus}}$  is the admittance matrix
  - $\mathbf{V}$  is a column matrix of node voltages
- Each component element of the interconnected network is a **branch** (even connections to ground)
- Branches are modeled as an admittance  $\mathbf{y}$  (primitive admittance), or impedance  $\mathbf{z}$  (primitive impedance)

Dr. Henry Louie

## Notation Change

- Previously:
  - $\mathbf{z}$ : impedance per length (e.g.  $\Omega/\text{m}$ )
  - $\mathbf{y}$ : admittance per length (e.g.  $\text{S}/\text{m}$ )
- Hereafter:
  - $\mathbf{z}$ : impedance in per unit (length accounted for)
  - $\mathbf{y}$ : admittance in per unit (length accounted for)


$$\mathbf{y} = \frac{1}{\mathbf{z}}$$

Dr. Henry Louie

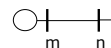
## Short Line

- Consider the 2-bus system
- Transmission line a:
  - short model with series impedance =  $\mathbf{z}_a$  or series admittance =  $\mathbf{y}_a$

$$\mathbf{y}_a = \frac{1}{\mathbf{z}_a} \quad \text{Do not confuse series admittance with shunt admittance}$$



Dr. Henry Louie



### Short Line


Analyzing the circuit:

$$\mathbf{I}_m = \frac{\mathbf{V}_m - \mathbf{V}_n}{\mathbf{z}_a} = \mathbf{y}_a \mathbf{V}_m - \mathbf{y}_a \mathbf{V}_n$$


$$\mathbf{I}_n = -\mathbf{y}_a \mathbf{V}_m + \mathbf{y}_a \mathbf{V}_n$$

In matrix form:

$$\begin{bmatrix} \mathbf{I}_m \\ \mathbf{I}_n \end{bmatrix} = \begin{bmatrix} \mathbf{y}_a & -\mathbf{y}_a \\ -\mathbf{y}_a & \mathbf{y}_a \end{bmatrix} \begin{bmatrix} \mathbf{V}_m \\ \mathbf{V}_n \end{bmatrix}$$
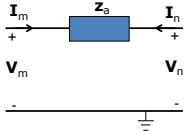
$$\mathbf{I} = \mathbf{Y}_{bus} \mathbf{V}$$


Dr. Henry Louie




### Notation

- $\mathbf{y}_a$  is the branch admittance
- Diagonal elements are self-admittances
- $Y_{jk}$  : refers to the element in the  $\mathbf{Y}_{bus}$  matrix located in the  $j^{\text{th}}$  row,  $k^{\text{th}}$  column

$$\begin{bmatrix} \mathbf{I}_m \\ \mathbf{I}_n \end{bmatrix} = \begin{bmatrix} \mathbf{y}_a & -\mathbf{y}_a \\ -\mathbf{y}_a & \mathbf{y}_a \end{bmatrix} \begin{bmatrix} \mathbf{V}_m \\ \mathbf{V}_n \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{I}_m \\ \mathbf{I}_n \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_m \\ \mathbf{V}_n \end{bmatrix}$$

Dr. Henry Louie




### Observations

- In general:
  - $\mathbf{Y}_{bus}$  is symmetric
  - $Y_{ii}$ , self-admittances are equal to sum of all the elements connected to that node
  - $Y_{ij}$  is equal to the negative of the primitive admittance of all components connected between node  $i$  and  $j$

$$\begin{bmatrix} \mathbf{I}_m \\ \mathbf{I}_n \end{bmatrix} = \begin{bmatrix} \mathbf{y}_a & -\mathbf{y}_a \\ -\mathbf{y}_a & \mathbf{y}_a \end{bmatrix} \begin{bmatrix} \mathbf{V}_m \\ \mathbf{V}_n \end{bmatrix} \quad \begin{bmatrix} \mathbf{I}_m \\ \mathbf{I}_n \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_m \\ \mathbf{V}_n \end{bmatrix}$$

Dr. Henry Louie




### Medium/Long Line

Analyzing the circuit:


$$\mathbf{I}_m = \mathbf{V}_m \left( \mathbf{y}_a + \frac{\mathbf{y}_{shunt}}{2} \right) - \mathbf{y}_a \mathbf{V}_n$$

$$\mathbf{I}_n = -\mathbf{y}_a \mathbf{V}_m + \left( \mathbf{y}_a + \frac{\mathbf{y}_{shunt}}{2} \right) \mathbf{V}_n$$

In matrix form:
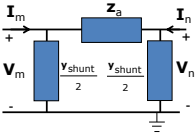
$$\begin{bmatrix} \mathbf{I}_m \\ \mathbf{I}_n \end{bmatrix} = \begin{bmatrix} \left( \mathbf{y}_a + \frac{\mathbf{y}_{shunt}}{2} \right) & -\mathbf{y}_a \\ -\mathbf{y}_a & \left( \mathbf{y}_a + \frac{\mathbf{y}_{shunt}}{2} \right) \end{bmatrix} \begin{bmatrix} \mathbf{V}_m \\ \mathbf{V}_n \end{bmatrix}$$


Dr. Henry Louie




### Medium/Long Line

- Diagonal element  $Y_{ii}$ : add the primitive admittances of all branches connected to node  $i$
- Off-diagonal element  $Y_{ij}$ : **negative** of the primitive admittance connecting  $i$  and  $j$

$$\begin{bmatrix} \mathbf{I}_m \\ \mathbf{I}_n \end{bmatrix} = \begin{bmatrix} \left( \mathbf{y}_a + \frac{\mathbf{y}_{shunt}}{2} \right) & -\mathbf{y}_a \\ -\mathbf{y}_a & \left( \mathbf{y}_a + \frac{\mathbf{y}_{shunt}}{2} \right) \end{bmatrix} \begin{bmatrix} \mathbf{V}_m \\ \mathbf{V}_n \end{bmatrix}$$

Dr. Henry Louie



### Example

A transmission line connects Bus 1 and Bus 2 with the following parameters:  $z = 0.01 + j0.1$  and  $\mathbf{y}_{shunt} = j0.15$ . Find  $\mathbf{Y}_{bus}$ .

Dr. Henry Louie

### Example

A transmission line connects Bus 1 and Bus 2 with the following parameters:  $z = 0.01 + j0.1$  and  $y_{shunt} = j0.15$ . Find  $Y_{bus}$ .

$$y = \frac{1}{z} = 0.99 - j9.90$$

$$\frac{y_{shunt}}{2} = j0.075$$

$$Y_{11} = Y_{22} = y + \frac{y_{shunt}}{2} = 0.99 - j9.825$$

$$Y_{12} = Y_{21} = -y = -0.99 + j9.90$$

$$Y_{Bus} = \begin{bmatrix} 0.99 - j9.825 & -0.99 + j9.90 \\ -0.99 + j9.90 & 0.99 - j9.825 \end{bmatrix}$$

Dr. Henry Louie

### Observations

- $Y_{bus}$  is symmetric
- Off-diagonal terms
  - Symmetric
  - Negative real, positive imaginary
  - $|\text{real}| < |\text{imaginary}|$
- Diagonal
  - Positive real, negative imaginary
  - $|\text{real}| < |\text{imaginary}|$

$$Y_{Bus} = \begin{bmatrix} 0.99 - j9.825 & -0.99 + j9.90 \\ -0.99 + j9.90 & 0.99 - j9.825 \end{bmatrix}$$

Dr. Henry Louie

### Transformer

- Typical transformer model:
  - Ignores resistance
  - Ignores shunt impedance
  - Nominal turns ratio

$$Y_{bus} = \begin{bmatrix} \frac{1}{jX} & -\frac{1}{jX} \\ -\frac{1}{jX} & \frac{1}{jX} \end{bmatrix} = \begin{bmatrix} y & -y \\ -y & y \end{bmatrix}$$

Dr. Henry Louie

### Off-Nominal Transformer

- For off-nominal transformers
  - $\frac{V_1}{a} I_1 = -V_2 I_2$  (complex power into ideal transformer is preserved)
  - $I_1 = -a I_2$
  - $I_2 = -\frac{I_1}{a}$

circuit analysis:

$$I_1 = \left( V_1 - \frac{V_2}{a} \right) y = V_1 y - \frac{V_2 y}{a}$$

$$I_2 = -\frac{V_1 y}{a} + \frac{V_2 y}{a^2} \text{ using } I_2 = -\frac{I_1}{a}$$

Dr. Henry Louie

### Off-Nominal Transformer

$$I_1 = V_1 y - \frac{V_2 y}{a}$$

$$I_2 = -\frac{V_1 y}{a} + \frac{V_2 y}{a^2}$$

- In matrix form:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y & -\frac{y}{a} \\ -\frac{y}{a} & \frac{y}{a^2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Dr. Henry Louie

### Off-Nominal Transformer

- Off-nominal transformer

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y & -\frac{y}{a} \\ -\frac{y}{a} & \frac{y}{a^2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- $\Pi$ -circuit:

$$\begin{bmatrix} I_m \\ I_n \end{bmatrix} = \begin{bmatrix} y_a + \frac{y_{shunt}}{2} & -y_a \\ -y_a & y_a + \frac{y_{shunt}}{2} \end{bmatrix} \begin{bmatrix} V_m \\ V_n \end{bmatrix}$$

Dr. Henry Louie

### Off-Nominal Transformer

- Off-nominal transformer

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y & \frac{y}{a} \\ -\frac{y}{a} & \frac{y}{a^2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- II-circuit:

$$\begin{bmatrix} I_m \\ I_n \end{bmatrix} = \begin{bmatrix} y_a + \frac{y_{shunt}}{2} & -y_a \\ -y_a & y_a + \frac{y_{shunt}}{2} \end{bmatrix} \begin{bmatrix} V_m \\ V_n \end{bmatrix}$$

Dr. Henry Louie

### Off-Nominal Transformer

- What should the shunt elements be?

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y & -\frac{y}{a} \\ -\frac{y}{a} & \frac{y}{a^2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- Diagonal elements: sum of admittances connected to them

$$\frac{y}{a} + F = y$$

$$F = y - \frac{y}{a} = y \left( \frac{a-1}{a} \right)$$

Dr. Henry Louie

### Off-Nominal Transformer

- Off-nominal transformer

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y & \frac{y}{a} \\ -\frac{y}{a} & \frac{y}{a^2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- II-circuit:

$$\begin{bmatrix} I_m \\ I_n \end{bmatrix} = \begin{bmatrix} y_a + \frac{y_{shunt}}{2} & -y_a \\ -y_a & y_a + \frac{y_{shunt}}{2} \end{bmatrix} \begin{bmatrix} V_m \\ V_n \end{bmatrix}$$

Dr. Henry Louie

### Off-Nominal Transformer

II has lost its symmetry!

- Off-nominal transformer

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y & -\frac{y}{a} \\ -\frac{y}{a} & \frac{y}{a^2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- II-circuit:

$$\begin{bmatrix} I_m \\ I_n \end{bmatrix} = \begin{bmatrix} y_a + \frac{y_{shunt}}{2} & -y_a \\ -y_a & y_a + \frac{y_{shunt}}{2} \end{bmatrix} \begin{bmatrix} V_m \\ V_n \end{bmatrix}$$

Dr. Henry Louie

### Y<sub>bus</sub> Construction

- Now that we have covered the basic elements we should focus on constructing **Y<sub>bus</sub>** for a network
- It is common to have transmission lines described by their primitive impedance (**z**), in p.u. and their shunt admittance, (**B**)
  - note: this means we must divide **B** by two to obtain the admittance on either leg of the II model

Dr. Henry Louie

### Ybus Construction

General Procedure:

- Determine the size of **Y<sub>bus</sub>**
- Convert all primitive impedances to primitive admittances
- Pick a bus to start, say bus j:
  - Y<sub>jj</sub> is the sum of the primitive admittances connecting bus j to all other buses and to ground
  - Y<sub>ij</sub> is the negative of the primitive admittance connecting bus j to bus i (zero if they are not connected)
- Continue until all buses have been computed

Dr. Henry Louie

### Example

- All impedances are in p.u.
- $T_1: z = 0.004 + j0.0533$
- $T_2: z = 0.006 + j0.08$
- Transmission line shunts:
  - line 2-4:  $B_{24} = 0.11$
  - line 2-3:  $B_{23} = 0.22$
  - line 3-4:  $B_{34} = 0.22$

It is assumed that B represents a capacitance

Dr. Henry Louie

### Example

- Calculate primitive admittances:
  - $y_{12} = 1/(.004 + j0.0533) = 1.4 - j18.657$
  - $y_{23} = 1/(0.02 + j0.25) = 0.318 - j3.975$
  - $y_{34} = 0.318 - j3.975$
  - $y_{24} = 0.442 - j6.637$
  - $y_{45} = 0.932 - j12.43$

$T_1: z = 0.004 + j0.0533$   
 $T_2: z = 0.006 + j0.08$   
 transmission line shunts:  
 line 2-4:  $B_{24} = 0.11$   
 line 2-3:  $B_{23} = 0.22$   
 line 3-4:  $B_{34} = 0.22$

Dr. Henry Louie

### Example

$$Y_{bus} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} & Y_{14} & Y_{15} \\ Y_{21} & Y_{22} & Y_{23} & Y_{24} & Y_{25} \\ Y_{31} & Y_{32} & Y_{33} & Y_{34} & Y_{35} \\ Y_{41} & Y_{42} & Y_{43} & Y_{44} & Y_{45} \\ Y_{51} & Y_{52} & Y_{53} & Y_{54} & Y_{55} \end{bmatrix}$$

transmission line shunts:  
line 2-4:  $B_{24} = 0.11$   
line 2-3:  $B_{23} = 0.22$   
line 3-4:  $B_{34} = 0.22$

$Y_{11} = Y_{12} = 1.4 - j18.657$   
 $Y_{12} = Y_{21} = -Y_{12} = -1.4 + j18.657$   
 $Y_{13} = Y_{14} = Y_{15} = Y_{31} = Y_{41} = Y_{51} = 0$   
 $Y_{22} = Y_{12} + Y_{23} + Y_{24} + j\frac{B_{23}}{2} + j\frac{B_{24}}{2}$   
 $= 2.16 - j29.104$   
 $Y_{23} = Y_{32} = -Y_{23} = -0.318 + j3.975$   
 $Y_{12} = 1.4 - j18.657$   
 $Y_{23} = 0.318 - j3.975$   
 $Y_{34} = 0.318 - j3.975$   
 $Y_{24} = 0.442 - j6.637$   
 $Y_{45} = 0.932 - j12.43$

Dr. Henry Louie

### Example

$$\begin{bmatrix} (1.4 - j18.66) & (-1.4 + j18.66) & 0 & 0 & 0 \\ (-1.4 + j18.66) & (2.16 - j29.10) & (-0.318 + j3.98) & X & X \\ 0 & (-0.318 + j3.98) & X & X & X \\ 0 & X & X & X & X \\ 0 & X & X & X & X \end{bmatrix}$$

complete the matrix

Dr. Henry Louie

### Example

$$\begin{bmatrix} (1.4 - j18.66) & (-1.4 + j18.66) & 0 & 0 & 0 \\ (-1.4 + j18.66) & (2.16 - j29.10) & (-0.318 + j3.98) & (-0.442 + j6.64) & 0 \\ 0 & (-0.318 + j3.98) & (0.636 - j7.73) & (-3.18 + j3.98) & 0 \\ 0 & (-0.442 + j6.64) & (-3.18 + j3.98) & (1.692 - j22.88) & (-0.932 + j12.43) \\ 0 & 0 & 0 & (-0.932 + j12.43) & (0.932 - j12.43) \end{bmatrix}$$

admittance matrix

Dr. Henry Louie

### Ybus Properties



- $Y_{bus}$ :
  - symmetric
  - sparse
  - has an inverse if at least one branch connects to the reference

$$\begin{bmatrix} (1.4 - j18.66) & (-1.4 + j18.66) & 0 & 0 & 0 \\ (-1.4 + j18.66) & (2.16 - j29.10) & (-0.318 + j3.98) & (-0.442 + j6.64) & 0 \\ 0 & (-0.318 + j3.98) & (0.636 - j7.73) & (-3.18 + j3.98) & 0 \\ 0 & (-0.442 + j6.64) & (-3.18 + j3.98) & (1.692 - j22.88) & (-0.932 + j12.43) \\ 0 & 0 & 0 & (-0.932 + j12.43) & (0.932 - j12.43) \end{bmatrix}$$

Dr. Henry Louie

### Generator Modeling


- $\mathbf{Y}_{bus}$  models the network, what about generators?
- Simple generator model: voltage source (emf) behind an impedance  $\mathbf{E}_a = \mathbf{I}_a \mathbf{z}_s + \mathbf{V}_a$
- Sometimes it is more convenient to model as a current source:  $\mathbf{I}_s = \frac{\mathbf{E}_a}{\mathbf{z}_s} = \mathbf{I}_a + \mathbf{V}_a \mathbf{y}_s$  where  $\mathbf{y}_s = 1/\mathbf{z}_s$

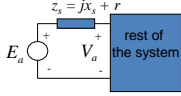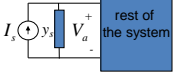Dr. Henry Louie
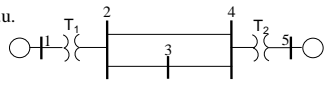
### Generator Modeling

- Voltage or current source formation can be used to form  $\mathbf{V}$  or  $\mathbf{I}$  in the equation:  $\mathbf{V} = \mathbf{Y}_{bus} \mathbf{I}$
- Gen. 1
  - emf:  $0.90 \angle 0^\circ$  p.u.
  - $\mathbf{z}_s = j1.25$  p.u.
- Gen. 5
  - emf:  $0.80 \angle -70^\circ$  p.u.
  - $\mathbf{z}_s = j1.25$  p.u.



Dr. Henry Louie

### Generator Modeling


- Use a current source model:
- Gen 1:  $\mathbf{I}_{s1} = \frac{0.90 \angle 0}{j1.25} = 0.72 \angle -90^\circ$
- Gen 2:  $\mathbf{I}_{s5} = \frac{0.80 \angle -70}{j1.25} = 0.64 \angle -160^\circ$
- We can now write the bus injection vector as

$$\mathbf{I} = \begin{bmatrix} 0.72 \angle -90^\circ \\ 0 \\ 0 \\ 0 \\ 0.64 \angle -160^\circ \end{bmatrix}$$

Dr. Henry Louie
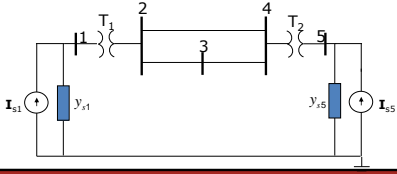
### Generator Modeling

Here is the same network data as before, but with the generators included as current sources in parallel with admittances



Dr. Henry Louie

### Using $\mathbf{Y}_{bus}$

- Corresponding matrix equation (ignoring resistance to simplify) is:

$$\begin{bmatrix} 0.72 \angle -90^\circ \\ 0 \\ 0 \\ 0 \\ 0.72 \angle -160^\circ \end{bmatrix} = \begin{bmatrix} -j19.56 & j18.76 & 0 & 0 & 0 \\ j18.76 & -j29.27 & j4.0 & j6.67 & 0 \\ 0 & j4.0 & -j7.78 & j4.0 & 0 \\ 0 & 0 & j6.67 & j4.0 & -j23.01 \\ 0 & 0 & 0 & j12.50 & -j13.30 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \\ \mathbf{V}_3 \\ \mathbf{V}_4 \\ \mathbf{V}_5 \end{bmatrix}$$

- See example 9.7 for details

Dr. Henry Louie

### Network Solution


- We have  $\mathbf{Y}_{bus}$  now what?
- Most often we know the current from the generators and into the loads, but not the bus voltages
- Find bus voltages through matrix operations

$$\mathbf{I} = \mathbf{Y}_{bus} \mathbf{V} \quad (\mathbf{Y}_{bus})^{-1} \mathbf{I} = \mathbf{V}$$

- What is  $(\mathbf{Y}_{bus})^{-1}$ ?

$$(\mathbf{Y}_{bus})^{-1} = \text{inv}(\mathbf{Y}_{bus}) = \mathbf{Z}_{bus}$$


Dr. Henry Louie



### Network Solution

- $\mathbf{Z}_{\text{bus}}$ : bus impedance matrix
- $\mathbf{V} = \mathbf{Z}_{\text{bus}} \mathbf{I}$
- note: generally
 
$$\begin{bmatrix} \frac{1}{\mathbf{Y}_{11}} & \frac{1}{\mathbf{Y}_{12}} \\ \frac{1}{\mathbf{Y}_{21}} & \frac{1}{\mathbf{Y}_{22}} \end{bmatrix} \neq \begin{bmatrix} \mathbf{Z}_{11} & \mathbf{Z}_{12} \\ \mathbf{Z}_{21} & \mathbf{Z}_{22} \end{bmatrix}$$
- $\mathbf{Z}_{\text{bus}}$  is:
  - not sparse
  - useful in fault studies and contingency analysis
  - we will discuss in future lectures


Dr. Henry Louie



### Network Solution

- We tend to use  $\mathbf{Y}_{\text{bus}}$  over  $\mathbf{Z}_{\text{bus}}$  because  $\mathbf{Y}_{\text{bus}}$  can be determined by inspection
- Computing  $\mathbf{Z}_{\text{bus}}$  is computationally burdensome
- We don't need to explicitly find  $\mathbf{Z}_{\text{bus}}$  to solve our equation
- We can use **LU** factorization (see text section 9.2 for details)
- We will rely on Matlab for matrix computations

Dr. Henry Louie




### Matlab Example

- from Matlab, we found

$$\mathbf{Z}_{\text{bus}} = \begin{bmatrix} j1.021 & j1.012 & j1.013 & j0.959 & j0.901 \\ j1.012 & j1.055 & j1.056 & j0.999 & j0.939 \\ j1.013 & j1.056 & j1.215 & j1.057 & j0.994 \\ j0.959 & j0.999 & j1.057 & j1.057 & j0.993 \\ j0.901 & j0.939 & j0.994 & j0.993 & j1.009 \end{bmatrix}$$

$$\mathbf{V} = \begin{bmatrix} 1.08 \angle -30.16^\circ \\ 1.092 \angle -31.17^\circ \\ 1.12 \angle -32.27^\circ \\ 1.087 \angle -33.33^\circ \\ 1.06 \angle -34.89^\circ \end{bmatrix}$$


Dr. Henry Louie



### Network Reduction

- Now that we have both the current injected as well as the voltage at each bus, we can compute the power
- We will save that for later
- For large power systems, the size of the  $\mathbf{Y}_{\text{bus}}$  can be a burden on memory (this isn't as true as it used to be)
- Can we reduce its size?


Dr. Henry Louie



### Network Reduction

- Observation: current injection is always zero when there are no external loads or generators connected
- We can eliminate the nodes and reduce the matrix size
- The procedure is also known as Kron Reduction

Dr. Henry Louie



### Network Reduction

- Assume we are given:
 
$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ 0 \end{bmatrix} = \begin{bmatrix} \mathbf{Y}_{11} & \mathbf{Y}_{12} & \mathbf{Y}_{13} \\ \mathbf{Y}_{21} & \mathbf{Y}_{22} & \mathbf{Y}_{23} \\ \mathbf{Y}_{31} & \mathbf{Y}_{32} & \mathbf{Y}_{33} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \\ \mathbf{V}_3 \end{bmatrix}$$
- 1. we can eliminate the third node by expressing  $\mathbf{V}_3$  in terms of  $\mathbf{V}_1$  and  $\mathbf{V}_2$
- 2. the dependence of  $\mathbf{I}_1$  and  $\mathbf{I}_2$  on  $\mathbf{V}_1$ ,  $\mathbf{V}_2$  and  $\mathbf{V}_3$  may be expressed in terms of  $\mathbf{V}_1$  and  $\mathbf{V}_2$  only
- 3. collect terms into a new  $2 \times 2$  matrix

Dr. Henry Louie



### Network Reduction

1. We can eliminate the third node by expressing  $\mathbf{V}_3$  in terms of  $\mathbf{V}_1$  and  $\mathbf{V}_2$

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ 0 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \\ \mathbf{V}_3 \end{bmatrix}$$

$$0 = Y_{31}\mathbf{V}_1 + Y_{32}\mathbf{V}_2 + Y_{33}\mathbf{V}_3$$

$$\mathbf{V}_3 = -\frac{Y_{31}}{Y_{33}}\mathbf{V}_1 - \frac{Y_{32}}{Y_{33}}\mathbf{V}_2$$

Dr. Henry Louie



### Network Reduction

2. the dependence of  $\mathbf{I}_1$  and  $\mathbf{I}_2$  on  $\mathbf{V}_1$ ,  $\mathbf{V}_2$  and  $\mathbf{V}_3$  may be expressed in terms of  $\mathbf{V}_1$  and  $\mathbf{V}_2$  only

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ 0 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \\ \mathbf{V}_3 \end{bmatrix}$$

$$\mathbf{I}_1 = Y_{11}\mathbf{V}_1 + Y_{12}\mathbf{V}_2 + Y_{13} \left( -\frac{Y_{31}}{Y_{33}}\mathbf{V}_1 - \frac{Y_{32}}{Y_{33}}\mathbf{V}_2 \right)$$

$$\mathbf{I}_2 = Y_{21}\mathbf{V}_1 + Y_{22}\mathbf{V}_2 + Y_{23} \left( -\frac{Y_{31}}{Y_{33}}\mathbf{V}_1 - \frac{Y_{32}}{Y_{33}}\mathbf{V}_2 \right)$$

$$\mathbf{V}_3 = -\frac{Y_{31}}{Y_{33}}\mathbf{V}_1 - \frac{Y_{32}}{Y_{33}}\mathbf{V}_2$$

using

Dr. Henry Louie



### Network Reduction

3. collect terms into a new 2 x 2 matrix

$$\mathbf{I}_1 = Y_{11}\mathbf{V}_1 + Y_{12}\mathbf{V}_2 + Y_{13} \left( -\frac{Y_{31}}{Y_{33}}\mathbf{V}_1 - \frac{Y_{32}}{Y_{33}}\mathbf{V}_2 \right)$$

$$\mathbf{I}_2 = Y_{21}\mathbf{V}_1 + Y_{22}\mathbf{V}_2 + Y_{23} \left( -\frac{Y_{31}}{Y_{33}}\mathbf{V}_1 - \frac{Y_{32}}{Y_{33}}\mathbf{V}_2 \right)$$

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} Y_{11} - \frac{Y_{13}Y_{31}}{Y_{33}} & Y_{12} - \frac{Y_{13}Y_{32}}{Y_{33}} \\ Y_{21} - \frac{Y_{23}Y_{31}}{Y_{33}} & Y_{22} - \frac{Y_{23}Y_{32}}{Y_{33}} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

Dr. Henry Louie