

# 17-Three Phase Transformers Part 2

ECEGR 450  
Electromechanical Energy Conversion



## Overview


- Delta-Y Transformer Connection
- Delta-Y Transformer Analysis
- Transformer Phase Shifts
- Y-Delta Transformer Connection
- Y-Delta Transformer Analysis
- Practical Considerations

Dr. Louise


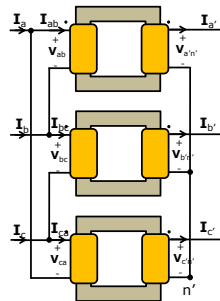
## Δ-Y Transformer

- Secondary has a neutral connection
- Primary connected "top-to-bottom"
- Line-line voltages appear on the coils on primary
- Phase voltages appear on the coils on the secondary
- Less insulation needed on HV winding




Dr. Louise


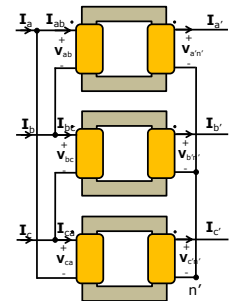
## Δ-Y Transformer Analysis

- By Faraday's Law:
  - $V_{ab}$  will be in-phase with  $V_{a'n'}$
  - Phase shift introduced
- By KCL:
  - $I_a = I_{ab} - I_{ca}$
- By Ampere's Law:
  - $I_{ab}$  will be in-phase with  $I_{a'}$
  - Phase shift introduced
- Similar results for b, c phases




Dr. Louise


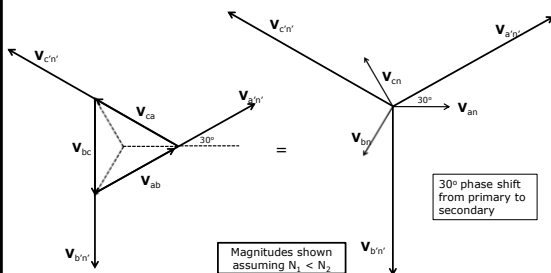
## Δ-Y Transformer Analysis

Phasor Diagram for Ideal Delta-Y Connected Transformer




Dr. Louise


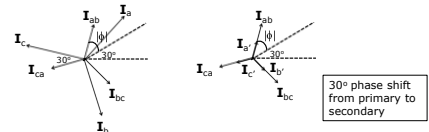
## Delta-Y Transformer Analysis

Phasor Diagram for Ideal Delta-Y Connected Transformer

$$\begin{aligned} I_a &= I_{ab} - I_{ca} \\ I_b &= I_{bc} - I_{ab} \\ I_c &= I_{ca} - I_{bc} \end{aligned}$$



Dr. Louise

### Three-Phase Transformer Analysis: Delta-Y

- Let  $k$  be the transformer voltage gain
- For  $\Delta$ -Y transformers:
 
$$\mathbf{V}_{a'n'} = n\mathbf{V}_{ab} = n\mathbf{V}_{an}\sqrt{3}e^{j\frac{\pi}{6}} = k\mathbf{V}_{an}$$
 therefore  $k = n\sqrt{3}e^{j\frac{\pi}{6}}$  Important result!
- $$\mathbf{I}_{a'} = \frac{\mathbf{I}_{ab}}{n} = \frac{\mathbf{I}_a e^{j\frac{\pi}{6}}}{\sqrt{3}n}$$

$$= \frac{\mathbf{I}_a}{k'} \quad \left. \vphantom{\frac{\mathbf{I}_a}{k'}} \right\} \text{ same phase shift as voltage}$$

7

### Delta-Y Transformer Analysis

- Voltage relationships
 
$$\begin{aligned} \mathbf{V}_{a'n'} &= k\mathbf{V}_{an'} & \mathbf{V}_{a'b'} &= k\mathbf{V}_{ab} \\ \mathbf{V}_{b'n'} &= k\mathbf{V}_{bn'} & \mathbf{V}_{b'c'} &= k\mathbf{V}_{bc} \\ \mathbf{V}_{c'n'} &= k\mathbf{V}_{cn'} & \mathbf{V}_{c'a'} &= k\mathbf{V}_{ca} \end{aligned}$$
- Current relationships
 
$$\begin{aligned} \mathbf{I}_{a'} &= \frac{\mathbf{I}_a}{k'} \\ \mathbf{I}_{b'} &= \frac{\mathbf{I}_b}{k'} \\ \mathbf{I}_{c'} &= \frac{\mathbf{I}_c}{k'} \end{aligned}$$

8

### Question

- Consider an ideal Delta-Y transformer, with 20 turns on each primary coil, and 80 turns on each secondary coil. If the primary side values are:
 
$$\begin{aligned} \mathbf{V}_{ab} &= 208\angle 0^\circ \text{ V} \\ \mathbf{I}_a &= 10\angle 5^\circ \text{ A} \end{aligned}$$
- Compute:  $\mathbf{V}_{a'b'}$ ,  $\mathbf{V}_{a'n'}$  and  $\mathbf{I}_{a'}$

9

### Question

- Consider an ideal Delta-Y transformer, with 20 turns on each primary coil, and 80 turns on each secondary coil. If the primary side values are:
 
$$\begin{aligned} \mathbf{V}_{ab} &= 208\angle 0^\circ \text{ V} \\ \mathbf{I}_a &= 10\angle 5^\circ \text{ A} \end{aligned}$$
- Compute:  $\mathbf{V}_{a'b'}$ ,  $\mathbf{V}_{a'n'}$  and  $\mathbf{I}_{a'}$ 

$$k = n\sqrt{3}e^{j\frac{\pi}{6}} = 4\sqrt{3}e^{j\frac{\pi}{6}} = 6.92\angle 30^\circ$$

$$\mathbf{V}_{a'b'} = \mathbf{V}_{ab}k = 1436\angle 30^\circ \text{ V}$$

$$\mathbf{V}_{a'n'} = \mathbf{V}_{ab}k = (120\angle -30^\circ)(6.92\angle 30^\circ) = 830.4\angle 0^\circ \text{ V}$$

$$\mathbf{I}_{a'} = \frac{\mathbf{I}_a}{k'} = \frac{10\angle 5^\circ}{6.92\angle -30^\circ} = 1.45\angle 35^\circ \text{ A}$$

10

### Y-Δ Transformer

- No neutral point on secondary
- $\mathbf{V}_{an'}$ ,  $\mathbf{V}_{a'b'}$  in phase
- $\mathbf{I}_{an'}$ ,  $\mathbf{I}_{b'a'}$  in phase
  - Similar results for b, c phase
- Phase voltage across primary coils
- Line voltage across secondary coils

11

### Three-Phase Transformer Analysis: Y-Δ

- Let  $k$  be the transformer voltage gain
- For Y-Δ transformers:
 
$$\mathbf{V}_{a'b'} = n\mathbf{V}_{an} = \frac{n\mathbf{V}_{ab}e^{-j\frac{\pi}{6}}}{\sqrt{3}} = k\mathbf{V}_{ab}$$
 therefore  $k = \frac{ne^{-j\frac{\pi}{6}}}{\sqrt{3}}$  Important result

Note: phase shift is  $-30^\circ$ , whereas for Delta-Y transformer connection in previous slides it is  $+30^\circ$

12

**Question**

Is there any concern in connecting a three phase Y-Delta transformer in parallel with a three phase Delta-Y transformer? Assume the transformers are appropriately rated.

Dr. Louie 13

**Y-Delta Transformer**

- To achieve at +30° phase shift connect as shown
- Note the phasing on the secondary
- $V_{an}, V_{a'c'}$  in phase
- $I_{an}, I_{c'a'}$  in phase

Dr. Louie 14

**Y-Delta Transformer**

- A side note:  $-V_{bn} = \frac{1}{\sqrt{3}} V_{ab} e^{j\frac{\pi}{6}}$

Dr. Louie 15

**Three-Phase Transformer Analysis: Y-Δ**

- Voltage relationship

$$V_{a'b'} = -nV_{bn} = \frac{n}{\sqrt{3}} V_{ab} e^{j\frac{\pi}{6}} = kV_{ab}$$

therefore  $k = \frac{n}{\sqrt{3}} e^{j\frac{\pi}{6}}$

$$V_{a'n'} = \frac{V_{a'b'}}{\sqrt{3}} e^{-j\frac{\pi}{6}} = \frac{nV_{an}}{\sqrt{3}} e^{j\frac{\pi}{6}} = kV_{an}$$

- For the other phases

$$V_{b'n'} = kV_{bn}$$

$$V_{c'n'} = kV_{cn}$$

Phase shift is now +30°

Dr. Louie 16

**Three-Phase Transformer Analysis**

- It can be shown:

$$\left. \begin{aligned} I_a &= \frac{I_a}{k'} \\ I_b &= \frac{I_b}{k'} \\ I_c &= \frac{I_c}{k'} \end{aligned} \right\} \text{same phase-shift as voltages}$$

Dr. Louie 17

**Three-Phase Transformer Analysis**

- What about power?

$$S = V_{a'n'} I_a = kV_{an} \left( \frac{I_a}{k'} \right) = V_{an} I_a \text{ for all configurations}$$

- For ideal three-phase xfmrs, power is conserved, as in the single phase case

Dr. Louie 18

### Three-Phase Transformer Analysis

- What about impedances?
- For all transformer connections:
 
$$\text{secondary impedance referred to the primary} = \frac{1}{|k|^2} Z_L$$

Dr. Louie 19

### Transformer Phase Shifts

- Various winding connections of  $\Delta$ -Y, and Y- $\Delta$  xfmr lead to different phase shifts
- Standard is to have **phase-neutral voltages advance** by 30 degrees when going from low voltage to high voltage
- Previous slides have followed this convention
- Note: convention is most critical in interconnected power systems. Some homework problems do not follow this convention

Dr. Louie 20

### Transformer Phase Shifts

- Which Y- $\Delta$  is correct?
- Check  $V_{a'n'}$  for each

Dr. Louie 21

### Transformer Phase Shifts

- Which Y- $\Delta$  is correct?
- Check  $V_{a'n'}$  for each case:
  - top  $V_{a'n'} = n \frac{V_{an}}{\sqrt{3}} \angle 30^\circ$
  - bottom  $V_{a'n'} = n \frac{V_{an}}{\sqrt{3}} \angle -30^\circ$

Dr. Louie 22

### Transformer Phase Shifts


Dr. Louie 23

### Transformer Phase Shifts

Dr. Louie 24

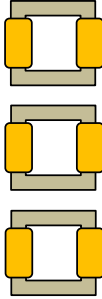**Example**


Draw the connections, polarity markers and label the primary and secondary phases for a Delta-Wye step down transformer (assume left side is the high side)



Dr. Louie 25

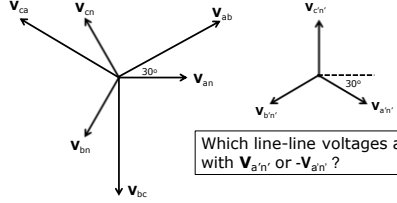**Example**

- Need secondary (right) side to be regressed in phase by 30 degrees (per convention)




Which line-line voltages are in phase with  $V_{a'n'}$  or  $-V_{a'n'}$ ?

Dr. Louie 26

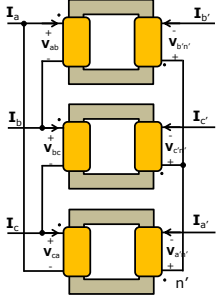**Example**


- $-V_{ca}$  must be connected to  $V_{a'n'}$  winding
- $-V_{ab}$  must be connected to  $V_{b'n'}$  winding
- $-V_{bc}$  must be connected to  $V_{c'n'}$  winding



Dr. Louie 27

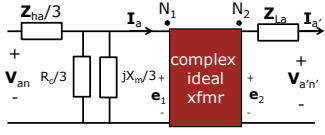**Per-Phase Analysis ( $\Delta$ -Y)**


- Per-phase equivalent of a non-ideal  $\Delta$ -Y transformer
- Complex ideal transformer with gain  $k$  or  $k^*$   
 $k = \sqrt{3}ne^{j\frac{\pi}{6}}$ 
  - +30° shift when primary is lower voltage and secondary is higher voltage



Dr. Louie 28

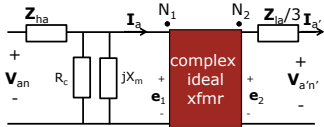**Per-Phase Analysis (Y- $\Delta$ )**

- Per-phase equivalent of a Y- $\Delta$  transformer
- Complex ideal transformer with gain  $k$  or  $k^*$   
 $k = \frac{ne^{j\frac{\pi}{6}}}{\sqrt{3}}$ 
  - +30° shift when primary is lower voltage and secondary is higher voltage



Dr. Louie 29

**Example**

- Consider three, single-phase transformers. The transformers have the following specifications:
  - 720VA, 360/120V,  $R_H = 18.9\Omega$ ,  $X_H = 21.6\Omega$ ,  $R_L = 2.1\Omega$ ,  $X_L = 2.4\Omega$ ,  $R_{ch} = 8.64k\Omega$ ,  $X_{mH} = 6.84k\Omega$
- Draw the per-phase equivalent circuit if the transformers are connected as Delta-Y
- What are the nominal line voltages on each side of the transformer?

Dr. Louie 30

### Example

- Nominal per-phase voltage on primary is 360V and 208V on secondary
  - Nominal primary line voltage: 360V
  - Nominal secondary line voltage: 208V

$k = 1.732 \angle -30^\circ$

31

### Example

- Consider three, single-phase transformers. The transformers have the following specifications:
  - 720VA, 360/120V,  $R_H = 18.9\Omega$ ,  $X_H = 21.6\Omega$ ,  $R_L = 2.1\Omega$ ,  $X_L = 2.4\Omega$ ,  $R_{CH} = 8.64k\Omega$ ,  $X_{MH} = 6.84k\Omega$
- Draw the per-phase equivalent circuit if the transformers are connected as Y-Delta
- What are the nominal line voltages on each side of the transformer?

32

### Example

- Nominal per-phase voltage on primary is 360V and 69V on secondary
  - Nominal primary line voltage: 624V
  - Nominal secondary line voltage: 120V

$k = 5.196 \angle -30^\circ$

33

### Practical Considerations

- Medium-voltage industrial facilities often use  $\Delta$ -Y incoming transformers
- Y-side is grounded through a resistor
  - Reduces ground current during fault
  - Reduces voltage dip during fault

primary      secondary

34

### Practical Considerations

Cause	Percent of Failures
Insulation failures	26%
Manufacturing problems	24%
Unknown	16%
Loose connections	7%
Through faults	5%
Improper maintenance	5%
Oil contamination	4%
Overloading	4%
Fire/Explosions	3%
Lighting	3%
Floods	2%
Moisture	1%

Source: Mozina, C.J., "Protection and Commissioning of Digital Transformer Relays: Improvements in Medium-Voltage Industrial Transformer Protection," *Industry Applications Magazine, IEEE*, vol.18, no.6, pp.63-73, Nov-Dec. 2012

35

### Practical Considerations

Source: Wang, M., Vandermaar, A.J., Srivastava, K.D., "Review of condition assessment of power transformers in service," *Electrical Insulation Magazine, IEEE*, vol.18, no.6, pp.12-25, Nov-Dec. 2002

36



## Practical Considerations

- Condition assessment of transformers: Wang, M.; Vandermaar, A.J.; Srivastava, K.D.; , "Review of condition assessment of power transformers in service," *Electrical Insulation Magazine, IEEE* , vol.18, no.6, pp.12-25, Nov.-Dec. 2002 [available online in IEEE Xplore through SU library]

Dr. Louie

37



## Summary

- There is a complex gain associated with Y-Delta and Delta-Y transformers
- Connection of transformer coils allows for different phase shifts to be achieved
- Convention: phase-neutral voltages advance by 30 degrees from lower voltage to higher voltage side
- Power in ideal three phase transformers is conserved
- Impedances are transferred from secondary to primary by:  $\frac{1}{|k|^2} Z_L$

Dr. Louie

38