

Power Flow Part 1

Text: 10-10.2

ECEGR 451
Power Systems

Dr. Louie 1


Topics

- Power Transmission Revisited
- Power Flow Equations
- Power Flow Problem Statement

Dr. Louie 2

Power Transmission

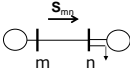Recall that for a short transmission line, the power from bus m to bus n, S_{mn} can be written as:



$$S_{mn} = \mathbf{V}_m \mathbf{I}_m^* = \mathbf{V}_m \left(\frac{\mathbf{V}_m - \mathbf{V}_n}{\mathbf{Z}_{mn}} \right)^* = \frac{|\mathbf{V}_m|^2}{\mathbf{Z}_{mn}} - \frac{\mathbf{V}_m \mathbf{V}_n^*}{\mathbf{Z}_{mn}}$$


$$S_{mn} = \frac{|\mathbf{V}_m|^2}{r_{mn} - jx_{mn}} - \frac{|\mathbf{V}_m| e^{j\theta_m} |\mathbf{V}_n| e^{-j\theta_n}}{r_{mn} - jx_{mn}}$$

$$= \frac{|\mathbf{V}_m|^2}{r_{mn} - jx_{mn}} - \frac{|\mathbf{V}_m|^2}{r_{mn} - jx_{mn}} - \frac{|\mathbf{V}_m| |\mathbf{V}_n| (\cos \theta_{mn} + j \sin \theta_{mn})}{r_{mn} - jx_{mn}}$$

Dr. Louie 3

Power Transmission

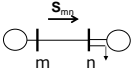Substituting and separating real and imaginary parts



$$\frac{1}{r_{mn} + jx_{mn}} \triangleq g_{mn} + jb_{mn}$$

$$S_{mn} = \frac{|\mathbf{V}_m|^2}{r_{mn} - jx_{mn}} - \frac{|\mathbf{V}_m| |\mathbf{V}_n| (\cos \theta_{mn} + j \sin \theta_{mn})}{r_{mn} - jx_{mn}}$$

$$= |\mathbf{V}_m|^2 (g_{mn} - jb_{mn}) - |\mathbf{V}_m| |\mathbf{V}_n| (\cos \theta_{mn} + j \sin \theta_{mn}) (g_{mn} - jb_{mn})$$


$$P_{mn} = g_{mn} |\mathbf{V}_m|^2 - g_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \cos \theta_{mn} - b_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \sin \theta_{mn}$$

$$Q_{mn} = -b_{mn} |\mathbf{V}_m|^2 - g_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \sin \theta_{mn} + b_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \cos \theta_{mn}$$

Dr. Louie 4

Power Transmission

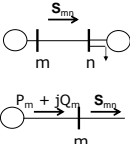Real, Imaginary Power from m to n must equal the power output by the generator




$$P_{mn} = g_{mn} |\mathbf{V}_m|^2 - g_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \cos \theta_{mn} - b_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \sin \theta_{mn} = P_m$$

$$Q_{mn} = -b_{mn} |\mathbf{V}_m|^2 - g_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \sin \theta_{mn} + b_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \cos \theta_{mn} = Q_m$$

Dr. Louie 5

Power Transmission

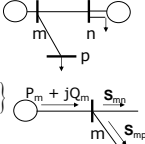- What if another bus is added?
- Equations become:




$$P_m = \left\{ g_{mn} |\mathbf{V}_m|^2 - g_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \cos \theta_{mn} - b_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \sin \theta_{mn} \right\} + \left\{ g_{mp} |\mathbf{V}_m|^2 - g_{mp} |\mathbf{V}_m| |\mathbf{V}_p| \cos \theta_{mp} - b_{mp} |\mathbf{V}_m| |\mathbf{V}_p| \sin \theta_{mp} \right\}$$

$$Q_m = \left\{ -b_{mn} |\mathbf{V}_m|^2 - g_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \sin \theta_{mn} + b_{mn} |\mathbf{V}_m| |\mathbf{V}_n| \cos \theta_{mn} \right\} + \left\{ -b_{mp} |\mathbf{V}_m|^2 - g_{mp} |\mathbf{V}_m| |\mathbf{V}_p| \sin \theta_{mp} + b_{mp} |\mathbf{V}_m| |\mathbf{V}_p| \cos \theta_{mp} \right\}$$

Dr. Louie 6

Power Transmission

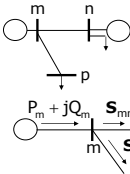- What if the transmission line from m to p is medium or long length?
- Let the total line shunt admittance be Y_{shunt}
- Note that since it is capacitance only, the real power is not affected




$$P_m = \{g_{mn}|V_m|^2 - g_{mn}|V_n||V_m|\cos\theta_{mn} - b_{mn}|V_n||V_m|\sin\theta_{mn}\} + \{g_{mp}|V_m|^2 - g_{mp}|V_p||V_m|\cos\theta_{mp} - b_{mp}|V_p||V_m|\sin\theta_{mp}\}$$

$$Q_m = -|V_m|^2 \frac{Y_{shunt}}{2} + \{-b_{mn}|V_m|^2 - g_{mn}|V_n||V_m|\sin\theta_{mn} + b_{mn}|V_n||V_m|\cos\theta_{mn}\} + \{-b_{mp}|V_m|^2 - g_{mp}|V_p||V_m|\sin\theta_{mp} + b_{mp}|V_p||V_m|\cos\theta_{mp}\}$$

Dr. Louie 7

Power Transmission

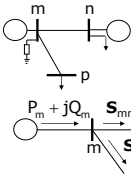- What if there was a shunt admittance added to bus m?
- Note this is difference from a load, since the load is modeled in terms of power
- Let the admittance be $y = g_m + jb_m$



$$P_m = \{|V_m|^2 g_m + g_{mn}|V_m|^2 - g_{mn}|V_n||V_m|\cos\theta_{mn} - b_{mn}|V_n||V_m|\sin\theta_{mn}\} + \{g_{mp}|V_m|^2 - g_{mp}|V_p||V_m|\cos\theta_{mp} - b_{mp}|V_p||V_m|\sin\theta_{mp}\}$$

$$Q_m = -|V_m|^2 b_m - |V_m|^2 \left(\frac{Y_{shunt}}{2}\right) + \{-b_{mn}|V_m|^2 - g_{mn}|V_n||V_m|\sin\theta_{mn} + b_{mn}|V_n||V_m|\cos\theta_{mn}\} + \{-b_{mp}|V_m|^2 - g_{mp}|V_p||V_m|\sin\theta_{mp} + b_{mp}|V_p||V_m|\cos\theta_{mp}\}$$

Dr. Louie 8

Power Transmission


- We can write similar expressions for the power out of buses n and p
- You can see that as we add more buses and transmission lines, the equations become quite long
- Let's see if we can simplify
 - use Y_{bus}
 - Y_{bus} works with current so we will start out by considering bus current

Dr. Louie 9

Power Flow Equations

- Total current entering the transmission system at bus i is equal to the current from the generator(s) at bus i minus the current to load at bus i
- I_i is the total current leaving bus i through transmission lines or shunts (not loads)
- Using Y_{bus} :
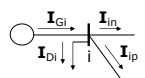
$$I_i \triangleq \sum_{k=1}^n Y_{ik} V_k \quad i = 1, 2, \dots, n$$



yields $I = Y_{bus} V$

Dr. Louie 10

Power Flow Equations

- Now for power
- $S_i = V_i I_i^*$
- Via substitution
- General case

$$S_i = V_i \left(\sum_{k=1}^n Y_{ik} V_k \right)^* \quad I_i \triangleq \sum_{k=1}^n Y_{ik} V_k$$

$$S_i = V_i \sum_{k=1}^n Y_{ik}^* V_k^* \quad i = 1, 2, \dots, n$$

Note: Y_{ik} refers to an element in Y_{Bus}

Dr. Louie 11

Power Flow Equations

- Recall $S_i = V_i \sum_{k=1}^n Y_{ik} V_k^*$
- via substitution and Euler's Identity


$$S_i = |V_i| e^{j\theta_i} \sum_{k=1}^n |V_k| e^{-j\theta_k} Y_{ik}^*$$

$$= \sum_{k=1}^n |V_i| |V_k| e^{j(\theta_i - \theta_k)} Y_{ik}^*$$

$$= \sum_{k=1}^n |V_i| |V_k| e^{j\theta_{ik}} (G_{ik} - jB_{ik})$$

$$= \sum_{k=1}^n |V_i| |V_k| (\cos\theta_{ik} + j\sin\theta_{ik}) (G_{ik} - jB_{ik})$$

Dr. Louie 12



Power Flow Equations

$$S_i = \sum_{k=1}^n |V_i||V_k|(\cos \theta_{ik} + j \sin \theta_{ik})(G_{ik} - jB_{ik})$$


- Split into real and reactive parts

$$P_i = \sum_{k=1}^n |V_i||V_k|(G_{ik} \cos \theta_{ik} + B_{ik} \sin \theta_{ik})$$

$$Q_i = \sum_{k=1}^n |V_i||V_k|(G_{ik} \sin \theta_{ik} - B_{ik} \cos \theta_{ik})$$

- Spend some time becoming familiar with these equations
- These equations match the equations derived for our simple 2 and 3 bus cases

Dr. Louie
13




Power Flow Equations

- To recap: for each bus i, we can find the **net power injected** (generation – minus load) by


$$P_i = \sum_{k=1}^n |V_i||V_k|(G_{ik} \cos \theta_{ik} + B_{ik} \sin \theta_{ik})$$
- $$Q_i = \sum_{k=1}^n |V_i||V_k|(G_{ik} \sin \theta_{ik} - B_{ik} \cos \theta_{ik})$$
- G_{ik} and B_{ik} values correspond to the element Y_{ik} in the Y_{bus} , and NOT the primitive admittance of line i-k
- If we have voltage magnitude and angle values at each bus, then we can easily determine all the power flows and power injections

Dr. Louie
14



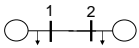
Example

- Voltage at bus 1 is 1.0 p.u. at zero degrees
- Voltage at bus 2 is 0.97 p.u. at -7 degrees
- Series line impedance is 0.01 + j0.1 p.u.
- $B_{12} = 0.10$ p.u.
- construct Y_{bus}




This is not Y_{bus} element 12, but is the total shunt capacitive reactance of line 1-2. If given in a problem statement, assume B_{mn} is defined as such.

Dr. Louie
15



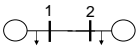
Example

- Voltage at bus 1 is 1.0 p.u. at zero degrees
- Voltage at bus 2 is 0.97 p.u. at -7 degrees
- Series line impedance is 0.01 + j0.1 p.u.
- $B_{12} = 0.10$ p.u.
- construct Y_{bus}




$$Y_{bus} = \begin{bmatrix} 0.99 - j9.85 & -0.99 + j9.90 \\ -0.99 + j9.90 & 0.99 - j9.85 \end{bmatrix}$$

Dr. Louie
16



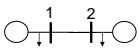
Example

- Voltage at bus 1 is 1.0 p.u. at zero degrees
- Voltage at bus 2 is 0.97 p.u. at -7 degrees
- What is the real power injected into bus 1?




$$Y_{bus} = \begin{bmatrix} 0.99 - j9.85 & -0.99 + j9.90 \\ -0.99 + j9.90 & 0.99 - j9.85 \end{bmatrix}$$

Dr. Louie
17



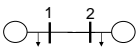Example

- Voltage at bus 1 is 1.0 p.u. at zero degrees
- Voltage at bus 2 is 0.97 p.u. at -7 degrees
- What is the real power injected into bus 1?




$$Y_{bus} = \begin{bmatrix} 0.99 - j9.85 & -0.99 + j9.90 \\ -0.99 + j9.90 & 0.99 - j9.85 \end{bmatrix}$$

$$P_1 = 1.0^2(0.99 \cos 0^\circ - 9.85 \sin 0^\circ) + 1.0 \times 0.97(-0.99 \cos 7^\circ + 9.90 \sin 7^\circ) = 1.2$$

Dr. Louie
18

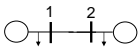Example

- Voltage at bus 1 is 1 p.u. at zero degrees
- Voltage at bus 2 is 0.97 p.u. at -7 degrees
- What is the reactive power injected into bus 1?




$$Y_{bus} = \begin{bmatrix} 0.99 - j9.85 & -0.99 + j9.90 \\ -0.99 + j9.90 & 0.99 - j9.85 \end{bmatrix}$$

Dr. Louie 19

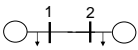Example

- Voltage at bus 1 is 1 p.u. at zero degrees
- Voltage at bus 2 is 0.97 p.u. at -7 degrees
- What is the reactive power injected into bus 1?



$$Y_{bus} = \begin{bmatrix} 0.99 - j9.85 & -0.99 + j9.90 \\ -0.99 + j9.90 & 0.99 - j9.85 \end{bmatrix}$$

$$Q_i = \sum_{k=1}^n |V_i||V_k|(G_k \sin \theta_k - B_k \cos \theta_k)$$


$$Q_1 = -1^2(-9.85) + 1(0.97)(-0.99 \sin(7) - 9.90 \cos(7))$$

$$Q_1 = 0.2 \text{ p.u.}$$

Dr. Louie 20

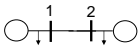Example

- In this example, the power injected to the bus is also the power transmitted down the power line
- To determine the power out of the generator, we must know the power into the load at bus 1
- If $P_{D1} = 1.0$ p.u. then the real power from the generator at bus 1 is 2.20 p.u.
- follow a similar procedure for reactive power



Dr. Louie 21

Power Flow Equations

- We can use the power flow equations to show the P- θ and Q- $|V|$ relationships
- The relationship can be quantified by find the sensitivity, or partial derivative of P w.r.t. θ and $|V|$
- From our example:

$$P_1 = P_{12} = |V_1|^2 G_{11} + |V_1||V_2|(G_{12} \cos(\theta_{12}) + B_{12} \sin(\theta_{12}))$$

$$\frac{\partial P_{12}}{\partial \theta_{12}} = 0 + |V_1||V_2|(-G_{12} \sin(\theta_{12}) + B_{12} \cos(\theta_{12}))$$

$$\frac{\partial P_{12}}{\partial |V_1|} = 2|V_1|G_{11} + |V_2|(G_{12} \cos(\theta_{12}) + B_{12} \sin(\theta_{12}))$$

Dr. Louie 22

Power Flow Equations

- Evaluating each derivative

$$\frac{\partial P_{12}}{\partial \theta_{12}} = 0 + 0.97(0.99 \sin(7) + 9.90 \cos(7))$$

$$= -9.6$$

$$\frac{\partial P_{12}}{\partial |V_1|} = 2(0.97)0.99 + 0.97(0.99 \cos(7) + 9.90 \sin(7))$$


$$= 4.04$$

- We expect a larger change of real power if the difference in voltage angles change, rather than a voltage magnitude change

Dr. Louie 23

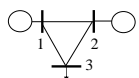Example

- Now try a three bus system
- Given:
 - $V_1 = 1 \angle 0^\circ$
 - $V_2 = 1.05 \angle -3^\circ$
 - $V_3 = 0.95 \angle -10^\circ$
- Find the power out of each generator and to the load



$$Y_{bus} = \begin{bmatrix} -j19.98 & j10 & j10 \\ j10 & -j19.98 & j10 \\ j10 & j10 & -j19.98 \end{bmatrix}$$

Dr. Louie 24

Example

- start at bus $i = 1$

$$P_i = \sum_{k=1}^n |V_i| |V_k| (G_{ik} \cos \theta_{ik} + B_{ik} \sin \theta_{ik}) \quad \mathbf{Y}_{bus} = \begin{bmatrix} -j19.98 & j10 & j10 \\ j10 & -j19.98 & j10 \\ j10 & j10 & -j19.98 \end{bmatrix}$$

- for $k = 1$

$$|V_1| |V_1| (G_{11} \cos \theta_{11} + B_{11} \sin \theta_{11}) = 0 \quad \mathbf{V}_1 = 1 \angle 0^\circ$$
- for $k = 2$

$$|V_1| |V_2| (G_{12} \cos \theta_{12} + B_{12} \sin \theta_{12}) = |1| |1.05| (0 + 10 \sin 3) = 0.549 \quad \mathbf{V}_2 = 1.05 \angle -3^\circ$$
- for $k = 3$

$$|V_1| |V_3| (G_{13} \cos \theta_{13} + B_{13} \sin \theta_{13}) = |1| |0.95| (0 + 10 \sin 10) = 1.65 \quad \mathbf{V}_3 = 0.95 \angle -10^\circ$$

- total real power: $0 + 0.549 + 1.65 = 2.19 \text{ p.u.}$

Dr. Louie 25

Example

- now bus $i = 2$

$$P_2 = \sum_{k=1}^n |V_2| |V_k| (G_{2k} \cos \theta_{2k} + B_{2k} \sin \theta_{2k})$$

- for $k = 1$

$$|V_2| |V_1| (G_{21} \cos \theta_{21} + B_{21} \sin \theta_{21}) = |1.05| |1| (10 \sin(-3)) = -0.549$$
- for $k = 2$

$$|V_2| |V_2| (G_{22} \cos \theta_{22} + B_{22} \sin \theta_{22}) = 0$$
- for $k = 3$

$$|V_2| |V_3| (G_{23} \cos \theta_{23} + B_{23} \sin \theta_{23}) = |1.05| |0.95| (10 \sin 7) = 1.215$$

- total real power: $-0.549 + 1.215 = 0.667 \text{ p.u.}$

Dr. Louie 26

Example

- now bus $i = 3$

$$P_3 = \sum_{k=1}^n |V_3| |V_k| (G_{3k} \cos \theta_{3k} + B_{3k} \sin \theta_{3k})$$

- for $k = 1$

$$|V_3| |V_1| (G_{31} \cos \theta_{31} + B_{31} \sin \theta_{31}) = |0.95| |1| (10 \sin(-10)) = -1.649$$
- for $k = 2$

$$|V_3| |V_2| (G_{32} \cos \theta_{32} + B_{32} \sin \theta_{32}) = |0.95| |1.05| (10 \sin(-7)) = -1.215$$
- for $k = 3$

$$|V_3| |V_3| (G_{33} \cos \theta_{33} + B_{33} \sin \theta_{33}) = 0$$

- total real power: $-1.649 - 1.215 = -2.865 \text{ p.u.}$

Dr. Louie 27

Example

- start at bus $i = 1$

$$Q_i = \sum_{k=1}^n |V_i| |V_k| (G_{ik} \sin \theta_{ik} - B_{ik} \cos \theta_{ik})$$

- for $k = 1$

$$|V_1|^2 (G_{11} \sin \theta_{11} - B_{11} \cos \theta_{11}) = -(1^2)(-19.98)$$
- for $k = 2$

$$|V_1| |V_2| (G_{12} \sin \theta_{12} - B_{12} \cos \theta_{12}) = 1(1.05)(-10 \cos 3) = -10.485$$
- for $k = 3$


$$|V_1| |V_3| (G_{13} \sin \theta_{13} - B_{13} \cos \theta_{13}) = 1(0.95)(-10 \cos 10) = -9.356$$

- total reactive power: $19.98 - 10.48 - 9.356 = 0.1365 \text{ p.u.}$

Dr. Louie 28

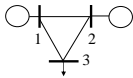Example

- Following the same procedure we can find reactive power for bus 2 and bus 3
- We can also find the power flow on each line
- If we have bus voltage angle and magnitude, we can completely describe the load and generation, as well as power flows
 - losses (real and reactive) can be computed



Dr. Louie 29

Example

- A very **common mistake** is to assume that the power flowing from bus i to k is found by substituting $i=1$ and $k=2$ into:

$$P_i = \sum_{k=1}^n |V_i| |V_k| (G_{ik} \cos \theta_{ik} + B_{ik} \sin \theta_{ik})$$
- This is **NOT** the case, and only would yield the correct answer if the transmission lines are lossless
- To find the power flowing on the individual lines, you can use

$$S_{i0} = \mathbf{V}_i (\mathbf{I}_{i0})^* + |\mathbf{V}_i|^2 (\mathbf{I}_{i0})^* = \mathbf{V}_i \left(\sum_{k=1}^n \mathbf{Y}_{ik} \mathbf{V}_k \right)^*$$
 where \mathbf{I}_{i0} is the current through the shunts connected to bus 1, if any

Dr. Louie 30



Example

- A similar statement can be made for the imaginary power flowing from bus 1 to bus 2
- The value corresponding to $i=1$ and $k=2$, in general, has no physical meaning, rather it is simply an element in an equation

Dr. Louie

31



Power Flow

- In general, when calculating the power flowing from bus m to bus n , the power flowing into the shunts from a π -modeled transmission line are included
- If the complex power flowing from bus m to all other buses is summed and added to the power flowing to any non-transmission line related shunts at bus m , then the resulting power is equal to S_m

Dr. Louie

32



Power Flow Problem

- As in our \mathbf{Y}_{bus} discussion, we generally do not know the voltage information at each bus
- Often, we know and can control the **voltage magnitude** and the **real power input** at buses with generators
- If a bus only has a load, we only know the **real and reactive power demand**
- Solving for bus voltage magnitudes and angles is known as the **power flow problem**


Dr. Louie

33



Power Flow Problem

- Solving the power flow equations for $|V|$ and θ is very difficult
- For example, given $V_1 = 1.0$
 $P_2 = -1.2$
 $Q_2 = -1$
- Find $|V_2|$ and θ_2
- Two unknowns, so we need two equations:

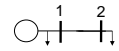

$$P_2 = -1.2 = |V_2|^2 G_{22} + 1|V_2|(G_{21} \cos \theta_2 + B_{21} \sin \theta_2)$$

$$Q_2 = -1.0 = -|V_2|^2 B_{22} + |V_2|1(G_{21} \sin \theta_2 - B_{21} \cos \theta_2)$$

Dr. Louie

34



Power Flow Problem

- Problem is nonlinear, so it is difficult to solve
 $P_2 = -1.2 = |V_2|^2 G_{22} + 1|V_2|(G_{21} \cos \theta_2 + B_{21} \sin \theta_2)$
 $Q_2 = -1.0 = -|V_2|^2 B_{22} + |V_2|1(G_{21} \sin \theta_2 - B_{21} \cos \theta_2)$
- Imagine a similar problem on a three bus system (equations are coupled)
- Clearly, finding the exact solution is going to take some work
- Luckily, we don't need an exact solution. Only a solution that is "close" to the answer
- If the exact solution was $|V_2| = 0.98554$, we might be satisfied with a solution that is $|V_2| = 0.98521$

Dr. Louie

35



Power Flow Problem

- Use some numerical methods to approximate the solution to the power flow problem
- We first need to have a better definition of the problem

Dr. Louie

36



Power Flow Problem: Terminology

- Generator Bus: a bus with a connected generator
 - voltage magnitude can be controlled by adjusting the exciter current
 - real power can be controlled by adjusting power to the prime mover
- Load Bus: a bus without a generator
 - real and reactive power are known

Dr. Louie

37



Power Flow Problem: Slack Bus

- Since we do not know how much power is flowing on each line, we cannot know in advance the real power out of each generator and load. Why?
 - **losses!** The amount of losses are not know beforehand
 - Even in a lossless system, the total power generated must equal the power at each load. With a given system load, all but 1 generator real power can be specified
- The generator without its real power specified is known as the "slack bus"

Dr. Louie

38



Power Flow Problem: Terminology

- Generator Bus: a bus with a connected generator
 - voltage magnitude can be controlled by adjusting the exciter current
 - real power can be controlled by adjusting power to the prime mover
- Load Bus: a bus without a generator
 - real and reactive power are known
- Slack Bus: a generator bus without its real power specified
 - voltage magnitude is controlled
 - voltage angle is set as the reference
 - usually numbered bus 1
 - Only one slack bus in each system

Dr. Louie

39



Power Flow Problem

- For each bus type, there are two variables that can be specified (controlled)
- We can also call
 - generator bus: PV bus
 - load bus: PQ bus
- There are certain cases in which a generator may not be PV, or a load not PQ, for example:
 - certain wind turbines
 - load buses with controlled capacitor banks

Dr. Louie

40



Power Flow Problem

- we are interested in solving nonlinear equations using numerical methods
- numerical methods are iterative and provide solutions that are exact to within a tolerance
- We will use Newton-Raphson to solve the problem

Dr. Louie

41