

24-DC Generators Part 2

Text: 5.9 – 5.16

ECEGR 450
Electromechanical Energy Conversion



Overview

- DC Generator Types
- Separately Excited Generator Model
- Shunt Generator Model
- Series Generator Model
- Compound Generator Model
- Voltage Regulation

2



DC Generator Types

DC generators can be classified by excitation method

- Separately-Excited
 - Excitation current supplied by external source
 - Field winding or PM
- Self-Excited
 - Excitation current self supplied

Dr. Louise

3



DC Generator Types

- Self-excited generators can also be classified based upon how the excitation winding is connected:
 - Series
 - Shunt (parallel)
 - Compound (combination of series and shunt)


Dr. Louise

4



Generator Types

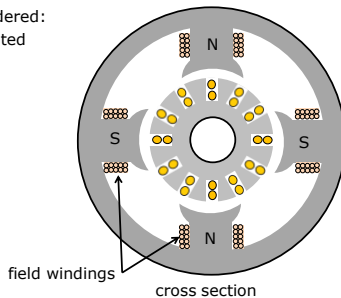- Three types considered:
 - Separately excited
 - Shunt
 - Series
 - Compound



Dr. Louise

5



Separately Excited Generator

- DC generator in which a external dc source is used to generate the field current
- External source can be
 - Battery
 - Another DC generator
 - Rectified AC

Dr. Louise

6

Separately Excited Generator Model

Equivalent circuit shown

- v_t : generator terminal voltage (V)
- v_f : applied field winding voltage (V)
- R_{fw} : field winding resistance (Ohm)
- R_{fx} : adjustable field winding resistance (Ohm)
- R_a : armature resistance (Ohm)
- X_f : field winding reactance (Ohm)

field circuit generator circuit

Dr. Louie 7

Separately Excited Generator

- Assume generator is operating in steady state
 - mechanical energy does not change
 - inductance (X_f) behaves a short circuit
- R_{fx} is used to control the field current, and hence the flux

Dr. Louie 8

Separately Excited Generator Model

Circuit equations:

$$v_f = i_f(R_{fw} + R_{fx}) = i_f R_f$$

$$E_a = v_t + i_a R_a$$

$$i_L = i_a$$

field circuit generator circuit

Dr. Louie 9

Separately Excited Generator

- If i_f and ω_m are constant, then E_a is independent of the armature current
- As load increases (i_L increases), the terminal voltage drops due to R_a
- $V_{tnl} = E_a$ (no load terminal voltage = induced emf)

Dr. Louie 10

Separately Excited Generator

terminal voltage (V)

load current (A)

$V_{tnl} = 250V$

Voltage drop due to R_a

Voltage drop due to armature reaction

Dr. Louie 11

Shunt Generator

- Terminals of the generator are connected to the field winding
- Defining equations:

$$v_t = i_f(R_{fw} + R_{fx}) = i_f R_f$$

$$v_t = E_a - i_a R_a$$

$$i_a = i_L + i_f$$

Dr. Louie 12



Shunt Generator

- Under no load $i_a = i_f$
- R_f is usually large since v_t can be large
 - Large number of turns of small gauge
- E_a will be 0 since there is no flux created by field winding ($i_a = 0$)

Dr. Louie

13



Shunt Generator

- However, generally there is residual magnetism in the stator and a small amount of voltage will be induced
 - i_a increases, which increases E_a , which increases i_a , and so on
 - process does not continue forever
 - saturation of the stator limits the process


Dr. Louie

14



Shunt Generator

Voltage build-up process

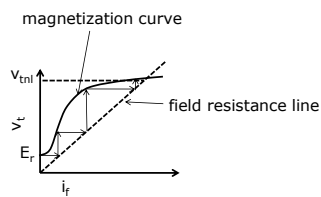

Dr. Louie

15



Shunt Generator

- The no-load voltage depends upon the field-circuit resistance
- Smaller resistances increase the rate of build-up
- If the resistance is too large (greater than the "critical resistance") then voltage build-up does not occur
- See Figure 5.24 for an example

Dr. Louie

16



Shunt Generator

- Under no load: $i_a = i_f$
 - V_t is nearly equal to E_a since $i_a R_a$ is small
- As i_l increases
 - $i_a R_a$ increases
 - Armature reaction demagnetization effect increases
- Hence, E_a decreases
 - This further lowers i_f and E_a

Dr. Louie

17



Shunt Generator

- If the load resistance continues to decrease, the load current will also start to decrease
 - due to the decrease in terminal voltage
- If the terminals are shorted, the field current becomes zero, but current still flows due to the residual magnetism E_r

Dr. Louie

18

Shunt Generator

Dr. Louie 19

Shunt Generators

- Shunt generators must operate in the saturated region
- Otherwise, an increase in load would appreciably decrease the field current, which would have a large effect on E_a
 - i_f would further drop and so on
- Operation in the saturated region desensitizes the change in flux due to the change in field current

Dr. Louie 20

Series Generator

- Field winding is placed in series with armature and external circuit
- A series field diverter resistance (R_d) is used to control the flux
- Defining equations:
 - $v_t = E_a - i_a R_a - i_a R_s$
 - $i_s = i_L = i_a + i_d$
 - $i_a R_s = i_d R_d$

Dr. Louie 21

Series Generator

- When under no load, the produced flux in the field is zero
 - E_a is equal to 0
- As load increases, flux increases
 - E_a increases
- Terminal voltage drops due to series resistance and armature reaction
- E_a and v_t are functions of the load current

Dr. Louie 22

Series Generator

- Note: $i_L = i_a$
- Terminal voltage increases with load current
- As i_L increases, it is possible to drive the terminal voltage to zero due to armature reaction

Magnetization curve

Dr. Louie 23

Compound Generator

- Terminal voltage:
 - Decreases with load in a shunt generator
 - Rises with load in a series generator
- Combine them into a single generator
- Known as a "Compound Generator"
- Several types, depending on how they are wound

Dr. Louie 24

Compound Generator

The diagram shows two pole pieces labeled 'S'. In the left configuration, labeled 'Cumulative (mmfs add)', the series winding current i_s and shunt winding current i_r both flow in the same direction, indicated by arrows pointing to the right. In the right configuration, labeled 'Differential (mmfs subtract)', the series winding current i_s flows to the right while the shunt winding current i_r flows to the left.

Dr. Louie 25

Compound Generator

- Short-shunt compound:
 - series winding is in between the shunt and load
- Long-shunt compound:
 - Shunt winding connected directly across the load

Dr. Louie 26

Compound Generator

- A long-shunt cumulative generator

The circuit diagram shows an armature circuit with induced EMF E_a and current i_a . The armature resistance is R_a . The field circuit is connected in shunt across the armature terminals. It consists of a field winding with resistance R_{fw} and N_f turns, and a series field winding with resistance R_s and N_s turns. The field current is i_f . The series field current is i_d . The terminal voltage is V_t and the load current is i_l . The series field winding is connected between the positive terminal and the junction between the armature and the field winding.

Dr. Louie 27

Compound Generator

- A long-shunt differential generator

The circuit diagram is similar to the long-shunt cumulative generator, but the series field winding with resistance R_s and N_s turns is connected between the positive terminal and the negative terminal, in parallel with the field winding.

Dr. Louie 28

Compound Generator

- In any configuration:
 - Shunt winding provides the majority of the flux
 - Series winding controls the total flux
- Adjusting the current through the series winding allows for three different degrees of compounding:
 - Under-compound
 - Normal compound
 - Over-compound

Dr. Louie 29

Compound Generator

- Under-compound generator
 - Full-load voltage is slightly higher than in a shunt generator, but still lower than no-load voltage
 - Voltage regulation is better than in a shunt generator
- Flat-compound generator
 - Full-load voltage is equal to the no-load voltage
 - Voltage regulation is better than in a shunt generator

Dr. Louie 30



Compound Generator

- Over-compound generator
 - Full-load voltage is higher than no-load voltage
 - Useful when connected to a long transmission line (to compensate for the voltage drop)
 - Compound generators are usually over-compound
 - See text for more details and comparison of generator types (Figure 5.32)

Dr. Louie

31



Voltage Regulation

- In all dc generators, as current (load) increases, the terminal voltage drops
 - Ohmic losses in the armature
 - Armature reaction
- The voltage drop is desired to be minimal
- Voltage Regulation is a metric for quantifying the voltage drop with respect to load

Dr. Louie

32



Voltage Regulation

$$VR = \frac{V_{nL} - V_{fL}}{V_{fL}} \times 100$$

- VR: percent voltage regulation (%)
- V_{nL} : terminal voltage under no load (V)
- V_{fL} : terminal voltage under full load (V)
- Ideal voltage regulation is 0%

Dr. Louie

33



Summary

- DC generators are less commonly used machines
- DC generators come in several varieties:
 - External (separately excited)
 - Series
 - Shunt
 - Compound
- Residual magnetism is used to “build up” voltage in self-excited generators

Dr. Louie

34