


30-Induction Machine Models


ECEGR 450
Electromechanical Energy Conversion



Overview

- Introduction
- General Characteristics
- Blocked Rotor Induction Motor Model
- Induction Motor Model
- Effective Resistance
- Induction Motor Power
- Induction Motor Torque
- Example


Dr. Louie 2



Questions

- Can an induction motor be used as an induction generator?
- What is the speed versus torque characteristic of an induction motor?
- What are the losses in induction motors?


Dr. Louie 3




Introduction

- We now analyze balanced three phase induction machines
- Focus is on Induction Motors (models are same for induction generators)


Dr. Louie 4



General Characteristics

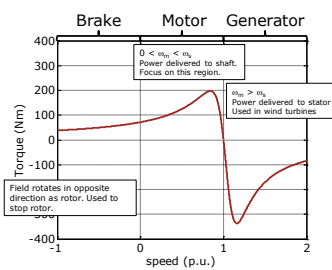


Dr. Louie 5









General Characteristics

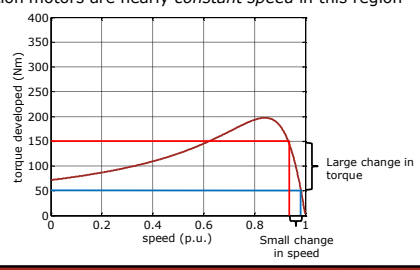Slip is generally low < 5%
Induction motors are nearly *constant speed* in this region



Dr. Louie 6

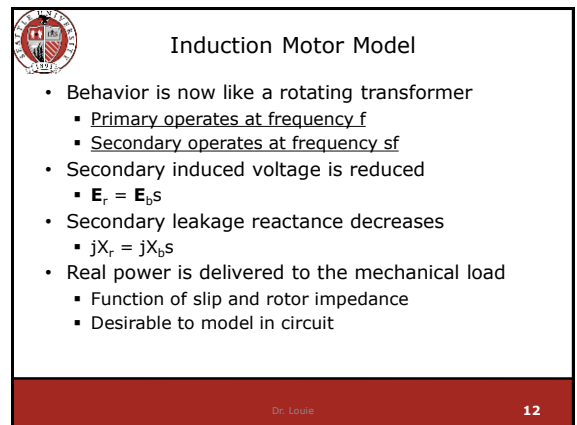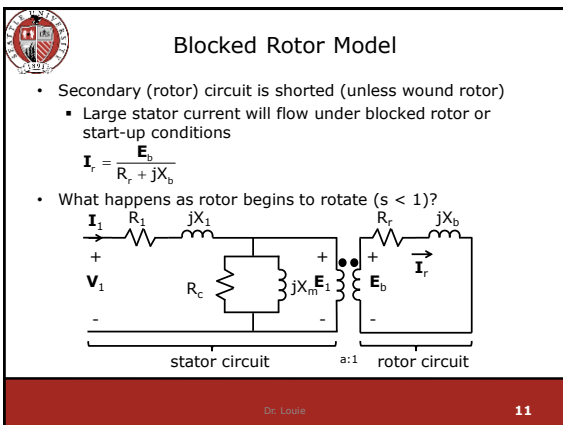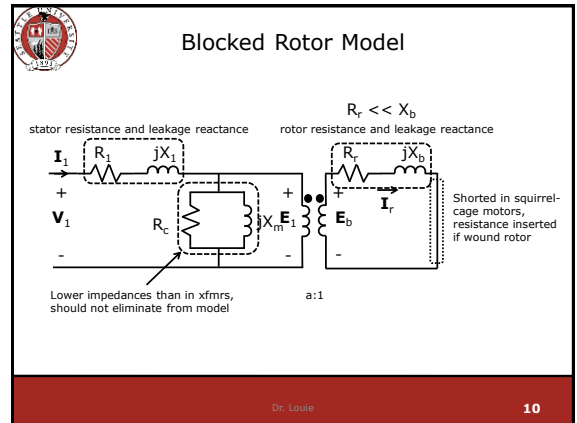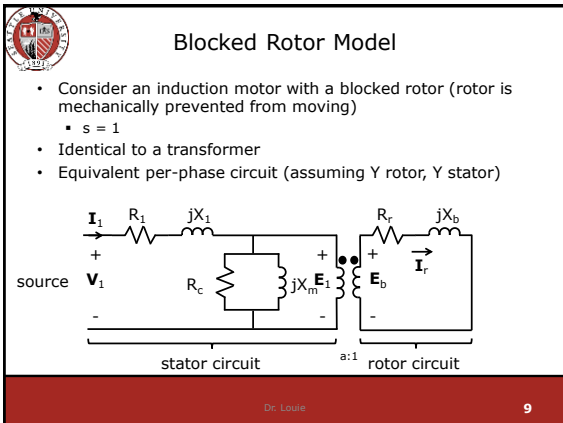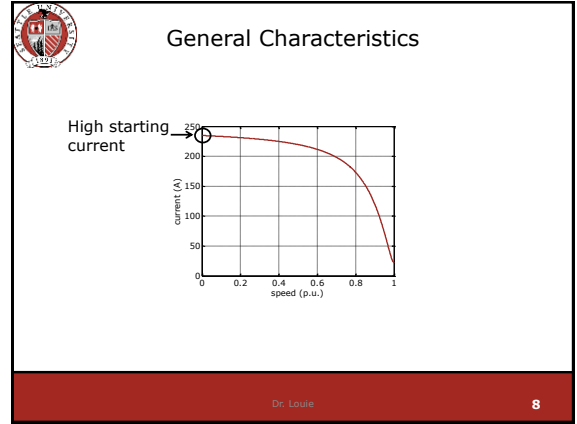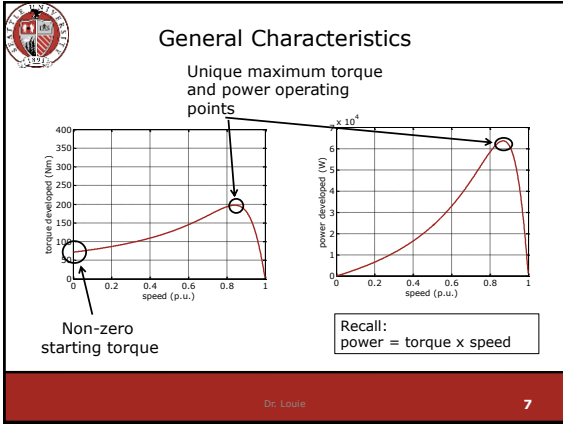

Induction Motor Model

- Note: V_1 , E_1 , I_1 , and E_b , I_r have different frequencies (f , sf)
- Solving secondary (rotor) circuit:

$$I_r = \frac{sE_b}{R_r + jsX_b}$$

frequency f a:1 frequency sf

Dr. Louie 13

Induction Motor Model

- Customary to write rotor current as:

$$I_r = \frac{sE_b}{R_r + jsX_b} = \frac{E_b}{R_r/s + jX_b} \quad (\text{divide numerator and denominator by } s)$$

frequency f a:1 frequency sf

Dr. Louie 14

An Observation

- Examine the previous operation:

$$I_r = \frac{sE_b}{R_r + jsX_b} = \frac{E_b}{R_r/s + jX_b} \quad (\text{divide numerator and denominator by } s)$$

- Current value is preserved, but are the circuits equivalent?
- Example:

Circuit 1 ? Circuit 2

Dr. Louie 15

An Observation

- Current is the same, but power is not
 - Circuit 1: $P_1 = I_r^2 R_1$
 - Circuit 2: $P_2 = I_r^2 2R_1 \neq P_1$
- Division by s does not preserve power
- Since $s < 1$, the new equivalent circuit is consuming power in R_r/s in addition to rotor copper loss

Circuit 1 ? Circuit 2

Dr. Louie 16

Effective Resistance

- R_r/s is the effective resistance
- Hypothetical, accounts for rotor copper losses and mechanical power delivered to load
- If $s = 1$, effective resistance is the rotor resistance
- If $s = 0$, effective resistance is inf

frequency f a:1 frequency sf

Dr. Louie 17

Induction Motor Model

- More convenient to eliminate ideal xfmr in circuit model
- Refer secondary side to primary (stator)
- Transformation ratio: $a = \frac{N_1 k_{a1}}{N_2 k_{a2}}$ (assume k_{a1}, k_{a2} are equal for now)
- Quantities become:

$$R_2 = a^2 R_r$$

$$X_2 = a^2 X_b$$

$$I_2 = \frac{I_r}{a}$$

Dr. Louie 18

Induction Motor Model

- Per-phase stator current: $\mathbf{I}_1 = \mathbf{I}_\phi + \mathbf{I}_2$
- Low speeds ($s \sim 1$): high current
- High speed ($s \sim 0$): low current

Dr. Louie 19

Induction Motor Power

- Per-phase power delivered to the rotor: $P_{r,\phi} = \frac{|\mathbf{I}_2|^2 R_2}{s}$
 - Copper loss
 - Power developed (available to shaft)
- Per-phase copper loss: $P_{r,cu,\phi} = |\mathbf{I}_2|^2 R_2$
- Per-phase power developed:

$$P_{d,\phi} = \underbrace{\frac{|\mathbf{I}_2|^2 R_2}{s}}_{P_{r,\phi}} - \underbrace{|\mathbf{I}_2|^2 R_2}_{P_{r,cu,\phi}} = |\mathbf{I}_2|^2 R_2 \left(\frac{1-s}{s} \right)$$

Dr. Louie 20

Effective Resistance

- Effective resistance can be decoupled into copper loss resistance, and resistance representing mechanical power

$$\frac{R_2}{s} = \underbrace{R_2}_{\text{rotor copper}} + \underbrace{R_2 \left(\frac{1-s}{s} \right)}_{\text{load resistance}}$$

Dr. Louie 21

Effective Resistance

Dr. Louie 22

Induction Motor Power

- Total input power to induction motor: $P_{in} = 3V_1 I_1 \cos \phi$
- Total stator copper loss: $P_{s,cu} = 3 |\mathbf{I}_1|^2 R_1$
- Total stator core loss: $P_m = 3 |\mathbf{I}_c|^2 R_c$
- Remaining power must be delivered to rotor (air-gap power):

$$P_{ag} = P_{in} - P_m - P_c = \frac{3 |\mathbf{I}_2|^2 R_2}{s} = 3 P_{r,\phi}$$

Dr. Louie 23

Induction Motor Power

- Total rotor copper loss: $P_{r,cu} = 3 P_{r,cu,\phi} = 3 |\mathbf{I}_2|^2 R_2 = s P_{ag}$
 - Percentage of air gap power consumed by electrical losses is s
- Mechanical power developed by the motor:

$$P_d = P_{ag} - P_{r,cu} = \frac{3 |\mathbf{I}_2|^2 (1-s) R_2}{s} = (1-s) P_{ag}$$

- Subtracting rotational losses yields total power output by the motor: $P_{out} = P_d - P_{rot}$

Dr. Louie 24

Induction Motor Torque

- The total developed torque is:

$$T_d = \frac{P_d}{\omega_m} = \frac{P_{ag}}{\omega_s} = 3 |I_2|^2 \frac{R_2}{s\omega_s}$$
- The total output torque is:

$$T_{out} = \frac{P_{out}}{\omega_m}$$

Dr. Louie 25

Induction Motor Torque

- Torque is non-zero at starting ($s = 1$)
- Torque is zero at synchronous speed ($s = 0$)
 - I_2 is zero

Dr. Louie 26

Approximate Circuit

- R_1, X_1 are designed to be minimized
- R_c, X_m designed to be maximized
- Per-phase circuit can be simplified (approximated)

Dr. Louie 27

Approximate Circuit

Move R_1, X_1 past shunt branch and combine with R_2, X_2

- $R_e = R_1 + R_2$
- $X_e = X_1 + X_2$

Dr. Louie 28

Approximate Circuit

- Further simplifications:
 - replace core resistance with constant power loss
 - Assume rotational losses are constant

Dr. Louie 29

Example

- A 60 Hz, 480-V, wye-connected induction motor has the following constants (referred to the stator)
 - $R_1 = 0.322 \Omega; R_2 = 0.196 \Omega; X_1 = 0.675 \Omega;$
 - $X_2 = 0.510 \Omega; X_m = 12.5 \Omega$
 - Rotational and core losses: 1850 W
- The motor operates at a slip of 3% (3492 RPM). Compute the stator current and the power factor of the motor using the approximate model.

Dr. Louie 30

Example

- A 60 Hz, 480-V, wye-connected induction motor has the following constants (referred to the stator)
 - $R_1 = 0.322 \Omega$; $R_2 = 0.196 \Omega$; $X_1 = 0.675 \Omega$;
 - $X_2 = 0.510 \Omega$; $X_m = 12.5 \Omega$
 - Rotational and core losses: 1850 W

Dr. Louie 31

Example

- Compute stator current by KCL: $I_1 = I_0 + I_2$

$$I_1 = \frac{277.13\angle 0^\circ}{12.5\angle 90^\circ} + \frac{277.13\angle 0^\circ}{6.858 + j1.185} = 22.17\angle -90^\circ + 39.83\angle -9.8^\circ$$

$$= 48.78\angle -36.42^\circ \text{ A}$$

- Compute the power factor:
 - PF: $\cos(-36.42^\circ) = 0.805$ (lagging)

How does this compare if the exact circuit model is used?

Dr. Louie 32

Example

Consider the motor in the previous example. Compute the input power and stator copper losses.

Dr. Louie 33

Example

- The stator and copper losses are:
 - $P_{\text{input}} = 3 |V_1| |I_1| \cos \phi = 32,634 \text{ W}$
 - $P_{s,\text{cu}} = 3 |I_2|^2 R_1 = 1,533 \text{ W}$

Dr. Louie 34

Example

Consider the motor in the previous example. Compute the air gap power, power developed and power output of the motor.

Dr. Louie 35

Example

Consider the motor in the previous example.

$$P_{\text{ag}} = P_{\text{in}} - P_{s,\text{cu}} = 31,101 \text{ W}$$

$$P_d = (1 - s)P_{\text{ag}} = 30,168 \text{ W}$$

$$P_{\text{out}} = P_d - P_{\text{rot}} = 28,318 \text{ W}$$

Efficiency: $P_{\text{out}}/P_{\text{in}} = 86.77\%$

Dr. Louie 36



Example

Consider the motor in the previous example.
Compute the torque developed and the output torque.

Dr. Louie

37



Example

Consider the motor in the previous example.
Compute the torque developed and the output torque.

$$\omega_m = \frac{3492 \times 2\pi}{60} = 365.8 \text{ (rad/s)}$$

$$T_d = \frac{P_d}{\omega_m} = 82.49 \text{ Nm}$$

$$T_{out} = \frac{P_{out}}{\omega_m} = 77.43 \text{ Nm}$$

Dr. Louie

38



Summary

- Induction motors are nearly constant speed
- Non-linear torque, power and current vs speed relationship
- Induction machine model is based on transformer model
- $R_s \left(\frac{1-s}{s} \right)$ term is the load resistance, which represents mechanical output

Dr. Louie

39